



## IV SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING) END SEMESTER EXAMINATIONS, APRIL - MAY 2017

### ANALOG SYSTEM DESIGN [ELE2204]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 28, April 2017

Max. Marks: 50

#### Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A. In the circuit shown in fig Q1a, determine the signs of op-amp such that dominant feedback is negative feedback. Determine  $V_o/V_i$ . (03)
- 1B. Using just one op-amp powered from  $\pm 12$ -V regulated power supplies, design a circuit to yield  $V_o(t) = (V_1 - 10V_2 - 5)$  V, where  $V_1$  and  $V_2$  are signals. Use a resistor of  $10\text{ k}\Omega$  between output and inverting terminal of the op-amp. (04)
- 1C. What is the highest frequency of a triangle wave of 10-V peak-to-peak amplitude that can be reproduced by an op amp whose slew rate is  $10\text{ V}/\mu\text{s}$ ? For a sine wave of the same frequency what is the maximum amplitude of output signal that remain undistorted? (03)
- 2A. With a neat circuit diagram, derive the expression for voltage gain of 3 op-amp instrumentation amplifier. State the advantages of this circuit compared to difference amplifier used for the same purpose. (04)
- 2B. For the circuit shown in fig Q2b, obtain an expression for output voltage in time domain. Hence comment on the working of the circuit with respect to the input applied. (03)
- 2C. Design an op-amp based system which adds a delay of  $70\mu\text{s}$  to a signal  $V_i(t) = 2 \sin 4000\pi t$  when passing through it. Use a capacitor of  $0.1\mu\text{F}$  if required. (03)
- 3A. Design an op-amp based system which receives an input of  $V_i(t) = \sin 2000\pi t + 2 \sin 12000\pi t + 3 \sin 16000\pi t + \sin 30000\pi t$  to produce an output of  $V_o(t) = 2 \sin 2000\pi t + 2 \sin 30000\pi t$ . Assume that the system has maximally flat response and the transition band roll off  $60\text{ dB/decade}$ . Derive the relevant expressions which justifies the required gain to be used in the system. Use a capacitor of  $0.1\mu\text{F}$  if required. (05)
- 3B. With a neat circuit diagram and waveforms, discuss the working of a full wave precision rectifier. (02)
- 3C. Design a suitable op-amp based circuit to obtain the output waveform shown in fig Q3c. Hence draw the voltage transfer characteristics. Assume the resistance connected between the op-amp output and non-inverting terminal as  $10\text{ k}\Omega$ . (03)
- 4A. With a neat circuit diagram discuss the working of an op-amp based triangular waveform generator. Derive the expression for the frequency of the output. (03)
- 4B. Design a 555 timer based circuit which can produce a pulse train of  $3\text{ kHz}$  with  $50\%$  duty cycle. Use capacitors of  $0.1\mu\text{F}$  if required. (03)

- 4C.** Design a 555 timer based circuit which can produce a pulse of 8ms along with the trigger circuit. Assume capacitors of  $0.01\mu\text{F}$  if required. (04)
- 5A.** Draw the equivalent circuit of a voltage Amplifier. What conditions must be satisfied if this amplifier is to behave ideally? (02)
- 5B.** Derive expressions for input and output Resistances with feedback for a Transconductance Amplifier. (03)
- 5C.** With a neat circuit diagram, discuss the working of Opamp based voltage controlled Oscillator. (03)
- 5D.** Identify the feedback topology of the circuits shown in fig Q5d and determine the value of  $\beta$  if  $R_S=1\text{K}$ ,  $R_D=5\text{K}$ ,  $R_F=100\text{K}$ ,  $R=10\text{K}$ . (02)

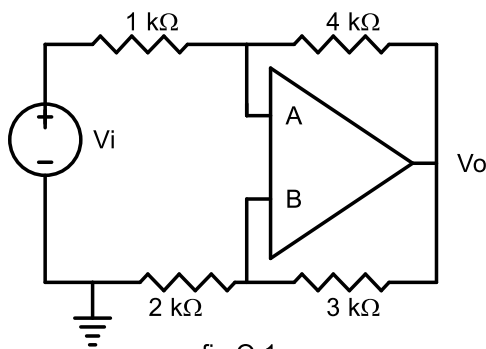


fig Q.1a

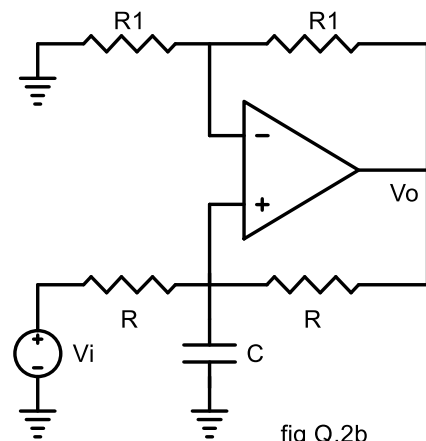


fig Q.2b

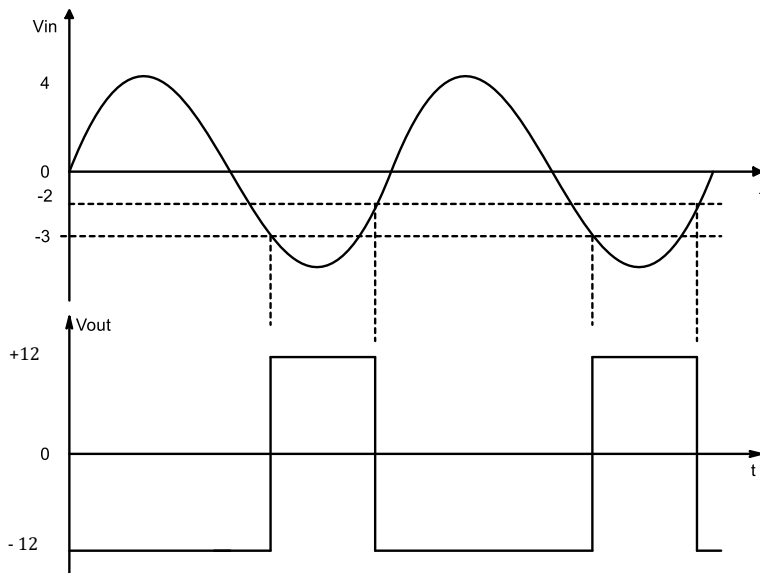


fig Q.3c

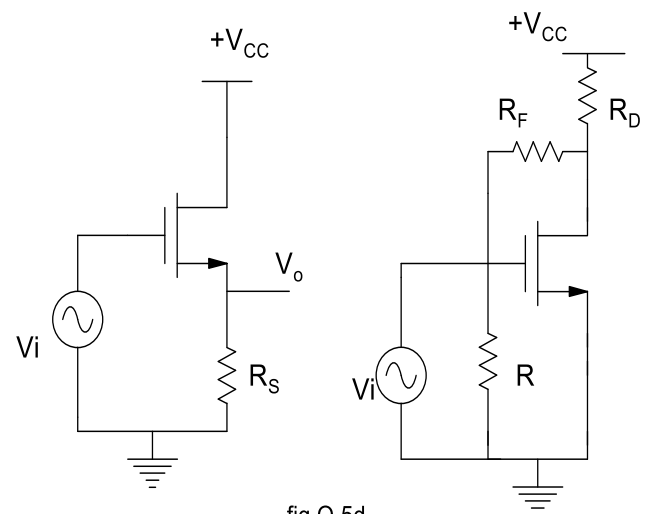


fig Q.5d