



FOURTH SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.)

END SEMESTER EXAMINATIONS, JUNE 2017

SUBJECT: ANALOG SYSTEM DESIGN [ICE 2204]

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ALL** questions.
- ❖ Missing data may be suitably assumed.

- 1A. Define slew rate. Explain the causes of slew rate. 2
- 1B. Explain briefly each stage of the op-amp internal circuit with its block schematic. 5
Draw the basic differential amplifier circuit using transistors and explain how the output voltages change when a difference mode signal is applied.
- 1C. Design a circuit such that $V_o = 6V_2 - 4V_1$. 3
- 2A. Draw the circuit diagram of a voltage to current converter with grounded load. 3
Derive the expression for load current.
- 2B. Obtain the transfer function between input and output voltages of Fig. Q2B. 3
- 2C. Draw the circuit for a twin T notch filter. Derive its transfer function. 4
- 3A. Draw the circuit diagram of monostable multivibrator using op-amp. With the help of waveforms, derive the expression for pulse width. 5
- 3B. Describe the working of astable multivibrator using 555 timer. 3
- 3C. Draw the circuit of a Schmitt trigger using 555 timer and explain its operation. 2
- 4A. Derive the expression for frequency of oscillation for Wien bridge oscillator with circuit diagram. 4
- 4B. Explain the working principle of Phase Locked Loop with block diagram. 4
- 4C. Design RC phase shift oscillator with $f_o = 1.5\text{KHz}$. Assume $C = 0.01\mu\text{F}$. 2
- 5A. Describe the working of counter type ADC with block diagram and relevant waveforms. List its disadvantages. 4
- 5B. Determine the output of an R-2R Ladder Digital to Analog Converter with input 0001. 4
- 5C. Define Linearity and Accuracy for a Digital to Analog Converter. 2

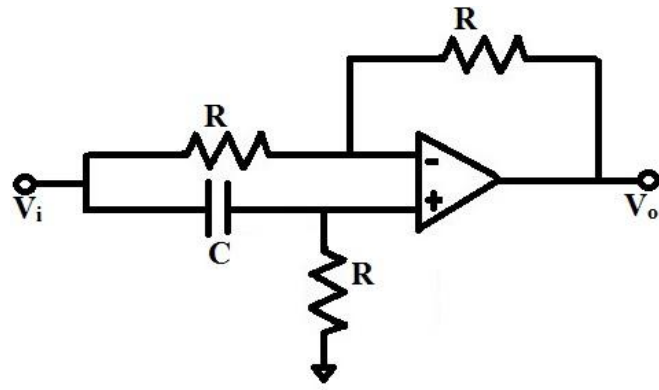


Fig. Q2B

***** END *****