



### II SEMESTER M.TECH (ESM/PED) MAKE UP EXAMINATIONS JUNE 2017

#### SUBJECT: POWER QUALITY ISSUES & MITIGATION [ELE 5238]

REVISED CREDIT SYSTEM

**Time: 3 Hours**

**Date: 17 June 2017**

**Max. Marks: 50**

#### Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A. What are the power quality problems that the hybrid power filters can mitigate? (02)
- 1B. How the power quality problems are classified? (03)
- 1C. Explain with a neat block diagram of unit template based control algorithm of three-leg VSC based three-phase 3-wire DSTATCOM for ZVR mode of operation (05)
- 2A. How the passive shunt compensators are classified based on supply/load systems. (03)
- 2B. Why an indirect current control method is superior when compared to the direct current control scheme of a DSTATCOM. (02)
- 2C. A single phase 230V, 50Hz, AC mains with feeder impedance of  $0.5 + j3\Omega$  supplies power to the load having  $Z_L = 16 + j12\Omega$ . Determine the voltage across the load. If a PWM based SSSC is used to regulate the load voltage to 230V with minimum rating, determine the VA rating of the compensator. (05)
- 3A. How the passive power filters are classified based on the connection used with neat sketches. (03)
- 3B. A single-phase shunt active power filter is used for harmonic current compensation at UPF for a single-phase 230V, 50Hz, AC source supplying load through diode bridge converter with 22A constant DC current. Determine the current and VA rating of shunt active power filter. (03)
- 3C. A single phase AC mains with source impedance supplies power to a single phase lagging p.f. load. Derive the expression for the susceptance of the shunt compensator to get unity p.f. at the substation. (04)
- 4A. Explain with a neat block diagram of synchronous reference frame theory based control algorithm for a three-phase four-wire VSC based UPQC for the operation of the DSTATCOM and DVR. (07)
- 4B. Determine percentage current unbalance in a 3-phase 3-wire system with three phase unbalanced load currents  $I_a = 9\angle 0^\circ A$ ,  $I_b = 11\angle 240^\circ A$  and  $I_c = 9.5\angle 120^\circ A$ . (03)
- 5A. A three phase four-wire 415 V, 50 Hz AC supply has a single phase 10 kW resistive load connected across line (say R-phase) and neutral terminal. If it is required to eliminate the neutral current using a shunt compensator. Determine
  - (i) Supply line currents
  - (ii) The values of compensator elements (L or C)
  - (iii) kVA rating of the compensator (05)
- 5B. Derive the expressions for the susceptances of the passive shunt compensator for load balancing and p.f. correction (UPF) of a three phase three-wire delta connected unbalanced load. (05)