



**MANIPAL
UNIVERSITY**



Question Paper

26-Apr-2017 12:46:51
TECHNICAL SUPPORT

[Support](#) | [Change Password](#) | [Logout](#)

[Basic Masters](#)

[Question Paper](#)

[Device & Dockets](#)

[Evaluation](#)

[Evaluation Reports](#)

[Reports](#)

[Utilities](#)



Select Exam Event SOIS End Semester April 2017 ▼

☐ Show answer keys for MCQ.

[Back](#)



MANIPAL UNIVERSITY

SCHOOL OF INFORMATION SCIENCES (SOIS)

SECOND SEMESTER MASTER OF SCIENCE - M.Sc. Tech /MASTER OF ENGINEERING - ME(VLSI DESIGN)

DEGREE EXAMINATION-APRIL / MAY 2017

Wednesday, 26, 2017

Time : 10:00 AM - 1:00 PM

Advanced VLSI Design [EDA 604]

Marks: 100

Duration: 180 mins.

A

Answer all the questions.

- 1) A) Explain the effect of Temperature and Voltage on CMOS Resistor. (10)
B) Estimate the minimum and maximum resistance of an n-well resistor with a length of 100μm and a width of 10μm over a temperature range of 0 to 100°C.
[Data Given: TCR = 10,000ppm/°C; N-well sheet resistance = 2KΩ to 3KΩ / square]
- 2) Starting from a general 2-port network, derive a complete low frequency, small signal model for a MOSFET. (10)
- 3) Draw and explain the circuit of Cascode Current Mirror and show that output resistance of the n-stage cascode current mirror $R_{o(n)} = r_o(1+g_m R_{o(n-1)}) + R_{o(n-1)}$, where r_o is output resistance of all the MOSFETs, g_m is the transconductance of all the MOS used in the circuit. (10)
- 4) With a diagram, explain cascode current mirror. What are its advantages over a simple current mirror? (10)
- 5) Draw a neat schematic and explain the Thermal Voltage Referenced Self-Biasing circuit (10)
- 6) What is differential amplification? What are its advantages over single-ended amplification? (10)
- 7) What are the advantages of switched-capacitor circuits? With the help of a simple diagram, explain a switched-capacitor resistor circuit (10)
- 8) (10)

With a neat schematic diagram showing all three stages, explain the working of a CMOS nonlinear analog comparator circuit

- 9) Discuss the different errors that occur in a Sample-and-Hold circuit (10)
- 10) With relevant diagrams, explain the working of Current Steering DAC. Derive an expression for its $|INL|_{\max}$ and $|DNL|_{\max}$ (10)



Copyright @ 2017 Littlemore Innovation Labs Pvt Ltd. IP: 52.66.163.73 epCloud 1.5
All rights reserved.

[^Top](#)