



**MANIPAL  
UNIVERSITY**



# Question Paper

28-Apr-2017 11:17:54  
TECHNICAL SUPPORT

[Support](#) | [Change Password](#) | [Logout](#)

[Basic Masters](#)

[Question Paper](#)

[Device & Dockets](#)

[Evaluation](#)

[Evaluation Reports](#)

[Reports](#)

[Utilities](#)



Select Exam Event SOIS End Semester April 2017 ▼

☐ Show answer keys for MCQ.

[Back](#)



## MANIPAL UNIVERSITY

**SCHOOL OF INFORMATION SCIENCES (SOIS)  
SECOND SEMESTER MASTER OF ENGINEERING - ME (VLSI DESIGN)  
DEGREE EXAMINATION - APRIL 2017  
Friday, 28, 2017  
Time : 10:00 AM - 1:00 PM**

### Physical Design [EDA 616.8]


Marks: 100

Duration: 180 mins.

**A**

#### Answer all the questions.

 - 1) State the static properties of Complementary CMOS Gates. Compare the Voltage Transfer Curves for of a two input NAND gate for different input combinations. (10)
- 2) What is Dynamic Logic in VLSI? Write a schematic of a four input NOR gate using Dynamic Logic. (10)
- 3) What is aspect ratio? Mention its effects in Floorplanning (10)
- 4) Explain Power Planning stage in Floorplanning of a VLSI chip (10)
- 5) Explain cluster and region in global placements (10)
- 6) What are the objectives of routing? Explain complete graph, Steiner minimal tree and half-perimeter methods in routing (10)
- 7) What are the advantages of modelling physical fault as a logical faults? Find out the collapse ratio for a two input XNOR gate built using NOR gates only. (10)
- 8) Explain stored pattern and pseudo exhaustive pattern generation (10)
- 9) Give the parallel vector pattern for finding the stuck at faults shown in the circuit. (10)



- 10) Define Fault Model, Fault Coverage, Fault Simulation, Fault Equivalence, Fault (10)  
Dominance in VLSI testing



Copyright @ 2017 Littlemore Innovation Labs Pvt Ltd. IP: 52.66.163.73 epCloud 1.5  
All rights reserved.