



VI SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING) MAKE-UP EXAMINATIONS JUNE 2017

SUBJECT: POWER ELECTRONICS [ELE 3201]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 13 June 2017

Max. Marks: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.
- ❖ Sine Graphs shall be supplied

- 1A. With the help of a neat sketch, discuss the I - V characteristics of an SCR, with brief discussion on each region of operation of SCR. (04)
- 1B. Draw a neat circuit for forced voltage commutation of an SCR. Hence, plot the waveforms for voltage across the capacitor, voltage across the SCR and voltage across the load. (04)
- 1C. Sketch the safe operating area of power MOSFET clearly indicating all the operating limits. (02)
- 2A. With the help of a neat sketch of Triac's structure, explain its working in first quadrant when turned on with positive gate current. (03)
- 2B. A controlled half-wave rectifier has a series resistance, inductance and dc voltage source with $R = 2 \Omega$, $L = 75 \text{ mH}$ and $V_{dc} = 48 \text{ V}$. The source is 120 V at 60 Hz . The delay angle is 50° . Determine an expression for load current and average load current. (03)
- 2C. A three phase controlled bridge rectifier has a delay angle of 120° . The three phase ac system is 416 V (line-to-line). The load comprises of series combination of a dc source = 300 V , $R = 2 \Omega$ and L is large enough to consider the current to be purely dc. Determine the power transferred back to the ac system. Hence, plot the load voltage and load current waveforms. (04)
- 3A. Show that the power factor for the controlled full-wave rectifier with a resistive load is

$$pf = \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} \quad (03)$$

- 3B. A resistive load absorbs 200 W when connected to a 120 V rms at 60 Hz ac voltage source. Determine the firing angle of the voltage controller such that 200 W is absorbed by the same resistance when the source is 240 V rms at 60 Hz . (03)
- 3C. A boost converter has an input of 5 V and an output of 25 W at 15 V . The minimum inductor current must be no less than 50 percent of the average. The output voltage ripple must be less than 1 percent. The switching frequency is 300 kHz . Determine the duty ratio, inductor and capacitor values. (04)
- 4A. A single phase full converter is made to deliver a constant load current. For zero degree firing angle, the overlap angle is 15° . Calculate the overlap angle when firing angle is 30° . (03)

- 4B.** A step-up dc-dc converter has input voltage of 220 V and an output voltage of 660 V. If the conducting time of the switch is 100 μ s, compute the pulse width of the output voltage. If, now the output voltage pulse width is halved for constant frequency operation, find the average value of new output voltage. **(03)**
- 4C.** With a neat circuit schematic, explain the working of a single phase full bridge square wave inverter. Hence, plot the output voltage waveform in synchronization with the switching scheme. Also, draw the harmonic spectrum. **(04)**
- 5A.** With a neat circuit schematic, explain the working of a 3-level H-bridge inverter. Hence, plot the relevant waveforms. **(03)**
- 5B.** Discuss how unipolar switching technique can be applied to a single phase full bridge inverter. Support your answer with relevant waveforms. **(03)**
- 5C.** With the help of relevant waveforms explain how zero current switching can be attained for a buck dc-dc converter. **(04)**