



Reg.No.									
---------	--	--	--	--	--	--	--	--	--

INTERNATIONAL CENTRE FOR APPLIED SCIENCES
(Manipal University)

III SEMESTER B.S. DEGREE EXAMINATION – OCT. / NOV. 2017

SUBJECT: COMBINATIONAL AND SEQUENTIAL LOGIC (EC 231)

(BRANCH: CS/CE/MET/E&E/E&C)

Friday, 10 November 2017

Time: 3 Hours

Max. Marks: 100

- ✓ Answer ANY FIVE full Questions.
- ✓ Missing data, if any, may be suitably assumed

- 1A) Using Quine Mccluskey method, Obtain the minimal sum
 $F(A,B,C,D) = \sum m(0,1,5,7,8,10,14,15)$
- 1B) Expand $A+BC'+ABD'+ABCD$ to minterms. Simplify the expanded minterms using karnaugh map and draw the circuit for the simplified expression using NAND gates. Also determine the essential prime implicant.
- 1C) Write a dataflow VHDL code for 1:4 demultiplexer (10+5+5)
- 2A) Simplify the following Boolean expression algebraically
(i) $AB'C+B+BD'+ABD'+A'C$ (ii) $(A+B).(A+C')+A'B'+A'C'$
- 2B) Simplify the following function using 3 variable VEM technique
 $F(A,B,C,D)=\sum m(2,3,5,6,8,11,12,13)$
- 2C) (i) Add $679.6 + 536.8$ in BCD number system
(ii) Convert the following to the indicated bases $(3A9E.B0D)_{16} = (?)_2 = (?)_8$
(iii) Define the term sensitivity list in VHDL
(iv) Derive a logic expression that equals 1 only when the two bit binary numbers A_1A_0 and B_1B_0 have the same value. Draw the logic diagram and construct the truth table to verify the logic. (5+5+10)
- 3A) Design a combinational circuit to convert 8421 BCD to 2421 BCD using basic gates.
- 3B) Implement the following function using PLA $F_1=\sum m(0,2,4,6,7,8)$ $F_2=\sum m(10,12,13,15)$
- 3C) Implement the following multiple output combinational circuit using 4 to 16 decoder with active low outputs.
 $F1=\sum m(1,2,4,7,8,11,12,13)$ $F2=\sum m(2,3,9,11)$ $F3=\sum m(10,12,13,14)$ $F4=\sum m(2,4,8)$
- 3D) Write a behavioral VHDL code for 8:1 multiplexer (5+5+5+5)
- 4A) Implement the following function $F(A,B,C) = AB+B'C$ using (i) 4:1 multiplexer and basic gates (ii) 2:1 multiplexer and basic gates.
- 4B) Design a circuit for 4 to 2 priority encoder using basic gates
- 4C) Explain the operation of a master slave SR flipflop with a neat circuit diagram
- 4D) Design a mod 10 ripple up counter using T flipflop (5+5+5+5)
- 5A) Design a synchronous J-K counter that goes through states 3,4,6,7 and 3,...Is the counter self starting. Modify the circuit such that whenever it goes to an invalid state it comes back to state 3
- 5B) Derive the characteristic equation of JK flipflop and convert JK to SR flipflop
- 5C) Draw the logic diagram of JK flipflop using NAND gates. Derive the truth table for the same and explain its operation (10+5+5)

- 6A) Design a Mealy type Sequence detector to detect an overlapping sequence “1010”
 6B) Explain the operation of 4 bit Ring counter with a neat circuit diagram and suitable timing waveforms
 6C) Write the behavioral VHDL code for JK flip flop using if statement **(10+5+5)**
- 7A) Design a 3 bit synchronous up / down counter using JK flipflops
 7B) With a neat circuit diagram, Explain the operation of 4 bit Universal Shift Register

S ₁	S ₀	Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

(10+10)

- 8A) Write the behavioral VHDL code for 4 bit binary parallel adder / subtractor
 8B) Reduce the following state table and draw reduced state diagram

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
A	E	D	0	1
B	F	D	0	0
C	E	D	0	1
D	F	D	0	0
E	C	F	0	1
F	B	C	0	0

- 8C) Define the following and give one example for each
- Weighted codes
 - Self complementing codes
 - Gray codes

(10+4+6)

