



Reg. No.									
----------	--	--	--	--	--	--	--	--	--

INTERNATIONAL CENTRE FOR APPLIED SCIENCES
(Manipal University)

III SEMESTER B.S. DEGREE EXAMINATION – NOV. / DEC. 2017

SUBJECT: DC AND AC CIRCUIT ANALYSIS (EE 232)

(BRANCH: MECHANICAL, MECHATRONICS)

Wednesday, 8 November 2017

Time: 3 Hours

Max. Marks: 100

- ✓ Answer ANY FIVE full Questions.
- ✓ Missing data, if any, may be suitably assumed

- 1A.** A 3 Phase, 220 V, 50 Hz, 11.2 kW induction motor has a full load efficiency of 88% and draws a line current of 38 A under full load. Find the power factor of the motor and the wattmeter readings to measure power input. (10)
- 1B.** Find the current supplied by the battery in the network (Fig 1B). (Use star-delta transformation)

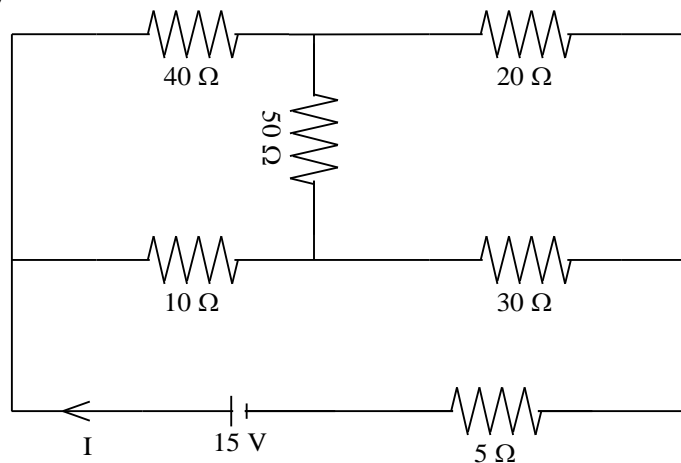


Fig 1B.

(10)

- 2A.** Find the power dissipated in the 6 Ω resistor (Fig 2A).

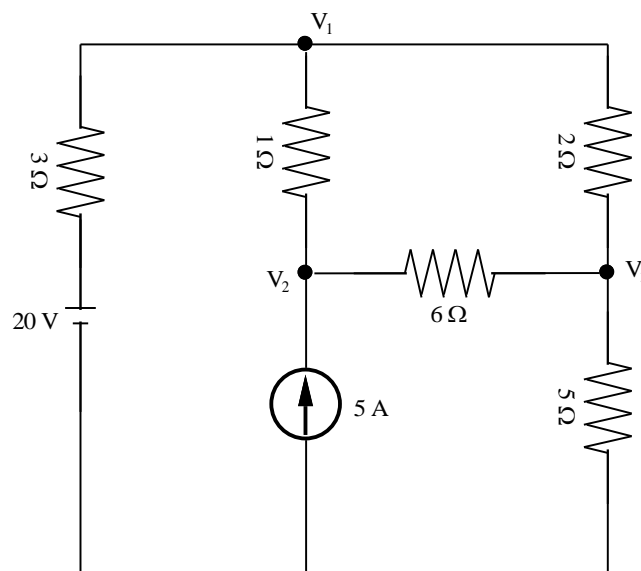


Fig 2A

(12)

- 2B.** Find the value of R such that the circuit is in resonance (Fig 2B)

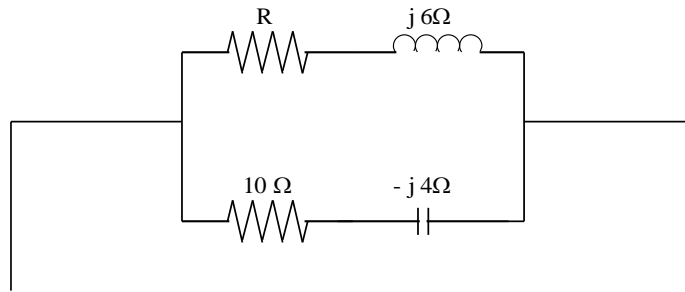


Fig 2B

(08)

- 3A.** Find the value of C in the circuit for resonance.

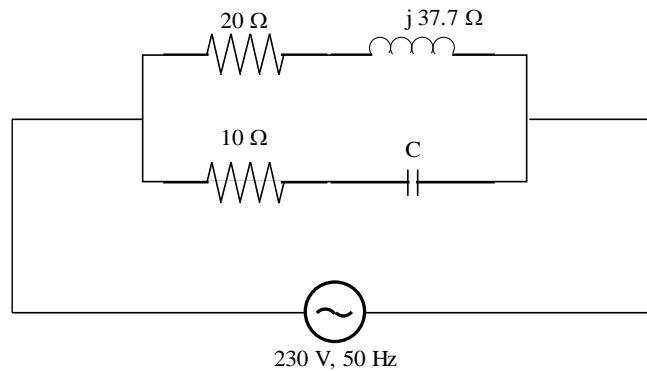


Fig 3A

(12)

- 3B.** A series RLC series circuit has a resistance of 10Ω , inductance of 0.2 H and a capacitance of $40 \mu\text{F}$. It is supplied with 100 V supply. Find

- Resonant frequency
- Half-Power frequencies
- Current at resonance
- Quality factor

(08)

- 4A.** Inductor loads of 0.8 kW and 1.2 kW at lagging power factors of 0.8 and 0.6 respectively are connected across a 200 V , 50 Hz supply. Find the total current, power factor and the value of the capacitor to be put in parallel to make the overall power factor 0.94 lag.

(10)

- 4B.** Use Norton's theorem to find current through Z_L (Fig 4B)

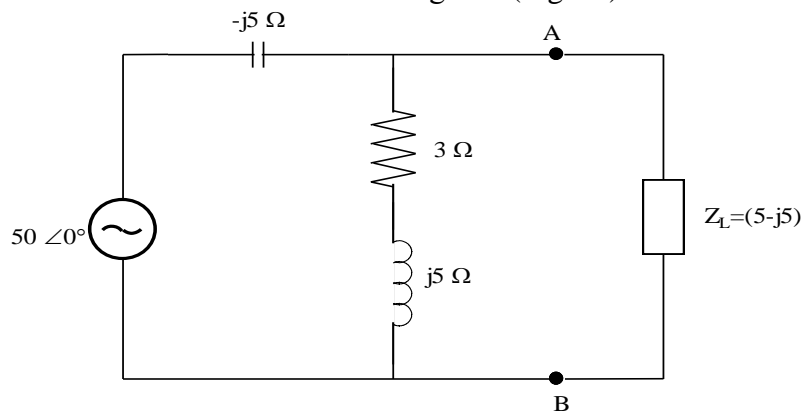


Fig 4B

(10)

- 5A** A Generator of voltage $400 \text{ V } \angle 0^\circ$ is connected to a motor of voltage $E_b \angle \Phi \text{ V}$, through a line impedance $(1 + j4) \Omega$.
Find the supply current, power input & power output of motor for the following cases.
- $E_b = 400 \angle -20^\circ \text{ V}$
 - $E_b = 350 \angle -20^\circ \text{ V}$
 - $E_b = 450 \angle -20^\circ \text{ V}$
- (12)**
- 5B** With a neat connection diagram & phasor diagram prove that two wattmeters are sufficient to measure three phase power. Explain how the wattmeter readings are affected by the load power factor. **(08)**
- 6A** Find the Thevenin equivalent for the network shown in Fig 6A

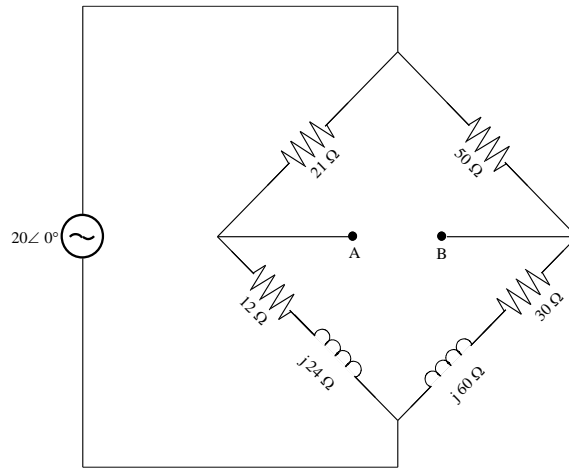


Fig 6A

(10)

- 6B.** Find the equivalent impedance and the power factor of the circuit given in Fig 6B

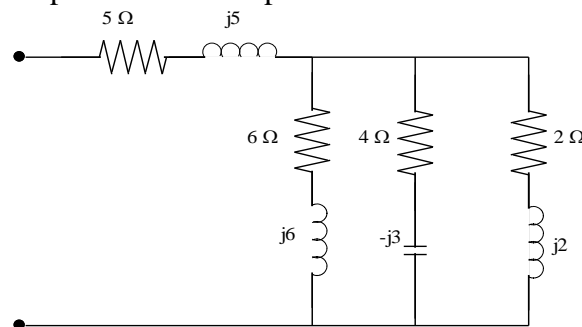


Fig 6B

(10)

- 7A.** An industry has the following loads
- A 3 phase circuit γ connected operating at 400 V drawing a line current of 20 A at 0.8 pf lag
 - A 3 phase circuit Δ connected with a phase current of 15 A at 400 V and power factor 0.707 lag.
 - A 10 kW motor with efficiency 0.8 and pf 0.8 operating at 400 V

Find the total load kVA and resultant power factor.

(10)

- 7B.** Find the value of Z_L so that maximum power can be transferred to it (Fig 7B). Find the maximum power.

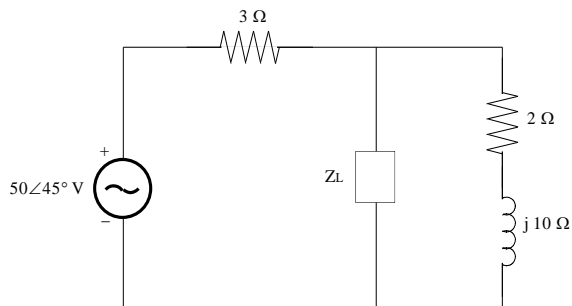


Fig 7B

(10)

- 8A.** Find the power output of the current source shown in Fig 8A

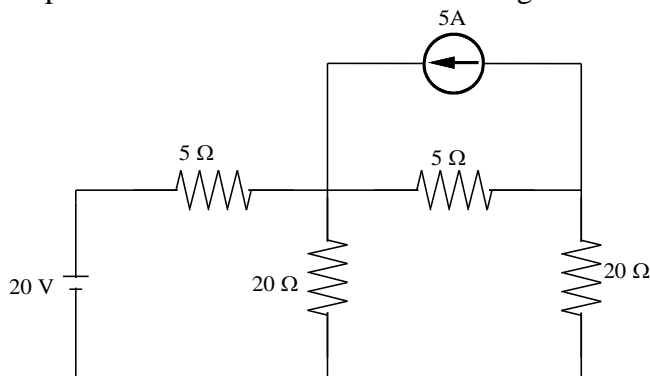


Fig 8A

(10)

- 8B.** Find the source voltage, source current and power input (Fig 8B).

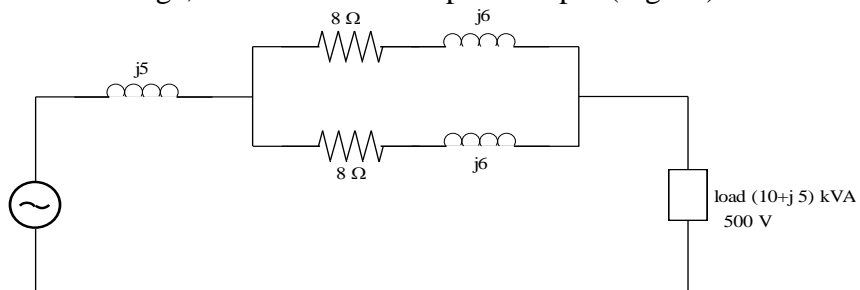


Fig 8B

(10)

