



INTERNATIONAL CENTRE FOR APPLIED SCIENCES
(Manipal University)
III SEMESTER B.S. DEGREE EXAMINATION – OCT. / NOV. 2017
SUBJECT: ELECTRONIC DEVICES AND CIRCUITS (EC 232)
(BRANCH: EC and EE)
Monday, 6 November 2017

Time: 3 Hours

Max.Marks: 100

- ✓ Answer ANY FIVE full Questions.
- ✓ Missing data, if any, may be suitably assumed

- 1A. Design a Zener diode shunt regulated power supply with following specifications
a) O/p voltage is 10V. b) Load current is 50mA c) Maximum power dissipation of 500mw and d) Input voltage is $15 \pm 2V$
- 1B. Draw the circuit of negative and positive clamper and explain its operation with the input and output waveform. (10+10)
- 2A. For a full wave rectifier using center tapped transformer, derive a) Ripple factor b) The average value of load current c) The rms value of load current d) Efficiency of the rectifier.
- 2B. Explain with a neat circuit diagram and waveforms, how transistor can be used as switch .
- 2C. In a transistor, 99% of the carriers injected into the base cross over to the collector region. If collector current is 4mA and collector leakage current is $6 \mu A$, calculate emitter and base currents. (10+6+4)
- 3A.What is the drawback of fixed bias? How do you overcome it? Explain with neat circuit diagram the modified biasing circuit.
- 3B. Explain with neat circuit diagram RC-coupled amplifier. Discuss the use of all the components in the circuit and why they are used. Also draw the frequency response of the amplifier. (10+10)
- 4A. Explain the construction, working and characteristics of enhancement P- MOSFET.
- 4B. What is Barkhausen criteria? Write the circuit of Hartley oscillator and explain its working. (10+10)
- 5A. Derive an expression for efficiency of Class B power Amplifier.
- 5B. Compare class A, B, C and D amplifier (10+10)
- 6A. Determine V_O for the network shown in Fig Q6A for the input indicated. Show the steps involved.

- 6B. For the circuit shown in Fig Q6B, determine I_{BQ} , I_{CQ} , V_{CEQ} , V_C , V_E , V_B . Draw the load line. (10+10)
- 7A. Explain how CMOS can be used as a NOT gate. What are the advantages of the CMOS?
- 7B. Sketch the transfer characteristic of a P-channel JFET device with $I_{dss}=4\text{ mA}$ and $V_p=3\text{V}$
- 7C. Compare FET and BJT. (10+6+4)
- 8A. Explain the operation of PN junction diode along with diode current equation and V-I characteristics under different bias conditions.
- 8B. Draw the circuit of Emitter follower. What are the advantages of emitter follower? (10+10)

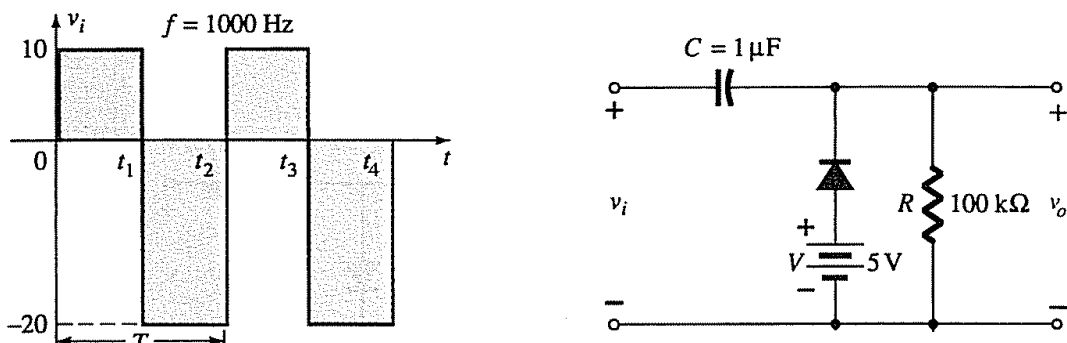


Fig Q6A.

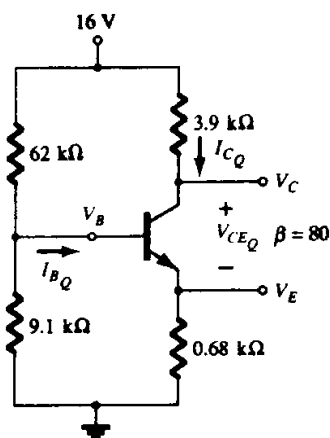


Fig.Q.6B

