



Reg. No.									
----------	--	--	--	--	--	--	--	--	--

INTERNATIONAL CENTRE FOR APPLIED SCIENCES

(Manipal University)

III SEMESTER B.S. DEGREE EXAMINATION – NOV. 2017

SUBJECT: LINEAR NETWORK TRANSIENT ANALYSIS (EE 231)

(BRANCH: E & E, E & C, CE, BM)

Wednesday, 8 November 2017

Time: 3 Hours


Max. Marks: 100

- ✓ Answer ANY FIVE full Questions.
- ✓ Missing data, if any, may be suitably assumed

1A. Find the even and odd part of the signal.

i) $x(t) = (1 + t + 3t^2 + 5t^3 + 9t^4)$

ii)

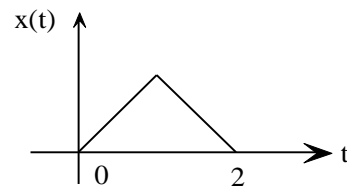

(06)

1B. A series RLC circuit is excited by a DC voltage of E volts by closing the switch, determine the voltage across the capacitor for the following cases with $L = 1H$; $C = \frac{1}{4}F$ and

i) $R = 2\Omega$ ii) $R = 3\Omega$ iii) $R = 5\Omega$

Comment on results.

(14)

2A. Find the function $V(t)$ using the pole-zero plot of following function.

$$V(s) = \frac{(s+2)(s+6)}{(s+1)(s+5)}$$

(06)

2B. Using convolution theorem evaluate the inverse laplace transform of the following.

i) $\frac{1}{s(s+a)}$

ii) $\frac{1}{s(s+a)^2}$

(08)

2C. Find the even and odd part of the discrete time signal $x(n)$ shown in Fig 2C.

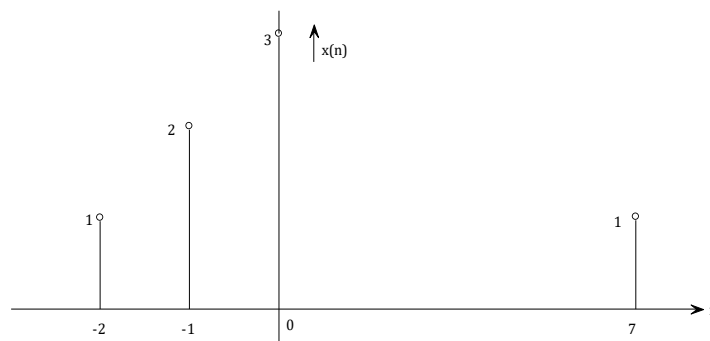


Fig 2C.


(06)

3A. Find the laplace transform of the following functions.

i) $x(t) = t \cos at$ ii) $\frac{(1 - e^{-t})}{t}$

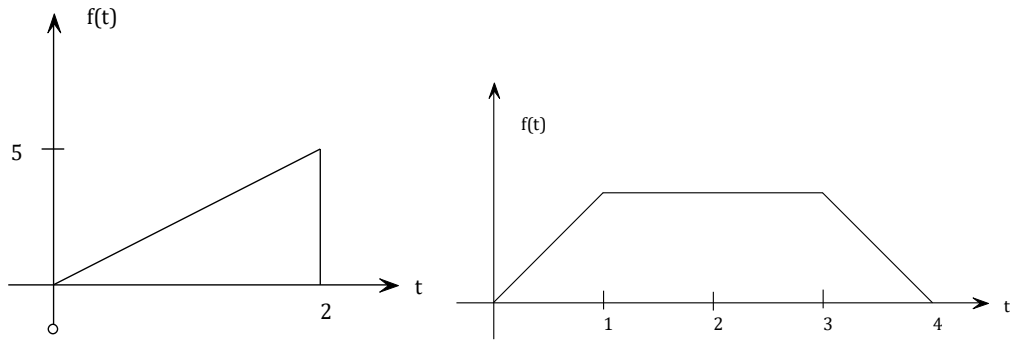(08)

3B. Find the laplace transform of the following non-periodic functions.



(12)

4A. Find the laplace transform of the periodic waveform shown in Fig 4A.

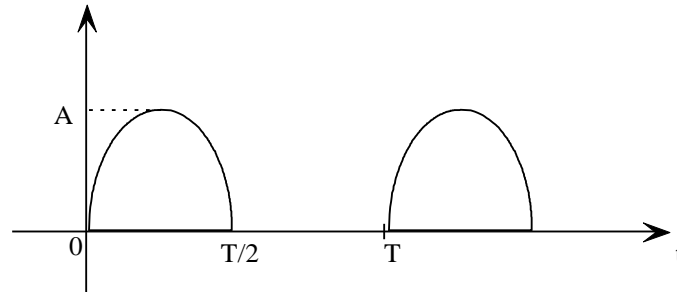


Fig 4A.

(10)

4B. Find the initial and final values of the function whose laplace transform is

i) $F(s) = \frac{(2S+1)}{(s^3+6S^2+11S+6)}$

ii) $F(s) = \frac{(s+6)}{S(S+3)}$

(10)

5A Find the network functions $\frac{V_1}{I_1}$, $\frac{V_2}{I_1}$ for the network shown in Fig 5A.

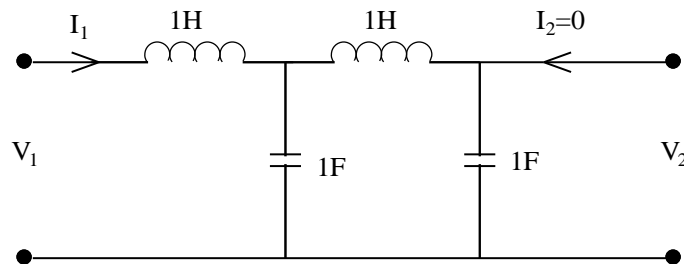


Fig 5A

(10)

5B Determine the source current when the switch is closed at $t=0$. (Fig 5B) Assume zero initial conditions.

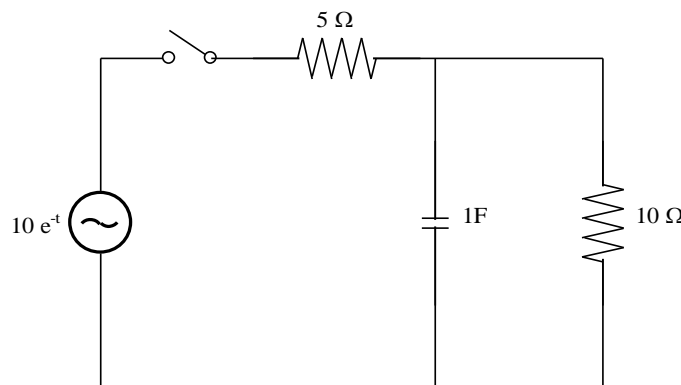


Fig 5B.

(10)

- 6A** The network shown in fig 6A is in steady state with S1 closed and s2 open. At $t=0$, S1 is opened & S2 is closed. Find the current through the capacitor.

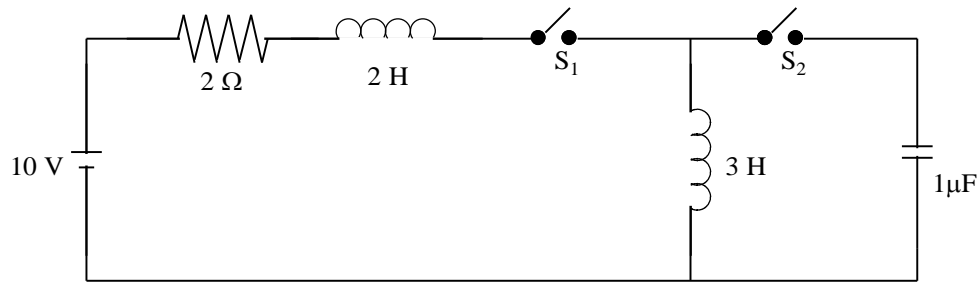


Fig 6A

(10)

- 6B.** $V=50 \sin 10 t$ is applied to a series R-C circuit with $R=2 \Omega$ and $C=0.25 \text{ F}$. Find the equation for current. Assume zero initial conditions

(10)

- 7A.** Find the complete response for $t > 0$ for an RLC circuit with $R=6 \Omega$, $L= 1 \text{ H}$ and $C= \frac{1}{9} \text{ F}$ with initial capacitor voltage = 2V .

The circuit is excited with $V(t)= 2 \cos 4t$.

(12)

- 7B.** Find the laplace transform of the periodic saw-tooth waveform as shown in fig 7B.

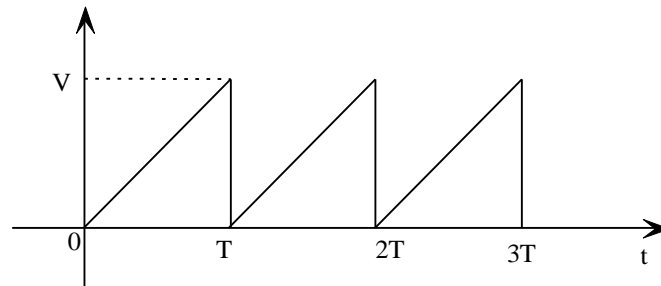


Fig 7B.

(08)

- 8A.** In the network shown in fig 8A find the currents $i_1(t)$ & $i_2(t)$ for $t>0$

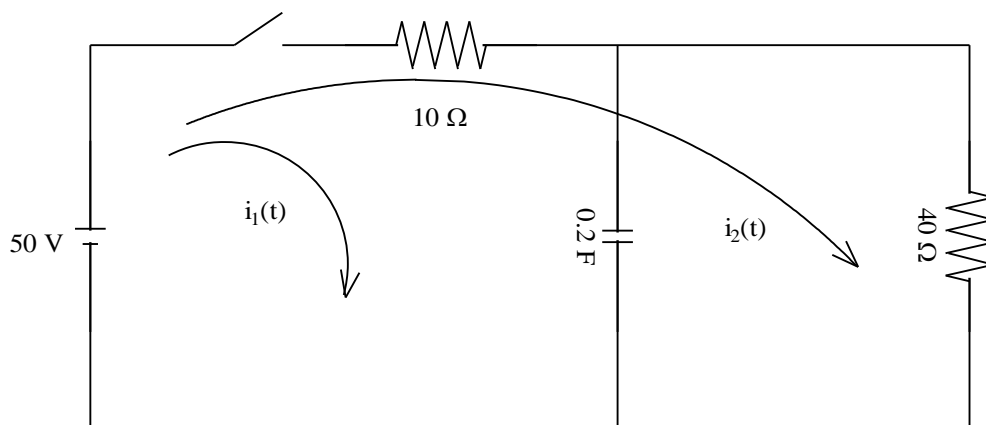


Fig 8A

(10)

- 8B.** IN the network shown in Fig 8B the switch is opened at $t=0$, the steady state having been established previously. Find $i(t)$ for $t > 0$

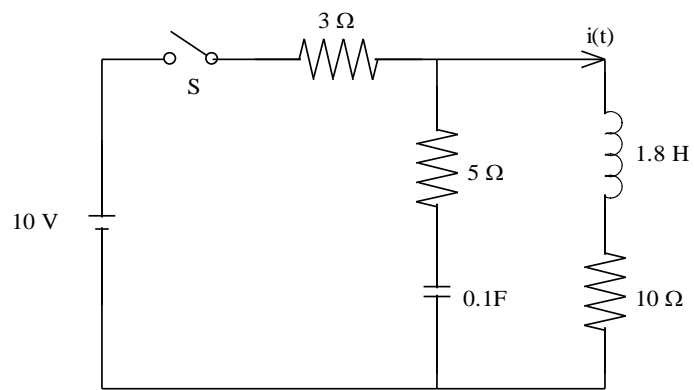


Fig 8B

(10)

