

INTERNATIONAL CENTRE FOR APPLIED SCIENCES

(Manipal University)

FOURTH SEMESTER B.S. DEGREE EXAMINATION - OCT. / NOV. 2017

SUBJECT: IC SYSTEMS (EC 243)

(BRANCH: E&C and E&E) Friday, 03 November 2017

Time: 3 Hours

Max. Marks: 100

- ✓ Answer ANY FIVE full Questions.
- ✓ Missing data, if any, may be suitably assumed
- 1A) Draw the circuit of an emitter coupled differential amplifier. Derive an expression for CMRR. Explain how CMRR can be improved by using current mirror circuit. Find the difference between $V_2 \& V_1$ assuming identical transistors with large β value for the circuit shown in Fig. Q1A.



Fig. Q1A

- 1B) Write short note on the classification of feedback.
- 1C) Draw the circuit diagram of RC phase shift oscillator and explain its operation.

(10+6+4)

2A) Analyze and determine the expression of the output voltage for the circuit shown in Fig. Q2A(i) & Q2A(ii).



2B) Draw a non-inverting amplifier using OP-AMP. Derive the expression for the voltage gain assuming ideal conditions. Design the circuit to obtain voltage gain of 20. Draw the output waveform for the input signal (i) $V_i = 0.5\sin(3140 t)$ (ii) $V_i = 3\sin(3140 t)$ Use supply voltage ± 12 V. (10+10)

- 3A) Draw the circuit diagram of 4-bit binary weighted resistor DAC and explain its operation. Convert the following input into equivalent analog output. i) 1111 ii) 0011. With $R=10k\Omega$, $R_F = 1k\Omega$. Draw the output waveform for decimal equivalent of binary input. What are the drawbacks of this DAC?
- 3B) Draw the circuit diagram of Log and Anti-Log amplifiers using OP-AMP. Derive the output voltage expressions. (10+10)
- 4A) i) Explain the working of mono-stable multivibrator using OP-AMP with the help of neat circuit diagram and waveforms. Derive the expression for monoshot time. ii)Design a square wave oscillator using OP-AMP for $f_o = 1 \text{ kH}_z$. Assume $R_1 = 1.16R_2$ and $C = 0.05 \mu$ F.
- 4B) Design a circuit using IC 555 timer to obtain a square wave of frequency 1 kHz for duty cycle of (i) 25% (ii) 50% (iii) 75%. Derive the equations used. Assume $C = 0.1 \mu F$.

(10+10)

- 5A) Draw the functional diagram of OP-AMP and explain each block.
- 5B) Define the following terms with respect to OP-AMP:
 - a) Slew Rate
 - b) Output offset voltage
 - c) Common mode gain
 - d) Output resistance
- 5C) Draw the circuit of an 8-bit successive approximation type ADC. Explain the conversion process with an example. List the names of other ADCs.

(5+5+10)

- 6A) Draw the circuit of second order Butterworth active High pass filter and derive the expression for $A_V(s)$.
- 6B) Explain the functional blocks of PLL. How it is used as frequency multiplier?

(10+10)

7A) Design a second order Butterworth low pass filter having cut off frequency of 1 kHz. Draw to scale its frequency response graph (gain (d_B) vs frequency) if $A_V = \frac{A_{VO}}{\sqrt{\left(1+\frac{f}{f_c}\right)^4}}$.

Assume capacitor is 0.01 µF.

- 7B) Mention any two important criteria for a good instrumentation amplifier. Draw the circuit diagram of instrumentation amplifier and derive the expression for V_O.
- With neat circuit diagram, discuss the method to use three terminal fixed voltage regulator as a current source. Show that it is possible to boost the output current of a three terminal regulator. Derive the necessary expressions. (5+5+10)

8)	Write short note on the following:		
	A. Series and Switching regulator	C. Inverting Schmitt trigger	
	B. Fixed Voltage Regulator	D. Analog Divider	(5×4)

##