

Reg. No.



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

A Constituent Institution of Manipal University

III SEMESTER B.Tech.(BME) DEGREE END SEM EXAMINATIONS NOVEMBER 2017
SUBJECT: DIGITAL ELECTRONICS (BME 2103)
(REVISED CREDIT SYSTEM)
Thursday, 23rd November 2017: 9AM to 12 NOON
TIME: 3 HOURS
MAX. MARKS: 100
Instructions to Candidates:

- 1. Answer all FIVE full questions. 2. Draw labeled diagram wherever necessary.**

1. (A) A switching circuit has two control inputs (C_1 & C_2), two data-inputs (X_1 & X_2), and one output (Z). The circuit performs logic operations on the two data-inputs, as shown in the table. The logic operations performed depends on the control inputs. 06

C_1	C_2	Logic operation performed by the circuit
0	0	OR
0	1	XOR
1	0	AND
1	1	MAGNITUDE COMPARISON

- (a) Derive the truth table for the output Z . (b) Use a K-Map to find the minimum gate-circuit to realize Z .

- (B) What is a digital comparator? Design the following digital comparators: 08

(a) 1-bit comparator using logic gates.

(b) 5-bit comparator using a 4-bit comparator (IC 7485) and suitable gates.

- (C) Design an 8-bit binary parallel adder/subtractor with a control input to select between addition and subtraction. 06

2. (A) What is a full adder? Design a full adder circuit using each of the following: 08

(a) 8:1 Multiplexers, and (b) 4:1 Multiplexers


- (B) Obtain the minimum sum of products (SOP) expression using Karnaugh map for each of the following Boolean functions. 06

(a) $f(A, B, C, D) = \sum m(0, 2, 4, 5, 6, 7, 8, 10)$

(b) $f(A, B, C, D) = \sum m(1, 8, 12, 13) + \sum d(3, 7, 10, 11, 14, 15)$ $d \rightarrow$ don't cares

- (C) Design an Excess-3 to BCD code converter using 4 to 16 line decoder and additional gates. 06

 3. (A) Calculate the output of the following logic circuit using Boolean algebra techniques. 04



- (B) What is the difference between common anode and common cathode type of 7-segment displays? Design a decoder/driver circuit for the common cathode type of 7-segment display, to display the decimal numbers from 0 to 7. 08
- (C) Explain the function table associated with a 4-bit universal bidirectional shift register – IC 74194. Construct a 4-bit Ring counter using IC 74194 and suitable gates. 08
4. (A) Construct the state diagram for a Mealy sequential circuit that will detect a sequence “1100” from an input sequence. 04
- (B) (i) Design a 4-bit ripple counter using JK Flip-flops. Illustrate its working using the timing diagram. 08
- (ii) A 4-bit ripple counter uses Flip-flops with a propagation-delay of 25ns each. What will be the maximum time required for change of state?
- (iii) The output frequency of a Mod-12 counter is 6kHz. What is its input frequency?
- (C) (i) Perform the addition of the following BCD numbers: 08
- (a) 0110 0111 and 0101 0011, (b) 0100 0100 1000 and 0100 1000 1001
- (ii) A computer system uses a 20-bit address code to identify each of over 1 million binary locations. How many hex-characters are required to identify the address of each memory location? What is the hex-address of the 200th memory location?
- (iii) Digital thermometers use BCD to drive their digital displays. How many BCD bits are required to drive a 2-digit thermometer display? What are the BCD bits sent to the display, to display the temperature 97°C?
- (iv) What range of decimal values can be represented by a 4-digit hex number?
5. (A) What is the advantage of a synchronous counter over a ripple counter? Design a 3-bit Gray-code synchronous counter using JK Flip-flops. 06
- (B) Using a suitable IC (and gates), design a circuit to subtract 1001 from 1101, using the following methods: (a) 1’s complement subtraction, and (b) 2’s complement subtraction 06
- (C) Design a Moore sequential circuit using D flip-flops, which detects an overlapping sequence 101 from an input sequence. 08