Reg. No.



$^{55}p_{tR_{\rm ED}} \propto V^{5}$ A Constituent Institution of Manipal University

III SEMESTER B.Tech. (BME) DEGREE END SEM EXAMINATIONS NOVEMBER 2017

SUBJECT: NETWORK ANALYSIS (BME 2101)

(REVISED CREDIT SYSTEM)

Tuesday, 21st November, 2017, 9 AM to 12 NOON

TIME: 3 HOURS

MAX. MARKS: 100

Instructions to Candidates:

1. Answer ALL questions.

2. Draw labeled diagram wherever necessary. Any missing data may be suitably assumed.

1a) In the circuit shown in Fig. Q1a, calculate the power dissipated in each of the resistor. (8) Use loop analysis to solve for the values of the current in each of the branch.



1b) For the circuit shown in **Fig. Q1b**, find the current I through the $(3-j4)\Omega$ impedance. (6) Then apply and verify the Reciprocity theorem for this circuit.



1c) For a series RLC resonant circuit, V=50 Volts, L=20mH, C=250 μ F and R=10 Ω . (6) Determine the resonant frequency, voltage drop across each of the components and the circuit current at resonance. Also find the half power frequencies of the circuit.

2a) For the circuit shown in Fig. Q2a, apply Thevinin's theorem to find the current in the (8) 5 Ω resister. Also find the power dissipated in this resistor.





2b) For the network shown in **Fig.Q2b**, the impedance Z_L is variable in terms of both resistance and reactance. Find the value of Z_L to get the maximum power in the load. What is the maximum power? (6)



2c) For the coupled circuit shown in **Fig.Q2c**, find the values of I_1 , I_2 and V_0



3a) For the network shown in **Fig.Q3a**, obtain the star equivalent circuit.



(6)

(6)

3b) In the network shown in **Fig.Q3b**, a steady state is reached with the switch K open for (8) t<0. At t=0, the switch K is closed. Find the values of,





3c) Find the inverse Laplace Transform of

(i)
$$F_1(s) = \frac{2s}{(s^2 + 4)(s + 5)}$$
 (ii) $F_2(s) = \frac{5s}{s^2 + 3s + 2}$ (ii) $F_3(s) = \frac{s + 5}{s^2 + 4}$

4a) For the circuit shown in **Fig.Q4a**, the switch K is closed at t=0 with the network (8) previously un-energized. For the element values given, find the values of currents $i_1(t)$ and $i_2(t)$.



Fig.Q4a

4b) For the waveform shown in the **Fig.Q4b**, write an equation for v(t) in terms of steps, (6) ramps and related waveforms as needed. Also obtain the expression of its Laplace transform V(s).



(6)

4c) Determine the Laplace transform for the periodic waveform shown in **Fig.Q4c**.



- 5a) Show that, the overall transmission parameter matrix for cascaded two port network is the matrix product of the transmission matrices associated with each of the two port networks in cascade.
- **5b**) Obtain the conversion of h-parameters in terms of transmission parameters. (6)
- 5c) For the network shown in **Fig. Q5c**, find the expressions of,



(6)

(8)