



III SEMESTER B.TECH. (COMPUTER AND COMMUNICATION ENGINEERING) MAKEUP EXAMINATIONS, DECEMBER 2017

SUBJECT: DIGITAL SYSTEM DESIGN [ICT 2151]

REVISED CREDIT SYSTEM (22/12/2017)

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer ALL the questions.
- ❖ Missing data, if any, may be suitably assumed.

- | | |
|---|---|
| 1A. Design a hardwired control unit for 4x4 Booth's multiplier. | 5 |
| 1B. Design a 1-bit magnitude comparator with cascading inputs. Using this, design a 2-bit magnitude comparator. | 3 |
| 1C. Design a T flip flop from SR flip flop. | 2 |
| 2A. Design a synchronous sequential circuit, with one input A and one output Y. The output Y is to be HIGH whenever the sequence "10011" is detected. Otherwise the output is LOW. Overlapping of the sequence is allowed. Implement using T flip flops and external gates. | 5 |
| 2B. Given $M = 17_{(10)}$ and $Q = -5_{(10)}$. Multiply using Booth's algorithm. | 3 |
| 2C. Design a 4:2 priority encoder. | 2 |
| 3A. Design a combinational circuit to evaluate the arithmetic expression $D = X^2 - Y^2$ using 7483 IC and external gates, where X and Y are 2-bit binary numbers | 5 |
| 3B. With necessary diagrams, explain various cache mapping techniques. | 3 |
| 3C. Using 7490 ICs ONLY, design a logic circuit which divides the frequency of the input square wave by a factor of '100' and produces an output waveform with 50 percent duty cycle. | 2 |
| 4A. Design a code converter to convert a decimal digit represented in 2 4 2 1 to decimal digit represented in 8 4 2 1 code, using NOR gates only. | 5 |
| 4B. What is a race around condition? How is it overcome using master-slave configuration? Give necessary circuit diagrams and waveforms. | 3 |
| 4C. Design 5: 32 decoder using 3 to 8 decoders only. | 2 |

5A. Design a self-starting synchronous counter using T flip flops and external gates to count the sequence $1 \rightarrow 2 \rightarrow 4 \rightarrow 9 \rightarrow 12 \rightarrow 5 \rightarrow 1$	5
5B. Design a 3-bit carry look ahead adder.	3
5C. Differentiate between restoring and non restoring division algorithms.	2
