



THIRD SEMESTER B.Tech. (E & C) DEGREE END SEMESTER EXAMINATION NOV 2017

SUBJECT: ANALOG ELECTRONIC CIRCUITS (ECE - 2101)

TIME: 3 HOURS

MAX. MARKS: 50

Instructions to candidates

- Answer **ALL** questions.
- Missing data may be suitably assumed.

- 1A. A CE stage exhibits a voltage gain of 20 and an output resistance of 1 k Ω . Determine the voltage gain of the CE amplifier if (a) The stage drives an 8 Ω speaker directly. (b) An emitter follower biased at a current of 5 mA is interposed between the CE stage and the speaker. Assume $\beta = 100$, $V_A = \infty$, and the follower is biased with an ideal current source.
- 1B. Determine input/output impedances for the circuit shown in Fig.Q1B. Assume $V_A = \infty$.
- 1C. A transistor is biased at a collector current of 1 mA. Determine small-signal model if $\beta = 100$ and $V_A = 15$ V.

(5+3+2)

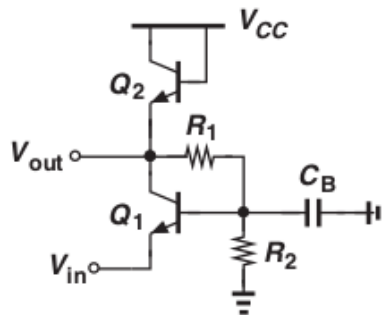


Fig Q1(B).

- 2A. Determine i) Input resistance ii) Output resistance iii) Voltage gain for the circuit shown in Fig.Q2A. Assume $I_D = 1\text{mA}$, $V_{DD} = 1.8\text{V}$, $V_{TH} = 0.4\text{V}$, $\mu_n C_{OX} = 100\mu\text{A/V}^2$, $W/L = 20$, $\lambda = 0$.
- 2B. Determine I_D and V_{DS} for the circuit shown in Fig.Q2B. Assume $V_{DD} = 1.8\text{V}$, $V_{TH} = 0.4\text{V}$, $\mu_n C_{OX} = 100\mu\text{A/V}^2$, $W/L = 20$, $\lambda = 0$.
- 2C. Draw the small signal equivalent circuit for the circuit shown in Fig.Q2C. Consider Early effect.

(5+3+2)

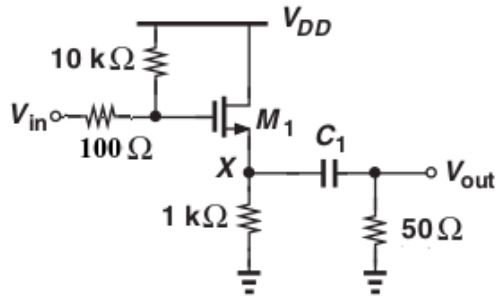


Fig Q2(A)

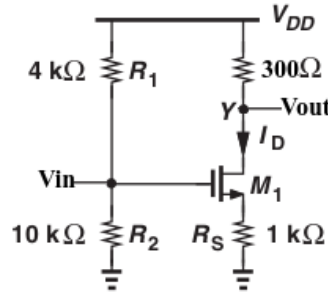


Fig Q2(B)

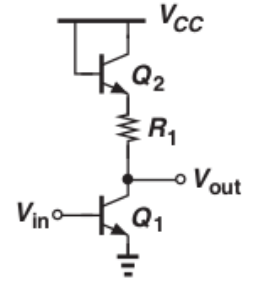


Fig Q2(C).

- 3A. Design an amplifier using MOSFET with a power budget of 2mW and input impedance of 30kΩ which provides a voltage gain of 7. Assume voltage drop across R_S as 0.3V, $V_{DD}=1.8V$, $V_{TH}=0.4V$, $\mu_n C_{OX}=100\mu A/V^2$, $\lambda=0$.
- 3B. The circuit of Fig. Q3B must be designed for a voltage drop of 200 mV across R_S . (a) Calculate the minimum allowable value of W/L if M_1 must remain in saturation. (b) What are the required values of R_1 and R_2 if the input impedance must be at least 30 kΩ?
- 3C. A MOSFET carries a drain current of 1 mA with $V_{DS}=0.5V$ in saturation. Determine the change in I_D if V_{DS} rises to 1V and $\lambda=0.1V^{-1}$. What is the device output impedance?

(5+3+2)

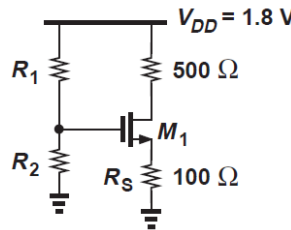


Fig Q3(B).

- 4A. In the network of Fig. Q4(A1),
 - (i) With $R_1 = R_2 = R$ and $C_1 = C_2 = C$, obtain an expression for the transfer function.
 - (ii) Determine the frequency at which the phase falls to zero.
 - (iii) If this network is placed around an op amp as in Fig. Q4(A2) and by denoting the gain of the non-inverting amplifier by 'A', determine the minimum value of gain 'A' for sustained oscillation.
 - (iv) For sustained oscillation, what should be the relationship between R_{F1} and R_{F2} ?
 - (v) Incorporating diodes, redraw the circuit to avoid uncontrolled amplitude growth.
- 4B. Consider an open-loop amplifier with a transfer function $A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$. The system is converted into a closed loop system with a feedback factor 'K'. Prove that the unity-gain bandwidth of the closed system remains independent of K if $1 + KA_0 \gg 1$ and $K^2 \ll 1$.
- 4C. In the amplifier of Fig. Q4(C), $R_D = 1k\Omega$ and $C_L = 1pF$. With $\lambda=0$ and junction capacitors neglected, Plot the frequency response, and determine the frequency at which the voltage gain falls by 3dB.

(5+3+2)

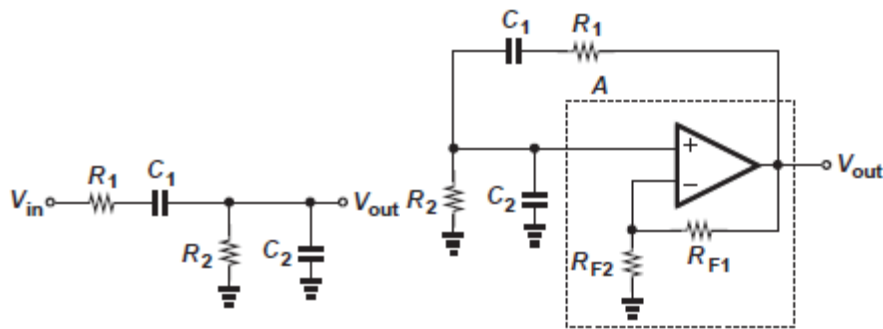


Fig. Q4(A1)

Fig. Q4(A2)

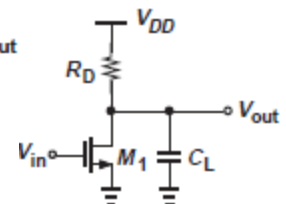


Fig. Q4(C)

- 5A. For the block diagram shown in Fig. Q5(A1),
- Identify the type of the feedback amplifier
 - Derive an expression for the closed loop gain I_{out}/I_{in}
 - Derive an expression for the input impedance
 - Derive an expression for the output impedance
 - Is the type of feedback amplifier in Fig. 5(A2) is same as that of Fig. Q5(A1)?
- 5B. In the emitter follower stage shown in Fig. Q5(B), assume $\lambda = 0$, voltage gain = 0.7 and $R_L = 4\Omega$.
- At what load current Q_1 turns off?
 - For a sinusoidal input, estimate the largest average power that can be delivered to the load without turning Q_1 off.
- 5C. (i) In a simple push-pull stage, the zone, at which neither transistor conducts and the small-signal gain falls to zero is known as ____.
- (ii) ____ amplifier has highest power conversion efficiency.
- (iii) Transformer coupled amplifier has a peak power efficiency of ____.
- (iv) An amplifier in which the device is ON for the entire cycle is called an ____ amplifier.

(5+3+2)

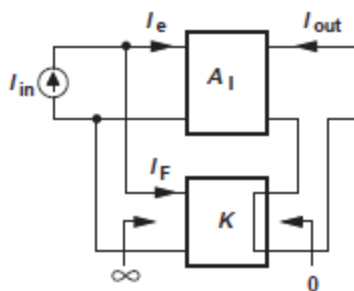


Fig. Q5(A1)

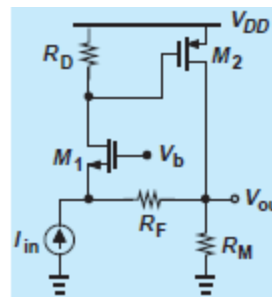


Fig. Q5(A2)

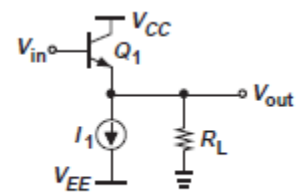


Fig. Q5(B)