

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



# MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

A Constituent Institution of Manipal University

## THIRD SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.) END SEMESTER EXAMINATIONS, NOV- 2017

SUBJECT: ELECTRICAL CIRCUIT ANALYSIS [ICE 2101]

Time: 3 Hours

MAX. MARKS: 50

### Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitable assumed.

- |            |  |          |
|------------|--|----------|
| <b>1A.</b> | Find the mesh currents in the circuit shown in Fig.Q1A.  | <b>5</b> |
| <b>1B.</b> | Obtain node voltages $V_1$ and $V_2$ for the circuit shown in Fig.Q1B  | <b>3</b> |
| <b>1C.</b> | Determine $V$ in the circuit shown in Fig.Q1C.   | <b>2</b> |
| <b>2A.</b> | Using Nortons's theorem determine current in $3\Omega$ resistor of Fig.Q2A.  | <b>5</b> |
| <b>2B.</b> | Obtain Thevinin's equivalent for the circuit shown in Fig.Q2B with respect to AB.  | <b>3</b> |
| <b>2C.</b> | Using superposition theorem determine the current in $R_L$ .   | <b>2</b> |
| <b>3A.</b> | In the network shown Fig. Q3A, the switch is opened at $t=0$ , a steady state having previously been attained. Obtain expression for current in complementary and particular solution form.                      | <b>5</b> |
| <b>3B.</b> | An impedance of $(10-j5) \Omega$ is connected in parallel with a coil with inductive reactance $j10\Omega$ and variable coil resistance of $R_L$ . Find the value of $R_L$ for which the circuit is in resonant. | <b>3</b> |
| <b>3C.</b> | For the circuit shown in Fig.Q3C find $V$ , if switch is opened at $t = 0$ assuming that a steady state having previously been attained.   | <b>2</b> |
| <b>4A.</b> | For the network shown in Fig. Q4A, find $V$ , $dV/dt$ & $d^2V/dt^2$ at $t=0+$ .  | <b>5</b> |
| <b>4B.</b> | Obtain expression for current in the circuit shown in Fig.Q4B.   | <b>3</b> |
| <b>4C.</b> | Express the waveform shown in Fig. Q4C using basic signals.  | <b>2</b> |
| <b>5A.</b> | For the circuit shown in Fig.Q5A, find h parameters  | <b>4</b> |
| <b>5B.</b> | For the network shown in Fig.Q5B find Y parameters.  | <b>4</b> |
| <b>5C.</b> | Sketch the signals (i) $x(t) = r(t) - r(t-1) - r(t-2) + r(t-3)$<br>(ii) $y(t) = 2u(t) - 4u(t-2) + 2u(t-4)$   | <b>2</b> |

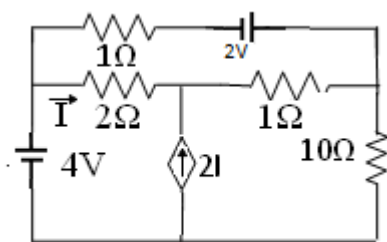


Fig. Q1A

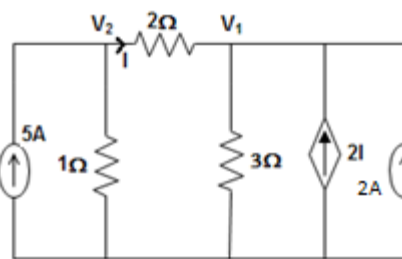


Fig. Q1B

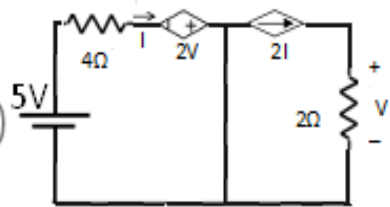


Fig. Q1C

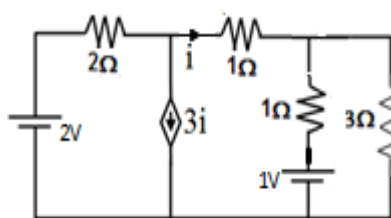


Fig. Q2A

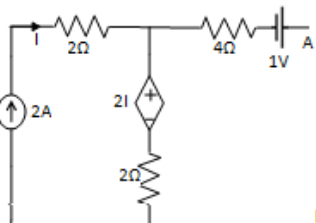


Fig. Q2B

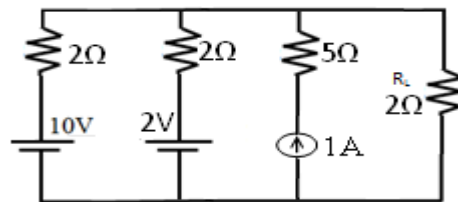


Fig. Q2C

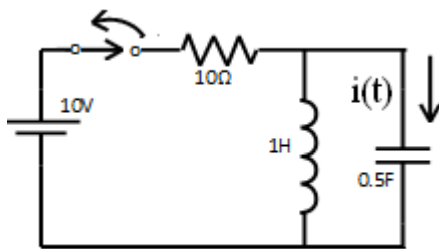


Fig. Q3A

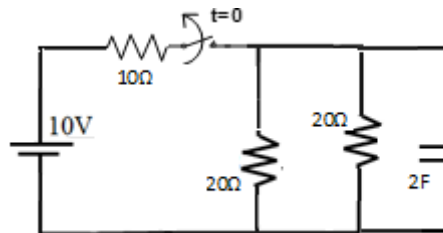


Fig. Q3C

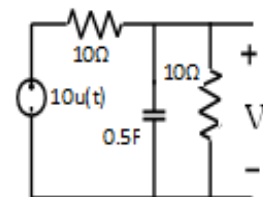


Fig. Q4A

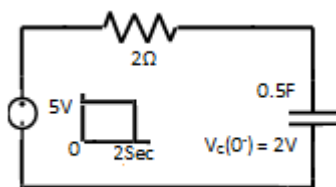


Fig. Q4B

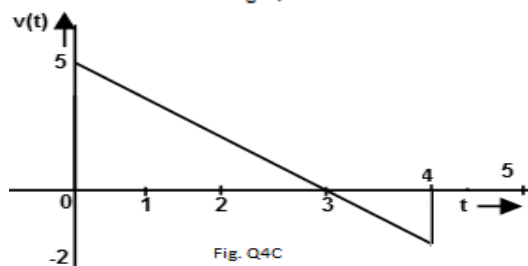


Fig. Q4C

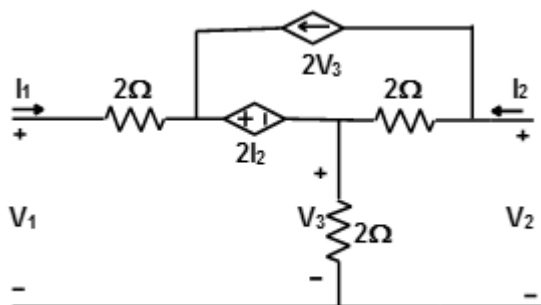


Fig. Q5A

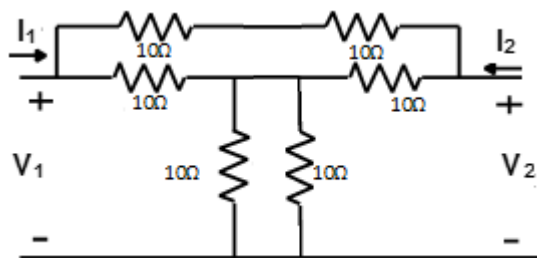


Fig. Q5B