

--	--	--	--	--	--	--	--	--	--



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

A Constituent Institution of Manipal University

I SEMESTER M.TECH (POWER ELECTRONICS & DRIVES)

END SEMESTER EXAMINATIONS, NOVEMBER 2017

SUBJECT: POWER ELECTRONICS DEVICES AND CONVERTER TOPOLOGIES [ELE 5121]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 21 November 2017

Max. Marks: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A. Explain dv/dt and di/dt protection for SCR. Also explain UJT oscillatory triggering circuit for generating gate pulse for SCR. (03)
- 1B. Derive an approximate and exact equivalent circuit of an IGBT from its structural details. Also describe the switching characteristics. (05)
- 1C. A 20V DC source is connected to an R-L load through an SCR with $R = 10 \Omega$ and $L = 20 \text{ mH}$. If the minimum pulse width of the gate current pulse required to turn ON the SCR is $100 \mu\text{s}$, find the latching current of the SCR. (02)
- 2A. With the help of circuit diagram and waveforms of load voltage and load current, explain the working of a single phase fully controlled full wave rectifier feeding an RL load with continuous current. And also derive the RMS output Voltage. (05)
- 2B. Controlled full bridge rectifier has discontinuous current with supply voltage 120V RMS at 60Hz, $R=10\Omega$, $L=20\text{mH}$ and $\alpha=60^\circ$ Determine (i) The average load current (ii) power absorbed by the load. (05)
- 3A. Explain the operation of a three-phase fully controlled converter feeding an RL load with continuous current. Draw the circuit diagram and waveforms of load voltage and load current at firing angle is 60° . Indicate the triggering instants of the devices on the waveform and also derive the output voltage. (05)
- 3B. What are the schemes used for the improvement of power factor in AC-DC converters? With the help of neat diagram and waveform explain the extinction angle control. (05)
- 4A. The boost converter has the input voltage is 6V. The average output voltage is 18V and the average load current is 4 Amp. The switching frequency is 20kHz of $L=250\mu\text{H}$ and $C=420\mu\text{F}$. Determine i) The duty cycle ii) The ripple current of Inductor iii) The peak current of the inductor iv) Ripple voltage of filter capacitor. (05)
- 4B. Discuss the switching scheme for 120° mode of operation of three-phase square wave inverter. Hence plot the phase voltages and any one line voltage waveform. (05)
- 5A. With the help of neat circuit diagram and relevant waveforms explain the working of diode-clamped multilevel inverter. (03)
- 5B. With the help of neat circuit diagram and waveform, explain the operation of ZVS resonant-switch dc-dc converter. (04)
- 5C. Explain Bipolar voltage switching of 1ϕ full bridge voltage source inverters with the help of suitable waveforms. Also draw and explain its harmonic spectrum. (03)