

# Question Paper



## MANIPAL UNIVERSITY


**SCHOOL OF INFORMATION SCIENCES**  
**FIRST SEMESTER Master of Engineering - ME ( VLSI DESIGN)**  
**DEGREE EXAMINATION - NOVEMBER 2017**  
**DATE : Thursday, November 16, 2017**  
**TIME : 10:00AM - 1:00PM**  
**High Level Digital Design [EDA 611]**

Marks: 100


Duration: 180 mins.

### Answer all the questions.

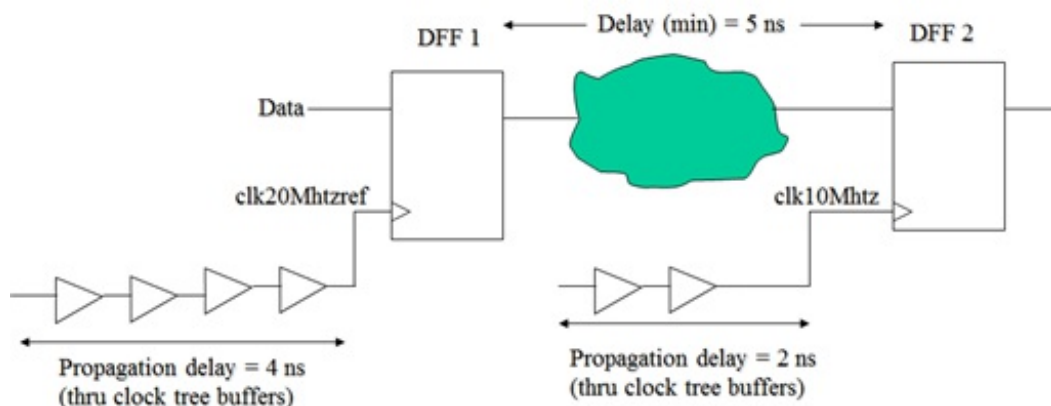- 1) What is VLSI design flow? Explain with a flowchart. (10)
- 2) Solve the logic equation  $F(a,b,c,d) = \sum(0, 1, 5, 7, 8, 10, 14, 15)$  (10)
- 3) Design a Moore machine with an example (10)
- 4) Explain Static Timing Analysis (STA) with necessary diagram & equations (10)
- 5) Detect the timing violation with neat timing diagram for the following design. Consider the following Clock skew of 3.72 between clk20Mhzref and clk10Mhz & clock network delay (10)



 - 6) Draw the timing diagram for the given design & calculate the setup slack (10)



R1 Source Clock signal timing parameters:  
 Clock Edge = 2.002 ns  
 Clock path delay = 0.002 ns

Data path delay = 13.002 ns  
 Setup time constraint = 0.046 ns

R2 Destination Clock signal timing parameters:  
 Min Edge = 20.02 ns  
 Min clock path delay = 0.500 ns

- 7) Design synchronous FIFO using dual port memory (10)
- 8) Explain in detail Logic Array Block (LAB) with neat diagram (10)
- 9) Explain features of AMBA AHB bus and its components (10)
- 10) What is the burst & wrap operation in AMBA bus explain with necessary timing diagram (10)

-----End-----