

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



# MANIPAL INSTITUTE OF TECHNOLOGY

## MANIPAL

A Constituent Institution of Manipal University

### V SEMESTER B.TECH. (MECHATRONICS ENGINEERING)

### END SEMESTER EXAMINATIONS, DEC 2017

SUBJECT: PROGRAMMABLE LOGIC CONTROLLER [MTE 3104]

Time: 3 Hours

MAX. MARKS: 50

#### Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Data not provided may be suitably assumed

- 1A.** Draw a block diagram showing the main units of PLC. Also, write a short note on each of them. **04**
- 1B.** With respect to network topologies explain the following terms along with their advantages and disadvantages: **04**
- i) Star Configuration
  - ii) Ring Configuration
- 1C.** Explain the significance of Remote Terminal Unit (RTU). **02**
- 2A.** With an example explain and compare SKIP function and MCR function in PLC. **03**
- 2B.** An output 'X' is ON only if a count value is less than 31 or more than 38. Write the ladder logic for the same. **03**
- 2C.** Discuss about the I/O modules of PLC. Differentiate between Discrete modules and Analog modules. **04**
- 3A.** With the required sketch, explain the OSI model utilization in PLC, layer by layer. **04**
- 3B.** Elucidate the difference between the following with the help of required sketch: **04**
- a) Sinking device with sourcing output module circuit
  - b) Sourcing device with sinking output module circuit

- 3C.** Explain: **02**
- (i) NEG
  - (ii) XPY
  - (iii) AVE
  - (iv) STD
- 4A.** A conveyor is supposed to have exactly 45 parts on it. There are 3 indicating lights to indicate conveyor count status: **04**
- Less than 45- Yellow
  - Exactly 45- Green
  - More than 45- Red.
- There are 2 sensors on conveyor. One is actuated by Parts entering the conveyor and other is activated by Parts exiting the conveyor.
- 4B.** Discuss the terms: CIM, Plant Controller, Area Controller **06**
- 5A.** Design ladder logic that uses normal timers and counters to measure time of 50 days. Note: Measure minutes, hours and days. **03**
- 5B.** Mention and explain different communication media used for transfer of data signals between devices. **04**
- 5C.** Explain the following with example using ladder logic: **03**
- 1) F-TRIG
  - 2) MCR