

MANIPAL INSTITUTE OF TECHNOLOGY MANIPAL.

SEVENTH SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.) **END SEMESTER EXAMINATIONS, DEC - 2017**

SUBJECT: VLSI DESIGN [ICE 4004]

Time: 3 Hours

MAX. MARKS: 50

	Instructions to Candidates:
*	Answer ALL the questions.
*	Missing data may be suitably assumed.

1A Illustrate the pMOS fabrication process with diagrams.

A Constituent Institution of Manipal University

- **1B** Obtain the expression for the drain to source current in the saturated region of a MOSFET.
- **1C** Briefly explain the importance of MOS transistor threshold voltage. What are the factors 3 affecting it? Illustrate with equations.
- Compare the various CMOS fabrication techniques by listing the advantages and disadvantages 2A 4 of each of them.
- Find the ratio $\frac{\beta_n}{\beta_n}$ needed to obtain an inverter midpoint voltage of V_M=1.3 V with a power supply **2B** 3

of 3 V. Assume that $V_{Tn}=0.6$ V and $V_{Tp}=-0.82$ V. What would be the relative device sizes if $K_n=110 \ \mu A/V^2$ and the mobility values are related by $\mu_n=2.2\mu_n$?

- **2C** Sketch a transistor-level schematic and stick diagram/layout of a 2-input NAND gate. 3 3 **3**A Draw the equivalent RC circuit of a 3-input NAND gate. Sketch a transistor-level schematic of a SR flip-flop. 3 **3B 3C** Illustrate the generalized flow of standard cell place and route with a flowchart. 4 **4**A 3 Explain the structured design techniques. **4B** Briefly explain the various programming technics used in FPGA. 4 3
- **4**C Find a minimum-row PLA table to implement the following equations:

$$x(A, B, C, D) = \sum m(0, 1, 4, 5, 6, 7, 8, 9, 11, 12, 14, 15)$$

$$y(A, B, C, D) = \sum m(0, 1, 4, 5, 8, 10, 11, 12, 14, 15)$$

$$z(A, B, C, D) = \sum m(0,1,3,4,5,7,9,11,15)$$

- 5A Implement a 4:1 MUX using an MUX based FPGA configurable logic block. 3 **5B** Compare each of the following four ASIC subcategories: 4
 - **PLDs** (a)
 - (b) Gate Arrays
 - (c) Standard-cell
 - (d) Full-custom
- **5**C Explain the general structure of a scan-based design with figure.

3

4

3