



SEVENTH SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.)

END SEMESTER EXAMINATIONS, NOV - 2017

SUBJECT: VLSI DESIGN [ICE 4004]


Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Use neat diagrams where ever needed.

- 1A** Illustrate the nMOS fabrication process with diagrams. 4
- 1B** Obtain the expression for drain to source current in non-saturated region of a MOSFET. 3
- 1C** Determine the pull-up to pull-down ratio for an nMOS inverter driven by another nMOS inverter. 3
- 2A** An inverter uses FETs with $\beta_n=2.1 \text{ mA/V}^2$ and $\beta_p=1.8 \text{ mA/V}^2$. The threshold voltages are given as $V_{tn}=0.6 \text{ V}$ and $V_{tp}=-0.7 \text{ V}$ and the power supply has a value of $V_{DD}=5 \text{ V}$. The parasitic FET capacitance at the output node is estimated to be $C_{FET}=74 \text{ fF}$.
 1. Find the midpoint voltage V_M .
 2. Find the values of R_n and R_p .
 3. Calculate the rise and fall times at the output when $C_L=0$.
 4. Calculate the rise and fall times when an external load of value $C_L=115 \text{ fF}$ is connected to the output. 4
- 2B** Sketch a transistor-level schematic and stick diagram/layout for the following function: 4
- $$Y = \overline{AB} + C.(A + B)$$
- 2C** What is body effect? How does it affect the operation of a MOSFET? 2
- 3A** Draw the equivalent RC circuit of a 2-input XOR gate. 3
- 3B** Construct a color-coded stick diagram to implement a priority encoder as in the following table:

 

E_2	E_1	E_0	P_1	P_0
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

- 3C** Sketch a transistor-level schematic of a JK flip-flop. 3
- 4A** Illustrate the design flow of a mixed-signal system with a flowchart. 4
- 4B** Briefly explain the types of basic logic cells employed in a programmable ASIC. 3
- 4C** Implement the following state table using a ROM and two D flip-flops:

Present State	Next State		Output (Z)	
	X = 0	X = 1	X = 0	X = 1
S_0	S_0	S_1	0	1
S_1	S_2	S_3	1	0
S_2	S_1	S_3	1	0
S_3	S_3	S_2	0	1

- 5A** Implement a 4:1 MUX using a 4-input LUT based FPGA configurable logic block. 3
- 5B** Briefly explain the different fault types and models. 3
- 5C** What are the essential circuit models required for Built-in-self-test (BIST)? Illustrate them with figures. 4
