

Question Paper

Exam Date & Time: 07-May-2018 (09:30 AM - 12:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

INTERNATIONAL CENTER FOR APPLIED SCIENCES
III Sem. B.S.(Engg.) Degree Examination April/May 2018
07 May 2018

ELECTRONIC DEVICES AND CIRCUITS [EC 232]

Marks: 100

Duration: 180 mins.

Answer 5 out of 8 questions.

Missing data, if any, may be suitably assumed.

- 1) Design a Zener diode shunt regulated power supply with (10)
following specifications
A)
 - a) O/p voltage is 10V.
 - b) Load current is 50mA
 - c) Maximum power dissipation of 500mw and
 - d) Input voltage is $15 \pm 2V$
- B) Draw the circuit of positive and negative shunt +ve clippers (10)
without bias and briefly explain its operation with the input
and output waveform.
- 2) For a full wave rectifier using center tapped transformer, (10)
derive a) Ripple factor b) Average load current c) RMS
load current d) Efficiency of the rectifier
A)
- B) Explain the working of bridge rectifier circuit Illustrate with (10)
waveform
- 3) With neat circuit diagram and relevant equation explain (8)
self-bias circuit for biasing BJT Describe the concept of
load line and operating point
A)
- B) In a transistor circuit, when the base current is increased (4)
from 0.32 mA to 0.48 mA the emitter current increases
from 15 mA to 20 mA. Determine α_{ac} and β_{ac} values.
- C) Explain with neat circuit diagram functioning of RC-coupled (8)
amplifier. Describe the frequency response of the amplifier.
- 4) Derive an expression for efficiency of Class 'A' power (10)
amplifier
A)
- B) Draw the circuit of class-B Push-Pull power amplifier and (10)
mention its advantages

- 5) Sketch and explain the transfer and output characteristics of Enhanced n type MOSFET (10)
- A)
- B) Design a Colpits oscillator for a frequency of 400MHz Draw the circuit (10)
- 6) With the help of circuit diagram and expressions, explain load regulation and line regulation of voltage using Zener diode. (10)
- A)
- B) Determine V_O for the network shown in Fig Q6B., for the input indicated. Show the steps involved. (10)

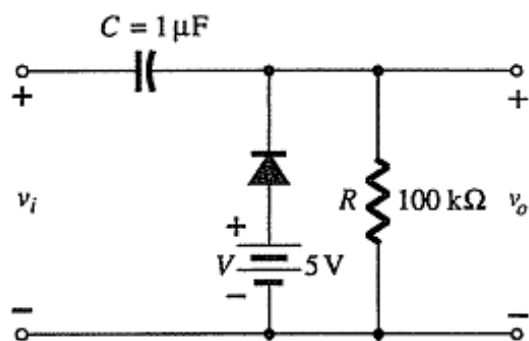
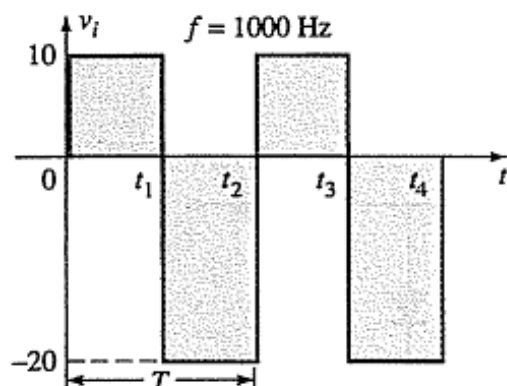


Fig Q6B

- 7) With neat circuit diagram explain the working of Crystal Oscillator Mention its advantages. (10)
- A)
- B) Draw the circuit of Emitter follower. What are the advantages of emitter follower? (10)
- 8) Explain the working of Transistor as a switch and highlight the biasing region of the operation. (10)
- A)
- B) Explain the operation of PN junction diode along with diode current equation and V-I characteristics under different bias conditions. (10)

-----End-----