

# Question Paper

Exam Date & Time: 09-May-2018 (09:30 AM - 12:30 PM)



**MANIPAL ACADEMY OF HIGHER EDUCATION**

**INTERNATIONAL CENTRE FOR APPLIED SCIENCES**

**III SEMESTER B.S. (ENGG.)**

**END - SEMESTER THEORY EXAMINATIONS APRIL - 2018**

**DATE: 09 MAY 2018**

**TIME: 9:30 AM TO 12:30 PM**

**LINEAR NETWORKS TRANSIENT ANALYSIS [EE 231]**


**Marks: 100**

**Duration: 180 mins.**


**Answer 5 out of 8 questions.**

1) Find odd and even components of the following (12)

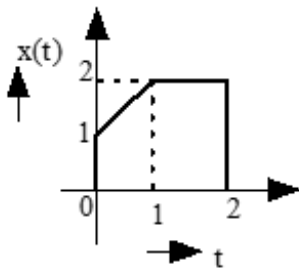
- A) (i)  $x(t) = (1 + t^3)\sin^3 10t$   
(ii)



(iii)

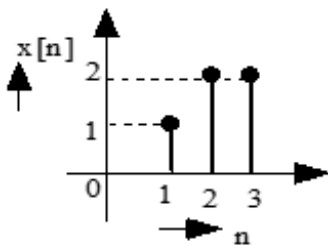

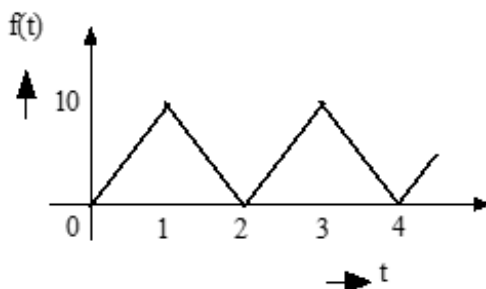B) Find the Laplace transformation of the periodic triangular wave shown (8)



2) Find the initial and final values of the functions whose Laplace transform is (8)

A)

$$(i) F(s) = \frac{2s+4}{6s^2+3s+3}$$

$$(ii) F(s) = \frac{1}{s(s+2)(s-2)}$$

- B) A series RLC circuit is excited by a voltage of E volts by closing the switch. Determine the voltage across the capacitor with  $L=1H$ ,  $C=1/4F$  for the resistance  $R= 2 \Omega, 4\Omega$  and for  $R=5\Omega$ . Comment on the results (12)

- 3) Plot the pole-zero diagram of the following function (10)

A) 
$$F(s) = \frac{10(s+2)(s+4)}{(s+1)(s+3)(s+5)}$$

Hence find the residues at poles and  $f(t)$


- B) Find the Laplace transform of the following functions (10)

(i)  $f(t) = \frac{\sin wt}{t}$   
(ii)  $f(t) = t \cos 3wt$   
(iii)  $f(t) = t^2 \sin wt$

- 4) Using convolution integral theorem, find the Laplace inverse of the following (12)


A) (i)  $F(s) = \frac{1}{s(s+1)}$   
(ii)  $F(s) = \frac{1}{(s-a)^2}$   
(iii)  $F(s) = \frac{1}{s(s+1)(s+2)}$

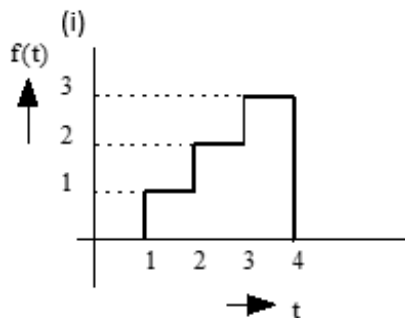- B) Find the Laplace transform of following signal (8)




- 5) Find the network functions  $\frac{V_2}{V_1}, \frac{I_2}{I_1}$  for the network shown below (10)

A)

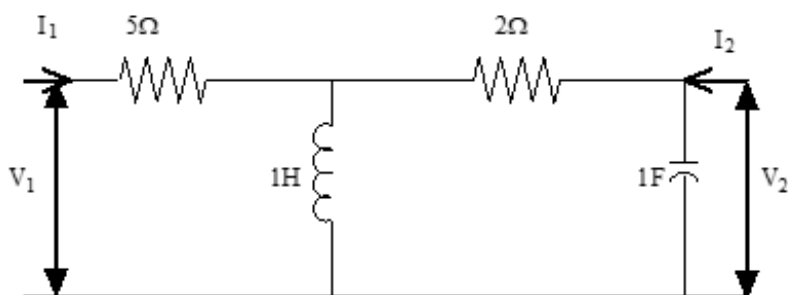

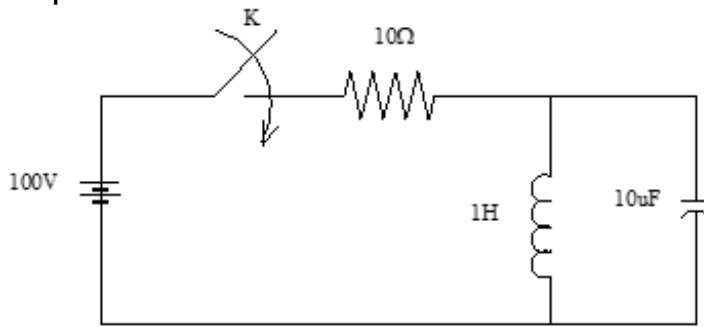- B) In the circuit shown, the switch K is closed and steady state is reached. At  $t=0$  the switch is opened, find the expression for the current in the inductor. (10)




- 6)  $V=10\sin 10t$  is applied to a series RC circuit with  $R=5\Omega$  and  $C=0.5F$ . Find the equation for current, assume zero initial conditions. (10)


- B) Find the current response of a series RL circuit excited by  $V = V_m \sin wt$  (10)

- 7) Determine the source current when the switch is closed at  $t=0$ . Assume zero initial conditions (10)

A)

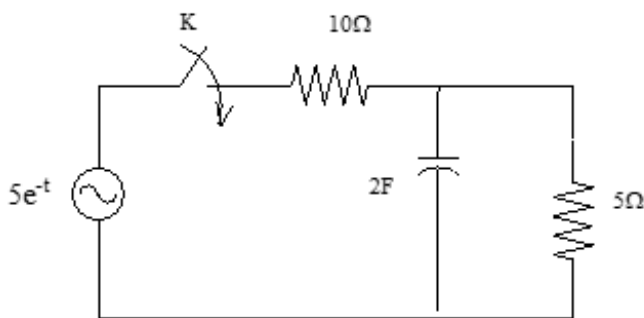

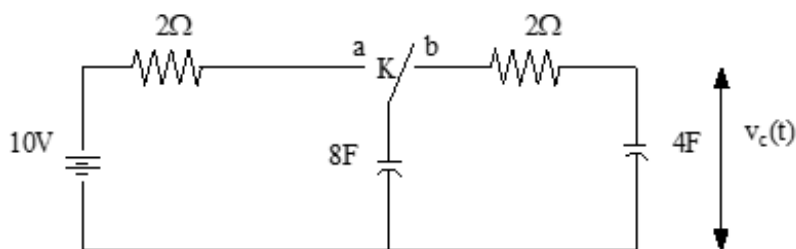- B) In the network shown, the switch is moved from a to b at  $t=0$ , Determine  $v_c(t)$  (10)



- 8) Find the current step and impulse response of the series RL circuit (10)

A)

- B) Find the step response of the voltage across the capacitor in the network with  $R=2\Omega$ ,  $L=1H$  and  $C=1F$  all connected in series. (10)

-----End-----