



### III SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)

#### MAKE UP EXAMINATIONS, MAY 2018

#### SUBJECT: ANALOG ELECTRONIC CIRCUITS [ELE 2105]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 16 MAY 2018

Max. Marks: 50

#### Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- |     |  |   |
|-----|--|---|
| 1A. | In the figure as shown in fig.Q1A, if $V_i$ has a peak of 20 V, then draw the output waveform and transfer characteristics.  | 4 |
| 1B. | Discuss the importance of Diode based Clampers with suitable examples.   | 3 |
| 1C. | Write a note on Zener Voltage regulator.   | 3 |
| 2A. | Define transconductance of MOSFET. Hence derive the equations governing the relationship between transconductance, current, aspect ratio and gate overdrive voltage of the MOSFET.   | 3 |
| 2B. | Discuss the different regions of operation of MOSFET.  | 3 |
| 2C. | Design the circuit shown in Fig. Q2C for a voltage gain of 5V/V and a power budget of 6mW. Assume that the voltage divider branch consumes 5% of total power and voltage drop across $R_s$ is equal to the overdrive voltage of the transistor. Also assume $R_D = 200\Omega$ , $V_{TH} = 0.4$ V, $\mu_n C_{ox} = 200 \mu A/V^2$ , $\lambda = 0$ .   | 4 |
| 3A. | For the NMOS common source amplifier shown in Fig. Q3A, the transistor parameters are: $V_{th} = 0.8$ V, $\mu_n C_{ox} (W/2L) = 1$ mA/V <sup>2</sup> , $V_{DD} = 5$ V, $R_s = 1$ k $\Omega$ , $R_D = 4$ k $\Omega$ , $R_1 = 225$ k $\Omega$ , $R_2 = 175$ k $\Omega$ . Calculate the quiescent values $I_{DQ}$ and $V_{DSQ}$ . Draw the small signal model and hence determine the small signal gain for $R_L$ is infinite. Neglect Channel length modulation. | 5 |
| 3B. | Determine the small signal voltage gain of the multistage cascade circuit shown in Fig. Q3B. Draw the small signal model and neglect channel length modulation.  | 5 |
| 4A. | Bandwidth of an amplifier lies between 100 Hz and 100 kHz. Find frequency range over which voltage gain is less than 1 dB from mid-band value.   | 3 |
| 4B. | Design an NMOS current mirror with $V_{DD} = 5$ V, $V_{SS} = 0$ V, $I_{ref} = 100 \mu A$ . For the matched transistors $L = 10 \mu m$ , $W = 100 \mu m$ , $V_{TH} = 1$ V, $\mu_n C_{ox} = 20 \mu A/V^2$ .  | 3 |
| 4C. | State and prove Millers theorem.   | 4 |
| 5A. | Classify the power amplifiers based on the operating point.  | 2 |
| 5B. | Derive the expression for conversion efficiency of Class A Power amplifier.  | 4 |
| 5C. | Derive expressions for Differential gain, Common mode gain and CMRR of a MOS Differential Pair.  | 4 |

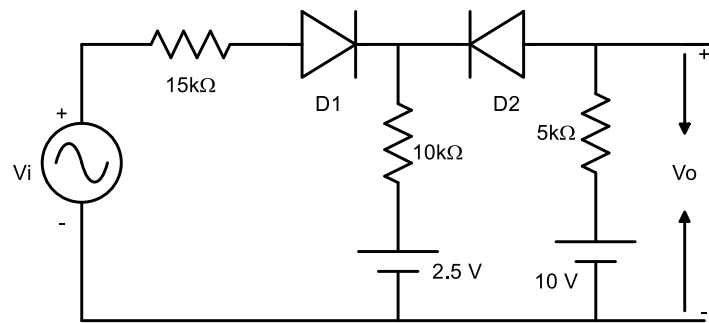


Fig Q1A

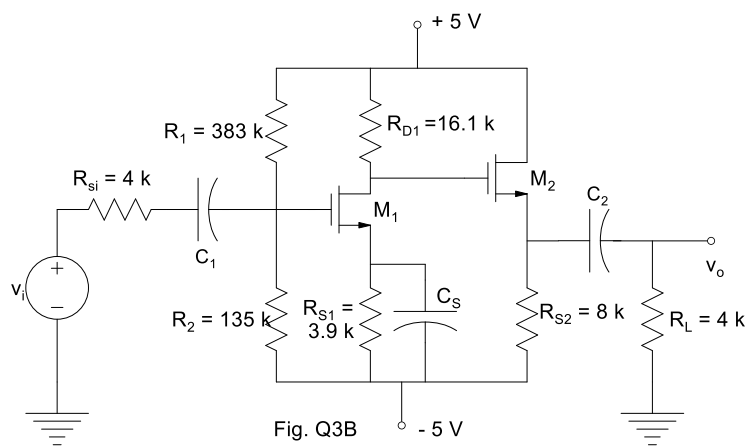


Fig. Q3B

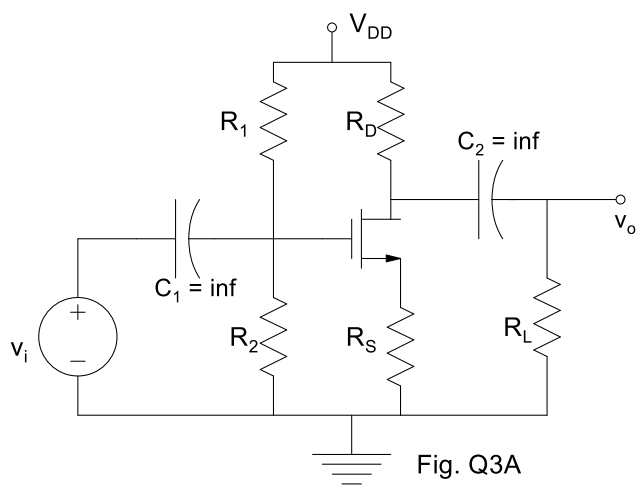


Fig. Q3A

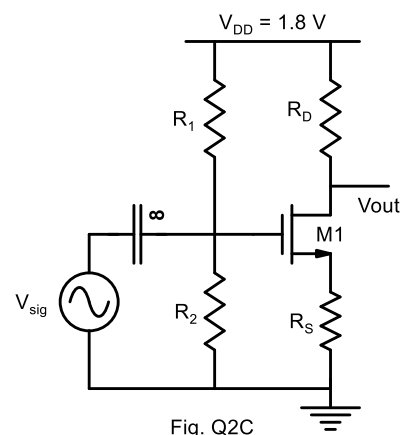


Fig. Q2C