

Reg. No.											
----------	--	--	--	--	--	--	--	--	--	--	--



# MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

A Constituent Institution of Manipal University

**IV SEM B.Tech (BME) DEGREE MAKE-UP EXAMINATIONS, JUNE 2018.**

**SUBJECT: INTEGRATED CIRCUIT SYSTEMS (BME 2202)**  
**(REVISED CREDIT SYSTEM)**

**Thursday, 14<sup>th</sup> June, 2018, 2 to 5 PM**

**TIME: 3 HOURS**


**MAX. MARKS: 100**

## Instructions to Candidates:

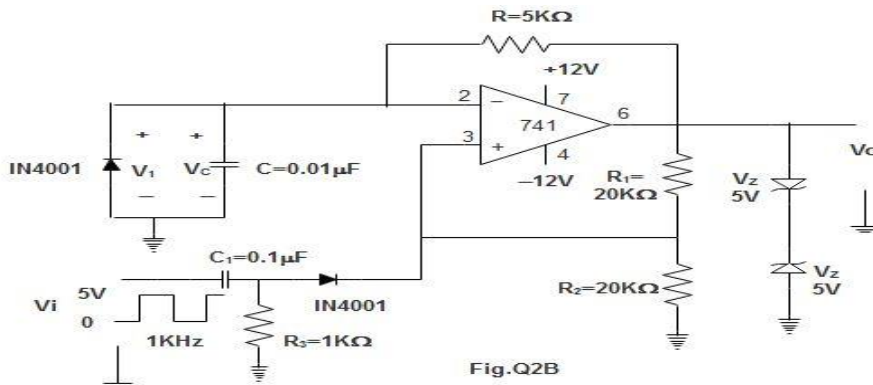1. Answer ALL questions.
2. Draw labeled diagram wherever necessary

- 1A) Draw a differential amplifier circuit included with constant current source. Derive the expression of the constant current  $I_o$ . 6
- 1B) (i) List the characteristics of an ideal Op-Amp. 2+4  
 (ii) Design and draw the circuit using Op-Amp to obtain the following expression.  

$$V_o = 3V_1 + 1.5V_2 - 2V_3$$
- 1C) Discuss on the temperature drift of input offset voltage and input offset current for an Op-Amp. An inverting Op-Amp amplifier has  $R_1=20K\Omega$  and  $R_F=200K\Omega$ . Assume the amplifier is nulled at  $27^\circ\text{C}$ . Calculate the error voltage  $E_v$  and the output voltage at  $40^\circ\text{C}$  with  $V_i=0.2\text{V}$  dc. Given, Input offset voltage drift is  $30\mu\text{V}/^\circ\text{C}$  and input offset current drift is  $300\text{pA}/^\circ\text{C}$ . 8
- 2A) Draw the circuit of an instrumentation amplifier suitable for amplifying the voltage from the bridge type of temperature transducer. Derive the expression of the output. 8
- 2B) The circuit shown in the Fig Q2B is a positive edge triggered mono-stable multi-vibrator. For this circuit draw the waveforms  $V_o$  and  $V_c$  with respect to the input waveform  $V_i$ . Calculate and label all the voltage levels of both waveforms and the pulse width  $t_P$  of  $V_o$ . 6



2C) Design and draw an inverting Schmitt trigger circuit using Op-Amp with, 6  
 UTP = 4V and LTP = -2V. Assume  $V_{CC} = \pm 12$  Volts.


3A) Design and draw a 4<sup>th</sup> order active low pass Butterworth filter suitable to pass ECG 8  
 signals up to a frequency of 100 Hz. The overall gain of the filter is 100. Given the factor of polynomials  $P_n(s)$  is,  $(s^2 + 0.675s + 1)(s^2 + 1.848s + 1)$

3B) With the help of suitable block/circuit diagram explain how two signals  $V_{S1}$  and 6  
 $V_{S2}$  are multiplied?

3C) Write a note on delay Equalizer. 6

4A) Draw the pin diagram and internal diagram of timer IC 555. Explain the function of 6  
 each pin of the IC.

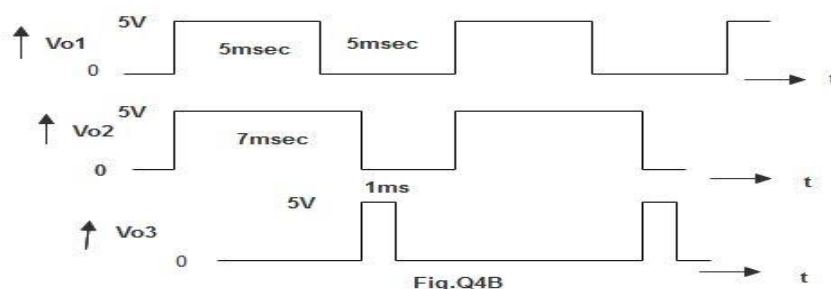4B) Design and draw the necessary circuit using timer IC to obtain the waveforms 8  
 shown in Fig.Q4B.



4C) With a suitable circuit explain how a mono-pulse is generated using timer IC 6  
 without using a trigger input?

5A) Design a regulated power supply for the following specifications. Output voltage 8  
 can be varied between -10 volts to -15 volts. The maximum load current is 450 mA. Input is 230V, 50 Hz ac. Use a suitable regulator IC and other components. Assume a suitable ripple factor to design the filter capacitor of the full wave bridge rectifier. Obtain the appropriate specifications of the transformer to be used for this circuit.

5B) With a suitable block diagram explain the working of a successive approximation 6  
 type ADC.

5C) Write a note on VCO IC 566. 6