



**FOURTH B.Tech (E & C) DEGREE END SEMESTER EXAMINATION**

**APRIL/MAY 2018**

**SUBJECT: DSD USING VERILOG (ECE - 2204)**

**TIME: 3 HOURS**

**MAX. MARKS: 50**

**Instructions to candidates**

- Answer **ALL** questions.
- Missing data may be suitably assumed.

- 1A. Consider a CPLD that contains 8 macrocells in one LAB block. A function  $F = ABCD + A'BCD + A'BCD' + AB'CD + A'B'C'D + A'B'CD' + ABCD' + A'BC'D$  should be implemented using CPLD. In one LAB block, there are four macrocells, each one is 3-wide OR array and remaining macrocells are 5-wide OR array. Implement the functions with minimum number of macrocells present in LAB block. Use parallel expander logic.
- 1B. Consider the sequential element of ACT-2 FPGA as shown in **Figure 1B**. Implement (i) Transparent low Latch (ii) Positive edge triggered D-FF.
- 1C. Implement  $F = A B' + A C$  using ALTERA MAX structure. Show the connections using applicable switching elements.

(5+3+2)

- 2A. Implement 0101 overlapping sequence detector using ACT-2 FPGA having combinational and sequential modules.
- 2B. Implement 4 to 1 multiplexer using Xilinx FPGA. Specify the content of LUT.
- 2C. List the disadvantages of Polysilicon diffusion anti-fuse.

(5+3+2)

- 3A. Write a structural Verilog program for a 4:1MUX using 2:1 MUX.
- 3B. Write the syntax for Verilog procedural assignments. Find the output of two statements

**S1: begin**  
 a = 1;  
 #10 a = 0;  
 #5 a = 4;  
**end**

**S2: begin**  
**begin**  
 a <= 1;  
 #10 a <= 0;  
 #5 a <= 4; **end**

- 3C. Write a switch level Verilog code for a CMOS inverter.


(5+3+2)

- 4A. Write a structural Verilog program for a sequential circuit of a BCD to XS-3 code converter as shown in **Figure 4A**. Write the Verilog code for D flip-flop, 3 input NAND gate and 2 input NAND gate.
- 4B. Write a sequential Verilog code for 3-bit binary-to-gray code converter using function that evaluates the two-input EX-OR expression.
- 4C. What are user defined primitives? List the types of UDPs.


(5+3+2)

- 5A. Consider the circuit shown in **Figure 5A** below and apply D-algorithm. Find (i) singular cover of G1 and G3 (ii) PDC of G4 and G5 (iii) PDCF of G2.
- 5B. Determine the test vector for the sequential circuit shown in **Figure 5B** using ITG.
- 5C. Find the test vector to test single SA0 fault for the circuit shown in **Figure 5C** using PODEM technique.


(5+3+2)

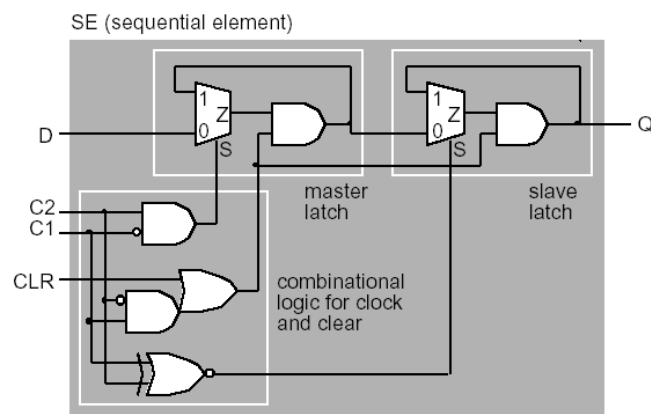


**Figure 1B**

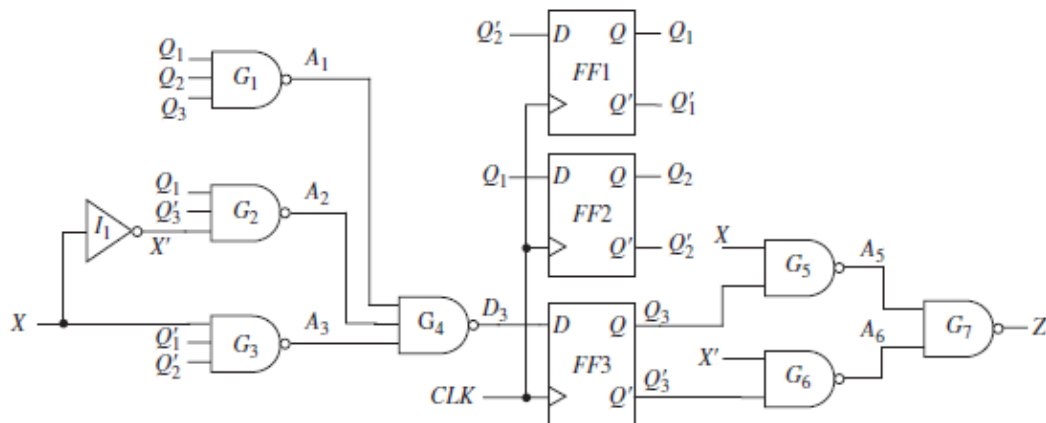


**Figure 4A**

 

**Figure 5A**

 

**Figure 5B**

 

**Figure 5C**