

Question Paper

Exam Date & Time: 16-Nov-2018 (02:00 PM - 05:00 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

**INTERNATIONAL CENTRE FOR APPLIED SCIENCES
THIRD SEMESTER B.Sc. Applied sciences in Engg.
END-SEMESTER THEORY EXAMINATIONS NOVEMBER-2018
LINEAR NETWORKS TRANSIENT ANALYSIS [EE 231]**


Marks: 100

Duration: 180 mins.

Answer 5 out of 8 questions.



- 1) Find the Laplace transformation of the periodic signal (8)
shown below

A)

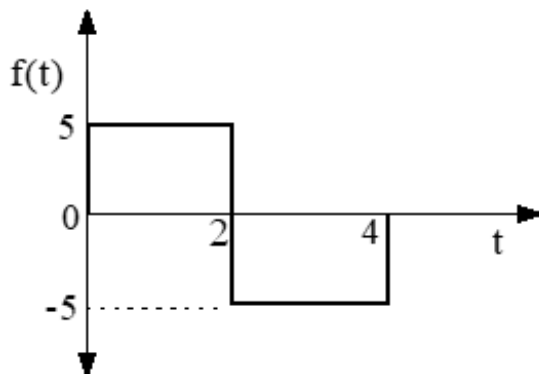

- B) Find odd and even components of the following (12)

(i) $x(t) = (2 + t^3)\cos^2 5t$

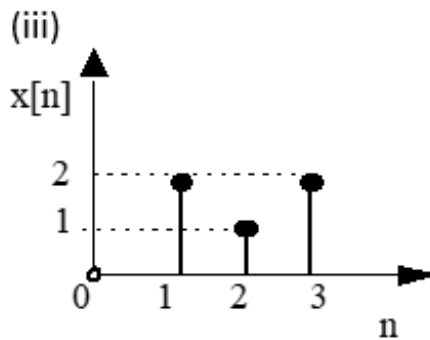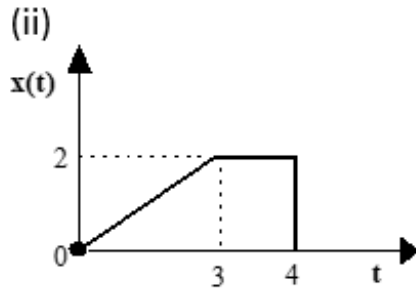

- 2) Find the initial and final values of the functions whose Laplace transform is (8)

A)

i. $F(s) = \frac{2(s+5)}{s^2 + 3s + 5}$

ii. $F(s) = \frac{1}{s(s+4)(s-4)}$

- B) A series RLC circuit is excited by a voltage of E volts by closing the switch. Determine the voltage across the capacitor with $L=1\text{H}$, $C=1/4\text{F}$ for the resistance $R= 2\Omega$, 4Ω and for $R=5\Omega$. Comment on the results (12)

- 3) Plot the pole-zero diagram of the following function (10)

A)

$$F(s) = \frac{5(s^2 + 4)}{s(s+1)(s+2)}$$

Hence find the residues at poles and $f(t)$


- B) Find the Laplace transform of the following functions (10)

- i. $f(t) = \frac{\sin wt}{t}$
- ii. $f(t) = t \sin 3wt$
- iii. $f(t) = t \cos 3wt$


- 4) Using convolution integral theorem, find the Laplace inverse of the following (12)
- A)

- i. $F(s) = \frac{s}{(s+1)(s+2)}$
- ii. $F(s) = \frac{1}{(s-b)^2}$
- iii. $F(s) = \frac{5}{s(s+1)(s+2)}$

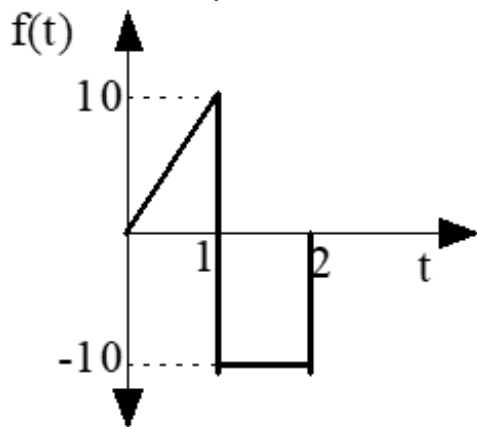- B) Find the Laplace transform of following signal (8)




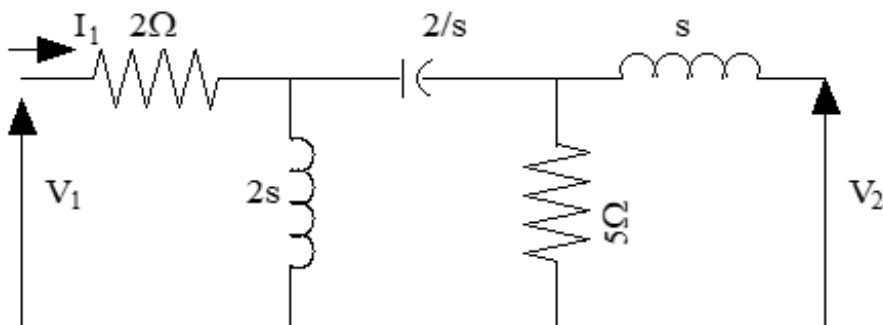- 5) Find the network functions V_2/V_1 , V_1/I_1 for the network shown below (10)
- A)



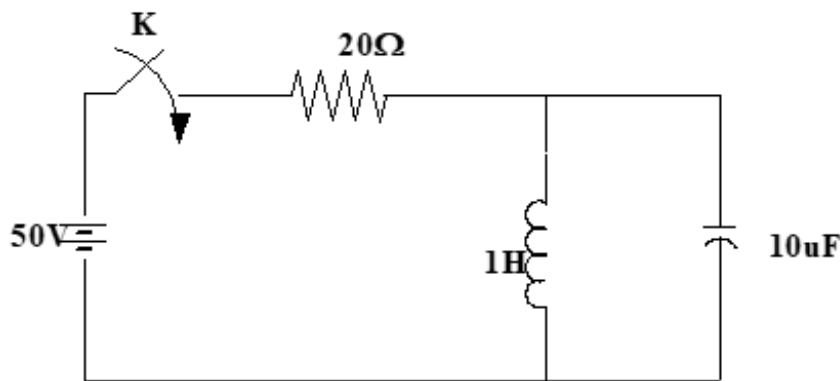- B) In the circuit shown, the switch K is closed and steady (10)


state is reached . At $t=0$ the switch is opened, find the expression for the current in the inductor




- 6) $V=20\sin 2t$ is applied to a series RC circuit with $R=10\Omega$ and $C=0.5F$. Find the equation for current, assume zero initial conditions. (10)

- A) Find the current response of a series RL circuit excited by $V=V_m\sin \omega t$ (10)

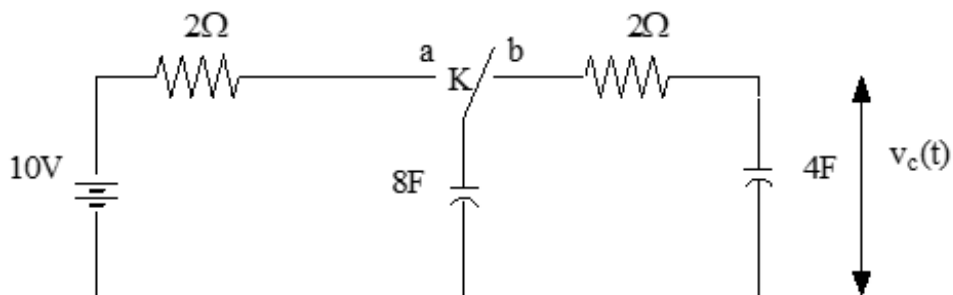- 7) In the network shown, the switch K is moved from a to b at $t=0$, Determine $v_c(t)$ (10)



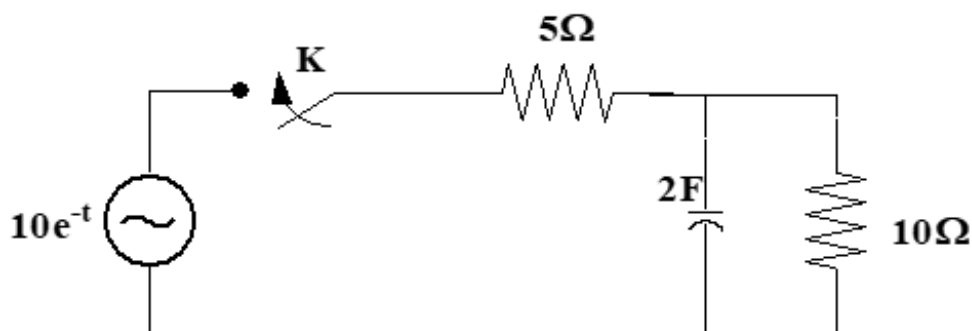- B) Determine the source current when the switch K is closed at $t=0$. Assume zero initial conditions (10)



- 8) Find the step response of the voltage across the capacitor (10)
in the network with $R=2\Omega$, $L=1H$ and $C=1F$ all connected in series.
- A)
- B) Find the current step and impulse response of the series (10)
RC circuit

-----End-----