

Question Paper

Exam Date & Time: 16-Nov-2018 (02:00 PM - 05:00 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

INTERNATIONAL CENTRE FOR APPLIED SCIENCES THIRD SEMESTER B.Sc. Applied Sciences in Engg. END-SEMESTER THEORY EXAMINATIONS NOVEMBER - 2018 NETWORK ANALYSIS [IEE 231]

Marks: 100

Duration: 180 mins.

Answer 5 out of 8 questions.

Missing data, if any, may be suitably assumed

- 1) Find the laplace transformation of the periodic rectified sine wave with period T and peak value of A (5)
- A)
- B) Find the initial and final values of the function whose laplace transform is (6)
- $$F(s) = \frac{(2S+1)}{(6S^2+11S+6)} \quad \text{and} \quad F(s) = \frac{10}{S(S^2+2S+4)}$$
- C) Currents I_1 & I_2 entering port1 & port 2 respectively are given by (9)
- $$I_1 = 0.5 V_1 - 0.2 V_2$$
- $$I_2 = -0.2 V_1 + V_2$$
- Find Y, Z and ABCD parameters.
- 2) A step voltage of E volts is applied to a series RLC circuit with (12)
- A) $L=1H$, $C=\frac{1}{4}F$. Find the voltage across the capacitor for the following values of resistance. (8)
- R=2 Ω , R=4 Ω and R=5 Ω . Comment on the results.
- B) Find the Thevenin equivalent for the network shown in Fig 2B (8)

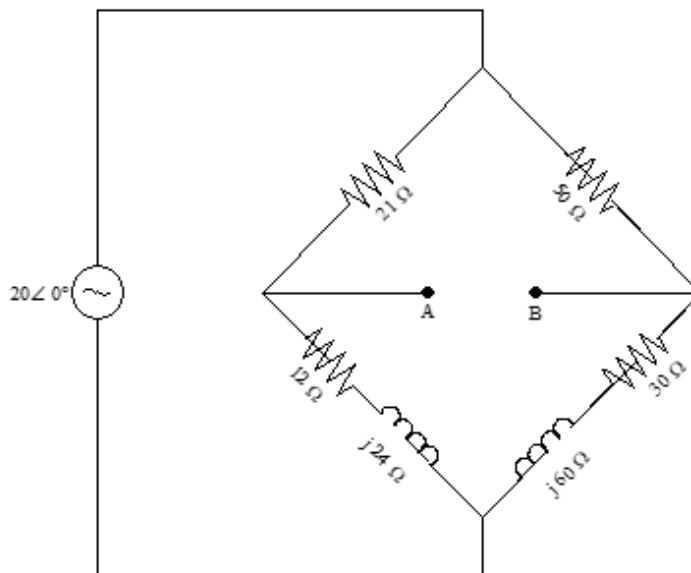


Fig 2B

- 3) Two coils with $L_1 = 6.8 \text{ mH}$ and $L_2 = 4.5 \text{ mH}$ are connected in series cumulative mode and differential mode. The equivalent inductance in cumulative mode is 19.6 mH and in differential mode is 3 mH . Find the value of mutual inductance and coefficient of coupling. (8)
- A)

- B) Using convolution theorem evaluate the inverse laplace transform of the following. (12)

i) $\frac{1}{(s+a)^2}$ ii) $\frac{1}{s(s+a)}$ iii) $\frac{1}{(s^2+1)^2}$

- 4) Find the laplace transform of the following functions. (12)

A) i) $f(t) = \cos^2 t$ ii) $f(t) = t \sin \alpha t$ iii) $f(t) = \frac{(1-e^{-t})}{t}$ iv) $(t+1)^2 e^t$

- B) Find the Y parameters of the network shown in Fig 4B. (8)

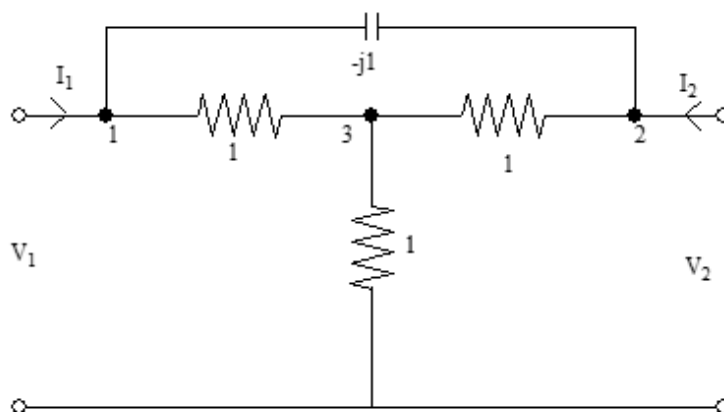


Fig 4B

- 5) Find the network functions $\frac{V_1}{I_1}$, $\frac{V_2}{I_1}$ for the network in Fig 5A. (10)
- A)

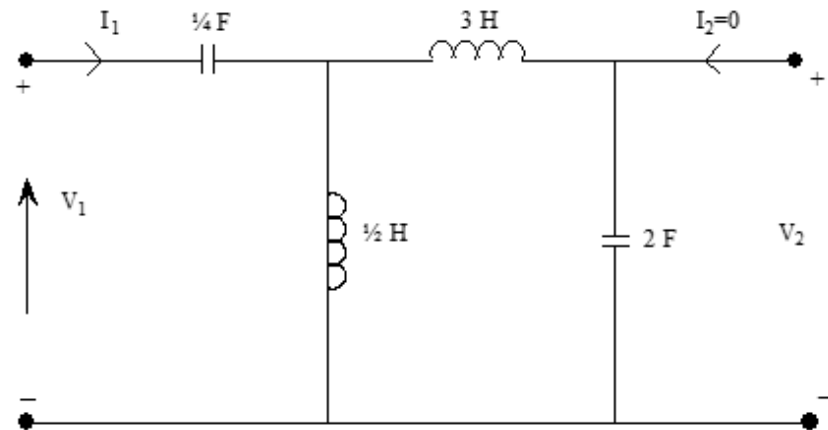


Fig 5A

- B) For the given electrical circuit shown in Fig 5B find $\frac{V_o(s)}{V_i(s)}$. (10)

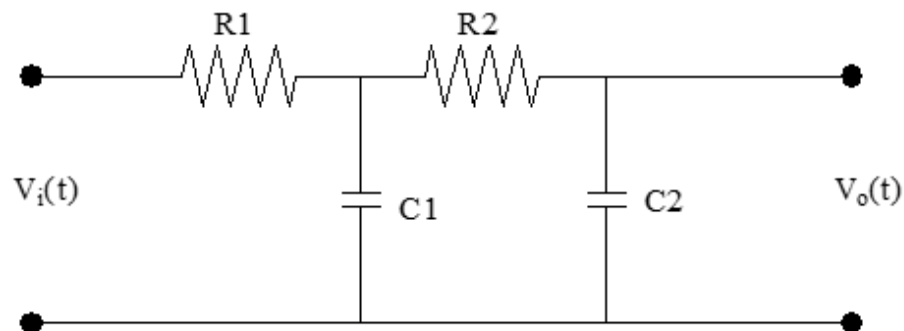


Fig 5B

- 6) A rectangular pulse of height 1 and width T is applied to a series RC circuit. Find the expression for voltage across the capacitor and plot the waveform. (10)
- A)
- B) Find the value of Z_L so that maximum power can be transferred to it (Fig 6B). Find the maximum power. (10)

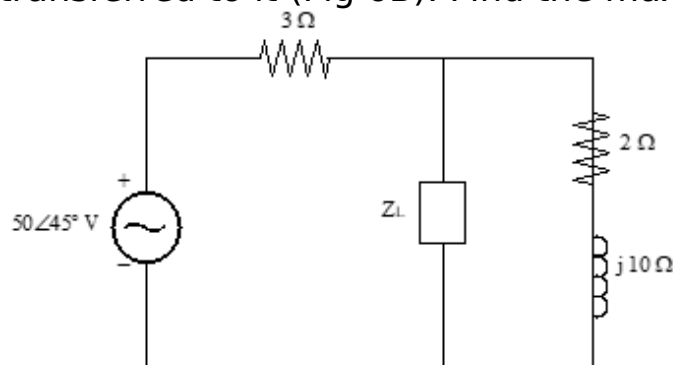


Fig 6B

- 7) For the network shown in Fig.7A find K and place the dots so that the power output of source is 168 W. (10)

A)

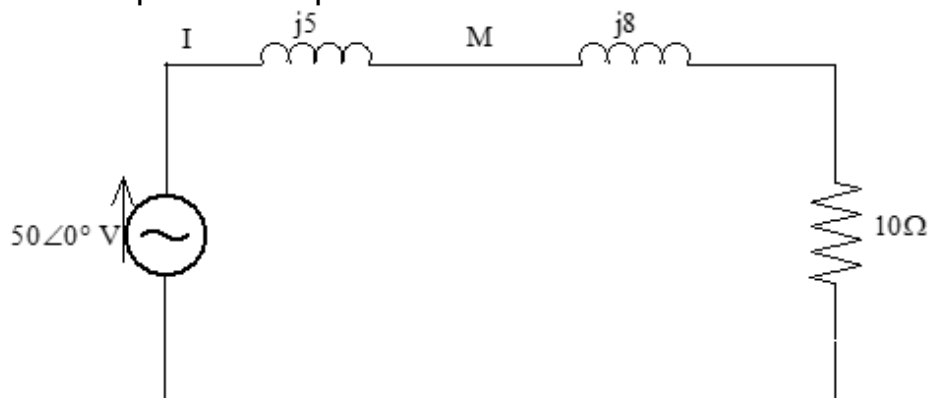


Fig.7A

- B) In the network shown in Fig 7B, the switch is moved from a to b, (10)
at $t=0$, find $V(t)$

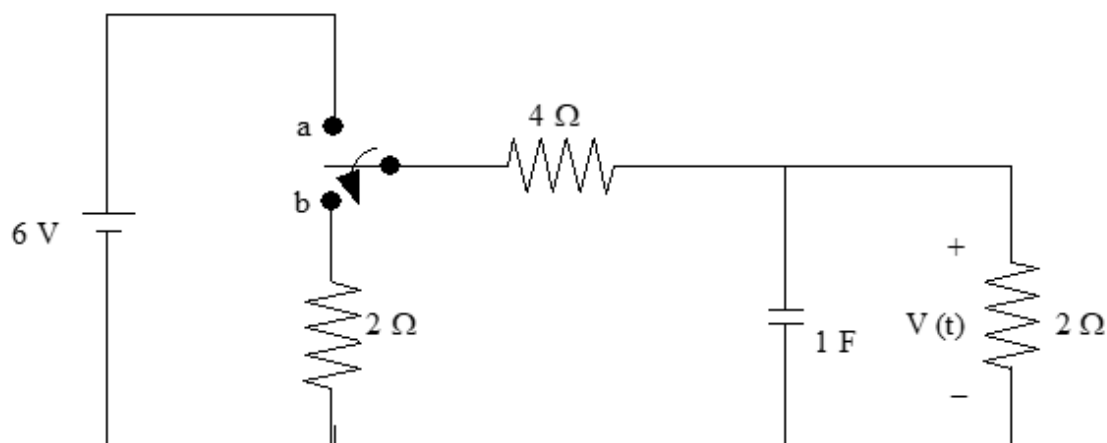


Fig 7B

- 8) Find the current through the 6Ω resistor on Fig 8A using mesh (10)
analysis.

A)

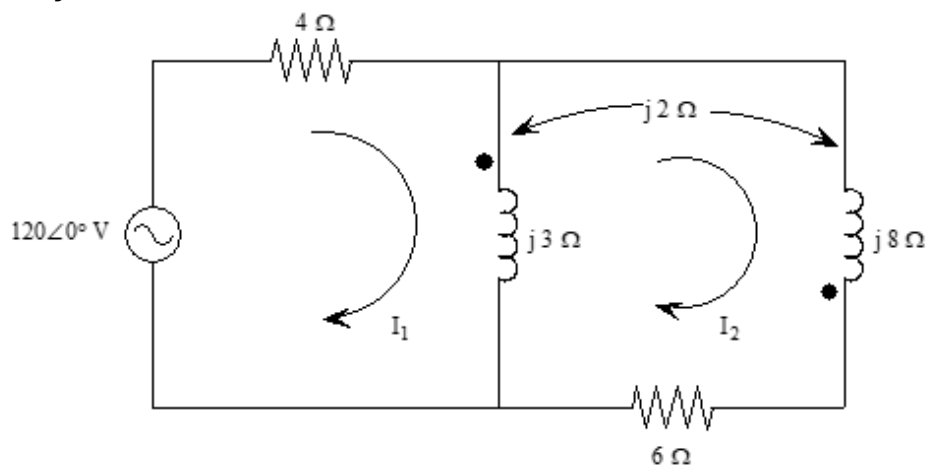


Fig 8A

- B) In the network shown in Fig 8B, the switch is moved from a to b at $t=0$, determine $V_c(t)$. (10)

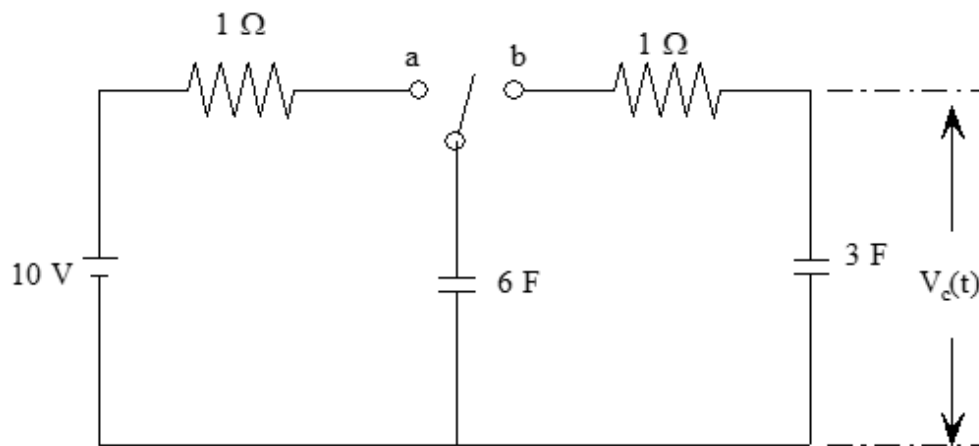


Fig 8B

-----End-----