

Question Paper

Exam Date & Time: 20-Nov-2018 (02:00 PM - 05:00 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

INTERNATIONAL CENTER FOR APPLIED SCIENCES END SEMESTER EXAMINATION NOV./DEC. 2018

SWITCHING CIRCUITS AND LOGIC DESIGN [ICS 232]

Marks: 100

Duration: 180 mins.

Answer 5 out of 8 questions.

Missing data may be suitably assumed

- 1) i) Express DeMorgan's theorem in terms of logic gates. (8)
4M
A) ii) Draw the NAND gate and NOR gate realization of $f(x_1, x_2, x_3) = \sum m(2, 3, 4, 6, 7)$. **4M**
- B) Simplify the following expressions using algebraic manipulation. (12)
i) $f = (x_1 + x_3 + x_4) \cdot (x_1 + x_2' + x_3) \cdot (x_1 + x_2' + x_3' + x_4)$ **3M**
ii) $A'B + A'B'C'D' + ABCD'$ **3M**
iii) $f = (x_1 + x_2 + x_3) \cdot (x_1 + x_2' + x_3) \cdot (x_1' + x_2' + x_3) \cdot (x_1 + x_2 + x_3')$ **3M**
iv) $f = x_1x_2'x_3' + x_1x_2x_4 + x_1x_2'x_3x_4'$ **3M**
- 2) i) Define the terms implicant, prime implicant, essential prime implicant and cover. **4M** (10)
A) ii) Consider the function $f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 4, 5, 10, 11, 13, 15)$. Using k-map, find the prime implicants, essential prime implicants and minimal cover. **6M**
- B) i) Using k-map, determine the simplest SOP and POS expressions for the function $f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$. **6M** (10)
ii) Consider the function $f(a, b, c, d) = \sum m(0, 4, 5, 6, 9, 10, 11, 15)$. Use functional decomposition to find the minimal SOP expression for f . **4M**
- 3) Consider the function $F(w, x, y, z) = \sum (1, 4, 6, 7, 8, 9, 10, 11, 15)$. (10)
A) Using tabulation method, find the minimal SOP expression

for F.

- B) Represent the following pairs of decimal numbers using 6-bit 2's-complement system, then subtract the second number from the first using binary addition. State whether or not overflow occurs in each case. (10)

a) +22 and +31 b) -31 and +29 c) -1 and +7
d) +7 and -8 e) +26 and -30

5x2M

- 4) Write Verilog code for 16-bit ripple carry adder constructed using 4-bit ripple carry adders. (10)

A)

- B) i) Write Verilog code to convert an n-bit binary number into equivalent grey code. **5M** (10)

ii) Draw the logic diagram of full adder. Write the truth table for full adder and derive the equations for S_i and C_{i+1} . **5M**

- 5) i) Implement three-input XOR function using (10)

A) a) 2-to-1 MUX **4M**

b) 4-to-1 MUX **3M**

ii) Implement three-input majority function using 2-to-1 MUX **3M**

- B) i) Write Verilog code for a 4-to-16 decoder constructed using 2-to-4 decoders. **6M** (10)

ii) A combinational circuit is specified by the following three functions:

$$F1 = X'Y'Z' + XZ$$

$$F2 = XY'Z' + X'Y$$

$$F3 = X'Y'Z + XY$$

Design a circuit for $F1$, $F2$ and $F3$ using a decoder and other gates. **4M**

- 6) Design a synchronous counter with the repeated binary sequence 0, 1, 2, 4, 5, 6. Use JK flip flops. (10)

A)

- B) Design a sequential circuit which has three flip flops, A, B, C; one input, x; and one output, y. The state diagram is given in Fig Q.6.B. Use D flip flops. (10)

 


Fig. Q.6.B

- 7) Design a 4-bit bi-directional shift register for the following operations using D flip flops and MUXs. (8)

A)

S₁S₀ Operation

- 00 No change
- 01 Right shift
- 10 Left shift
- 11 Parallel load

- B) Write behavioral verilog code for N-bit shift register. (6)
- C) Draw the logic diagram of JK flip flop. Write its characteristic table, characteristic equation and excitation table. (6)
- 8) Explain the following with a neat diagram for each. (12)
- A)
- i) NMOS realization of a NAND gate. **3M**
 - ii) NMOS realization of a NOR gate. **3M**
 - iii) CMOS realization of a NAND gate. **3M**
 - iv) CMOS realization of a NOR gate. **3M**
- B)
- i) Discuss PLA with a neat logic diagram. **6M**
 - ii) Define a tri-state buffer. Write its truth table. **2M**

-----End-----