

# Question Paper

Exam Date & Time: 28-Nov-2018 (09:30 AM - 12:30 PM)



## MANIPAL ACADEMY OF HIGHER EDUCATION

### INTERNATIONAL CENTRE FOR APPLIED SCIENCES

#### IV SEMESTER B.S. ENGG END SEMESTER EXAMINATION - Nov./ Dec. 2018

#### Electronic Devices and Computer Interfacing [CS 241 A]

Marks: 100

Duration: 180 mins.

#### Answer 5 out of 8 questions.

- 1) What is doping of a semiconductor? Draw the energy band diagrams and explain p-type and n-type Doping. (10)
  - A)
  - B) Explain drift current and diffusion current with relevant expressions. (10)
- 2) Draw and explain the input and output characteristics of npn transistor in common emitter configuration indicating different regions of operation. (10)
  - A)
  - B) With help of circuit diagram and waveforms explain the working of half-wave rectifier. Give the expressions for ripple factor and output voltage. (10)
- 3) A Silicon diode has a saturation current of  $1\text{pA}$  at  $20^{\circ}\text{C}$ . (10)
  - A) Determine (i) Diode bias voltage when diode current is  $3\text{mA}$  (ii) Diode bias current when the temperature changes to  $100^{\circ}\text{C}$ , for the same bias voltage.
  - B) In a zener network,  $R_S = 120\Omega$ ,  $R_L = 250\Omega$  and  $V_Z = 5\text{V}$ . (10)  
Find the  $I_{Z\min}$ ,  $I_{Z\max}$ ,  $P_{Z\min}$  when input varies from  $9\text{V}$  to  $15\text{V}$ . Draw the circuit.
- 4) Realize each of the following equations using single OPAMP. Draw the circuit diagram. Derive the input output relation and determine the component values. (10)
  - A) (i)  $V_o = -(2V_1 + 5V_2)$  (ii)  $V_o = V_1 - 0.2V_2$
  - B) Draw the fixed bias circuit for junction transistor. (10)  
Determine  $R_B$  and  $R_C$  if  $V_{CC} = 10\text{V}$  and operating point is  $(5\text{V}, 3\text{mA})$ . Assume  $\beta = 100$ ,  $V_{BE} = 0.3\text{V}$ .

- 5) Explain the working of an op-amp integrator. Sketch the out waveform if the input is a square wave. (10)
- A)
- B) Draw the circuit for 8 bit flash ADC and explain it's working. (10)
- 6) Draw the circuit diagram of an RC phase shift oscillator. (10)
- A) Give the expression for output frequency.
- B) Explain what is meant by line regulation and load regulation. (6)
- C) For an astable multivibrator using IC555,  $R_A=390\Omega$ ,  $R_B=180\Omega$ , and  $C=6.8\mu F$ . Calculate  $T_{on}$  and frequency of the output. (4)
- 7) Draw the cross section of n-channel enhancement mode MOSFET. What is the difference between enhancement mode and depletion MOSFETs? (10)
- A)
- B) Draw the cross section of SCR and label its parts. Also Draw the VI characteristics. (10)
- 8) Explain the working of AC to AC converter using Triac. (10)
- A) Draw the circuit, and input and output waveforms.
- B) Explain the working of Opamp subtractor with proper circuit and mathematical expression for output. (10)

-----End-----