

Question Paper

Exam Date & Time: 03-Dec-2018 (09:30 AM - 12:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

INTERNATIONAL CENTRE FOR APPLIED SCIENCES

IV SEMESTER B.S. ENGG. END SEMESTER EXAMINATION - NOV./ DEC. 2018

IC Systems [EC 243A]

Marks: 100

Duration: 180 mins.

Answer 5 out of 8 questions.

- 1) Draw the circuit of an emitter coupled differential amplifier. (10)
Derive an expression for CMRR.
 - A)
 - B)
- 2) Mention any four characteristics of ideal OP-AMP. Draw the internal block diagram of OP-AMP and explain each block. (10)
 - A)
 - B)
- 3) Draw the circuit diagram of OP-AMP based i) differential amplifier ii) four input summing amplifier. Derive the expression of the output voltage for both the circuits. (10)
 - A)
 - B)
- 4) Draw the schematic diagram of feedback amplifier and derive the expression for closed loop gain. What are the advantages of negative feedback? (10)
 - A)
 - B)
- 5) Draw an inverting amplifier circuit using OP-AMP. Derive the expression for the output voltage assuming ideal conditions. Design the circuit to obtain voltage gain of 10. Draw the output waveform for the input signal
(i) $V_i = 0.5\sin(3140t)$ (ii) $V_i = 4\sin(3140t)$ Use supply voltage $\hat{A}\pm 11V$. Assume gain of OP-AMP is 10. (10)
 - A)
 - B)
- 6) Draw the circuit diagram of OP-AMP based triangular wave generator. Explain its working principle with neat waveform and necessary derivations. (10)
 - A)
 - B)
- 7) Draw the circuit diagram of second order Butterworth active High pass filter and derive the expression for Transfer function. (10)
 - A)
 - B)
- 8) Draw the circuit diagram of precision full wave rectifier. Explain its working principle with neat waveform and necessary derivations. (10)
 - A)
 - B)

- 5) Draw the circuit diagrams of V to I converter with Floating and Grounded load using OP-AMP. Derive the expressions for load current. (10)
- A)
- B) Draw the circuit of an 8-bit successive approximation type ADC. Explain the conversion process with an example. List the names of other ADCs. (10)
- 6) Draw the functional diagram of 555 timer and explain its operation. Explain the function of following pin numbers 4, 5, 6 and 7. (10)
- A)
- B) Draw the functional diagram of VCO (IC 566) and explain its operation. Derive the expression for frequency of oscillation. (10)
- 7) What is PLL? Give the applications of PLL. Draw the block diagram of IC565 & explain the working of each block. (10)
- A)
- B) Draw the circuit diagram of series voltage regulator and adjustable regulator. Explain its operation and derive the output voltage expressions. (10)
- 8) Explain the following with circuit diagram, waveforms and expressions: (20)
- i) Anti-Log amplifier
 - ii) Precision Half wave rectifier
 - iii) Inverting Schmitt trigger
 - iv) Analog Divider

-----End-----