



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent Institution of MAHE, Manipal)

III SEMESTER B.TECH (ELECTRICAL & ELECTRONICS)

END SEMESTER EXAMINATIONS, NOVEMBER 2018

SUBJECT: ELECTRICAL CIRCUIT ANALYSIS [ELE 2101]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 20 November 2018

Max. Marks: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A. For the network shown in Fig 1A, determine the value of R_L for maximum power transfer and also, find the value of maximum power transferred. (04)
- 1B. In the network of Fig 1B, find the current through $j3 \Omega$ inductor using Superposition theorem. (04)
- 1C. In the circuit of Fig 1C, find the current through 3Ω resistor and hence verify Reciprocity theorem. (02)
- 2A. In the circuit of fig 2A, draw the locus of total current if X_C varies from zero to infinity. Also, determine (i) currents at UPF (ii) values of X_C at resonance. (04)
- 2B. The first derivative of the function $f(t)$ is shown in Fig 2B. Sketch the function $f(t)$. Also, determine the value of K such that $\int_{-\infty}^{+\infty} f(t)dt = 0$. (03)
- 2C. Resolve the waveform given in Fig 2C into its even and odd components. (03)
- 3A. In the circuit of Fig 3A, switch is moved from position A to B at $t = 0$. Find $v_{C1}(0^+)$, $v_{C2}(0^+)$ and $v_R(0^+)$. (02)
- 3B. In the network of Fig 3B, the switch is moved from position A to B at $t = 0$ after attaining steady state in position A. Find an expression for the voltage across the capacitor for $t > 0$ using time domain analysis. (04)
- 3C. In the network of Fig 3C, switch S_1 is closed at $t = 0$ and S_2 is opened at $t = 4$ m-sec. Obtain the expression for the current through the inductor for $t > 4$ m-sec using time domain analysis. (04)
- 4A. In the network of Fig 4A, switch was in position A for a long time. At $t = 0$, switch is moved to position B. Draw the transformed network and hence write the mesh equations. Given $e(t) = e^{-t} \sin 10t$. (04)
- 4B. A series RL circuit with $R = 3 \Omega$ and $L = 1$ H is excited by a voltage $v(t) = 2e^{-4t} u(t)$. Determine the expression for current through the inductor for $t > 0$ using Laplace transform technique. (02)
- 4C. The current response of a network is given by

$$I(s) = \frac{10(s^2 + 3s + 2)}{(s+3)(s^2 + 2s + 5)}$$
Determine $i(t)$ using pole-zero diagram method. (04)

- 5A. For the network shown in Fig 5A, determine the hybrid parameters. (04)
- 5B. The networks shown in Fig 5B(i) and 5B(ii) are connected in parallel. Determine the overall Y parameters. (04)
- 5C. A two port network is defined by the parameters: $Y_{21} = 6$, $Y_{22} = 8$, $h_{11} = 5$, $h_{12} = 2$. Find the T parameters. (02)

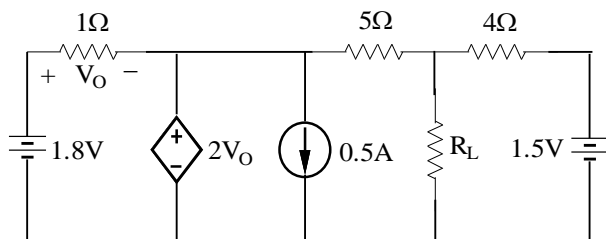


Fig 1A

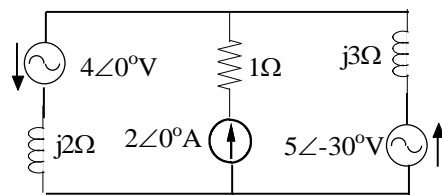


Fig 1B

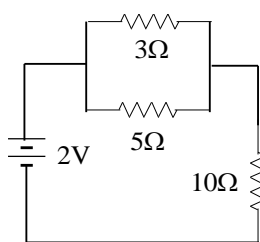


Fig 1C

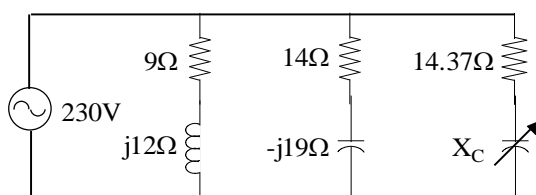


Fig 2A

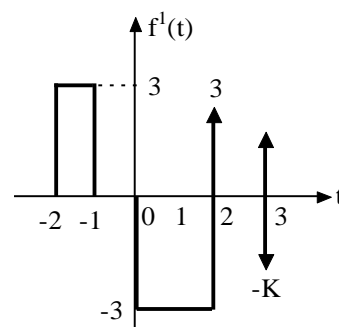


Fig 2B

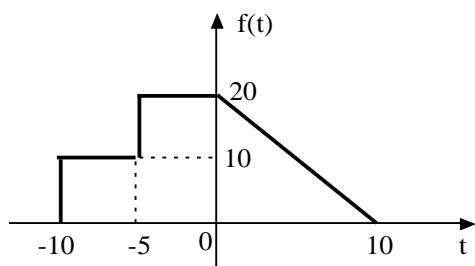


Fig. 2C

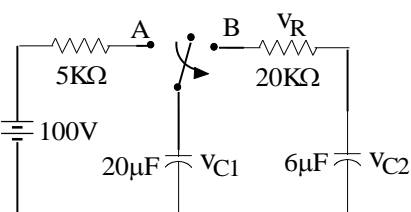


Fig 3A

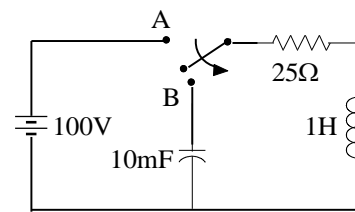


Fig 3B

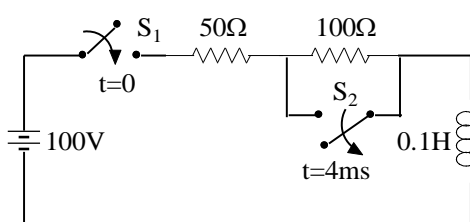


Fig 3C

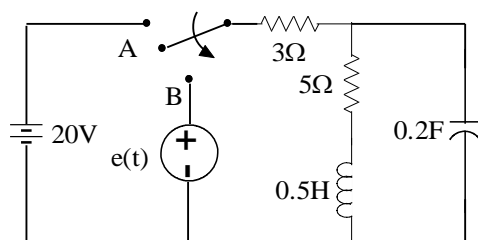


Fig 4A

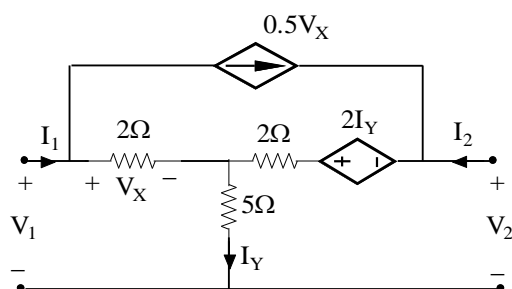


Fig 5A

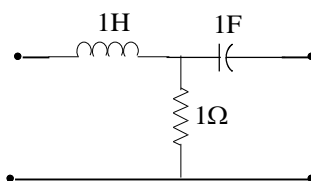


Fig 5B(i)

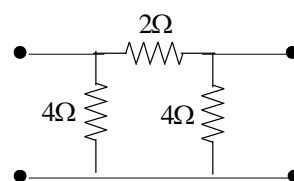


Fig 5B(ii)

---000---