



III SEMESTER B.TECH (ELECTRICAL & ELECTRONICS)

MAKE UP EXAMINATIONS, DECEMBER 2018

SUBJECT: ELECTRICAL CIRCUIT ANALYSIS [ELE 2101]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 22 December 2018

Max. Marks: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A. In the network of Fig 1A, determine the current in the capacitor using Norton's theorem. (04)
- 1B. In the circuit of Fig 1B, find the parameters of the coil to be connected across A and B for maximum power transfer to the coil. (02)
- 1C. In the network of Fig 1C, find the voltage across 3Ω resistor using Superposition theorem. (04)
- 2A. For the locus diagram shown in Fig 2A, draw the circuit configuration and write all the element values. Also, find the value of variable at unity power factor. (04)
- 2B. Draw the odd and even components of waveform shown in Fig 2B. (03)
- 2C. Evaluate the following integrals
 - i) $\int_{-\infty}^{\infty} \delta(t-5)\{u(t-2) + (t-4)u(t-4)\}dt$
 - ii) $\int_{-\infty}^{\infty} \cos t \{\delta(t-\pi) + \delta'(t-\frac{\pi}{2}) + \delta''(t-\frac{\pi}{4})\}dt$
 - iii) $\int_{-\infty}^{\infty} e^{-jnt}\{A\delta(t) - 2A\delta'(t-\pi)\}dt$ (03)
- 3A. In the circuit of Fig 3A, switch is changed from A to B at $t = 0$, after attaining steady state at A. Determine i_L , i_C , $\frac{di_L}{dt}$ and $\frac{di_C}{dt}$ at $t = 0^+$. (03)
- 3B. A series RLC circuit with $R = 5\Omega$, $L = 0.2H$ and $C = 0.1F$ is excited by a voltage of $v(t) = 15e^{-5t}$ at $t = 0$, the initial charge on the capacitor being 1 coulomb before $t = 0$. Determine the current in the circuit at $t = 0.5$ sec. Use time domain analysis. (04)
- 3C. The network shown in Fig 3C is in steady state with the switch in position A. The switch is changed from A to B at $t = 0$. The current response of the circuit is $i(t) = 4e^{-0.4t}u(t)$. Determine the values of R and C. (03)
- 4A. A series RC circuit with $R = 2\Omega$ and $C = 0.5F$ is excited by a voltage $e(t) = 2u(t) + 3r(t-1) - 3r(t-4) - 11u(t-4)$. Determine the current response of the circuit using laplace transform method. (03)
- 4B. In the network of Fig 4B, switch is changed from A to B at $t = 0$, the steady state being achieved with switch at A before $t=0$. Determine the expression for current through the inductor using laplace transform method. (04)

- 4C. Draw the pole – zero diagram of the function below. Hence find $i(t)$.

$$I(s) = \frac{5(s^2 + s)}{(s + 2)(s^2 + 2s + 10)}$$

(03)

- 5A. Find the T parameters of the network shown in Fig 5A

(04)

- 5B. Two similar 2 port networks, each as in Fig 5B, are connected in parallel. Find the overall Z parameters.

(04)

- 5C. Given the h parameters of a network, deduce the values of Y parameters in terms of h parameters.

(02)

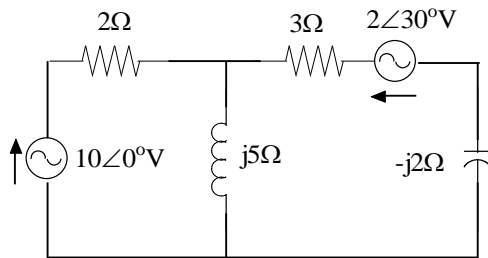


Fig 1A

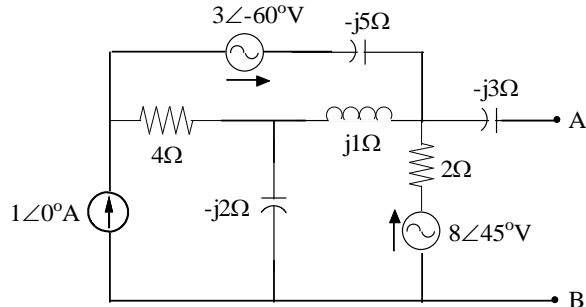


Fig 1B

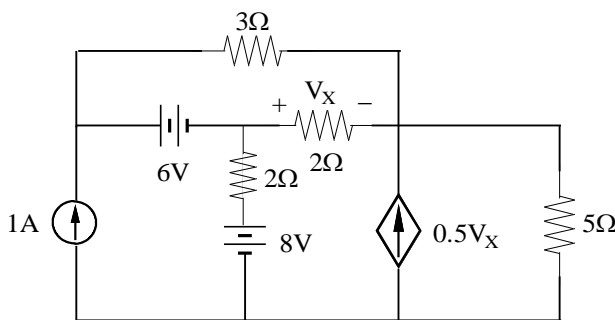


Fig 1C

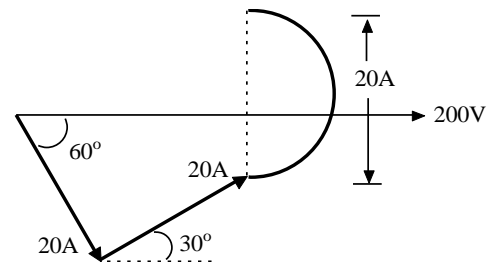


Fig. 2A

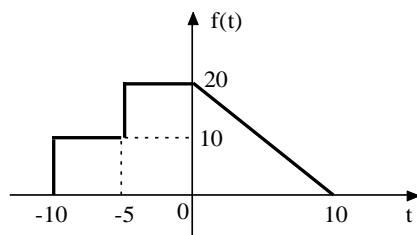


Fig 2B

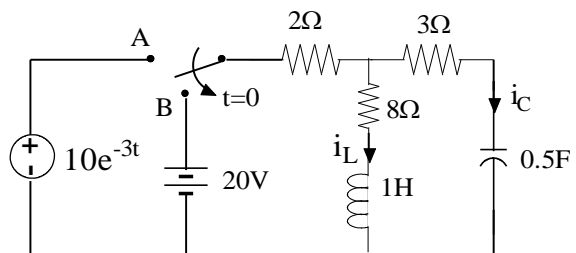


Fig 3A

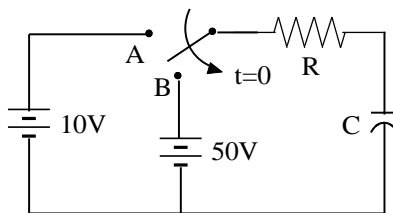


Fig 3C

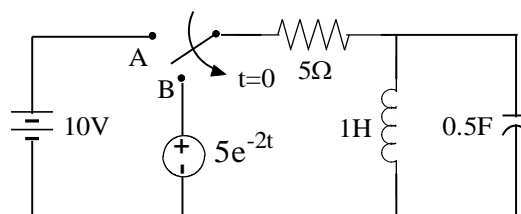


Fig 4B

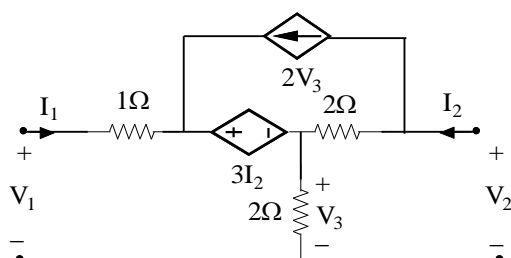


Fig 5A

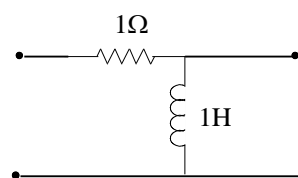


Fig 5B