MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL (A constituent unit of MAHE, Manipal)

## THIRD SEMESTER B.TECH. (E & C) DEGREE END SEMESTER EXAMINATION DECEMBER 2018/JANUARY 2019 SUBJECT: NETWORK ANALYSIS (ECE -2103)

## TIME: 3 HOURS

MAX. MARKS: 50

## **Instructions to candidates**

- Answer **ALL** questions.
- Missing data may be suitably assumed.
- Do not use Laplace Transforms unless specified.
- 1A. In the network shown in Figure 1A, find the current through  $10\Omega$  resistor using Norton's theorem.
- 1B. Write the loop equations for the coupled network shown in Figure 1B.
- 1C. Find an equivalent resistance between A and B in the network Figure 1C.

(4+3+3)

2A. For the circuit shown in Figure 2A, the switch is closed at t=0. Find

a) 
$$i_1(0^+)$$
 and  $i_2(0^+)$ 

b) 
$$\frac{di_1(0^+)}{dt}$$
 and  $\frac{di_2(0^+)}{dt}$ 

- c)  $i_1(\infty)$  and  $i_2(\infty)$
- 2B. In the network shown in Figure 2B, the switch is moved from position 1 to 2 at t = 0, after reaching the steady state. Determine the expression for current i(t).
- 2C. In the network shown in Figure 2C, the switch is closed at t = 0. Determine v(t), assuming  $v_c(0) = 0.5V$ .

(4+3+3)

- 3A. A symmetrical square wave whose average value is zero has a peak-to-peak amplitude of 20V and a period of 2µs. This waveform is applied to a low pass RC circuit whose upper 3dB frequency is  $\frac{1}{2\pi}MHz$ . Calculate and sketch the steady state output waveform. What is the peak-to-peak output amplitude?
- 3B. A limited ramp shown in Figure 3B is applied to an RC differentiating circuit. Draw to scale the output waveform for the following cases:

(i) T = RC (ii) T = 0.2 RC (ii) T = 5 RC

3C. With the help of circuit and relevant expressions explain how high pass RC circuit can be used as a differentiator.

(4+3+3)

4A. A series *RC* circuit, with  $R = 10 \Omega$  and  $C = 4 \mu$ F, has an initial charge  $Q_0 = 800 \mu$ C on the capacitor at the time the switch is closed, which results in applying a constant-voltage source V = 100 V. Find the resulting current transient if (i)  $Q_0$  is of the same polarity, and (ii)  $Q_0$  is of the opposite polarity. Use **Laplace Transform.** 

4B. In the series RLC circuit shown in Figure 4B, there is no initial charge on the capacitor. If the switch is closed at t = 0, determine the resulting current using **Laplace Transform**.

4C. Find y(t), if 
$$Y(s) = \frac{s-1}{s^2+4s+20}$$
 (4+3+3)

- 5A. Find the open circuit impedance parameters for the network shown in Figure 5A.
- 5B. For the network shown in Figure 5B, find  $Z_{11}(s)$  and  $G_{12}(s)$ .
- 5C. Express z parameters in terms of ABCD parameters.

(4+3+3)







Figure. 2B



Figure. 3B



Figure. 2C



Figure. 4B





Figure. 5B