Reg. No.											
----------	--	--	--	--	--	--	--	--	--	--	--



III SEMESTER B.TECH. (MECHATRONICS ENGINEERING) END SEMESTER EXAMINATIONS

LINEAR INTEGRATED CIRCUITS AND APPLICATIONS [MTE 2104]

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ✤ Answer ALL the questions.
- Data not provided may be suitably assumed.
- 1A. With necessary mathematical expression, elucidate how IC 555 timer can be utilized to design a circuit of 50% duty cycle.
- 1B. Explain the working principle of the fastest Analog to Digital Converter to get a 3-bit digital word as the output.
- 1C. Design a Phase Locked Loop circuit using IC 565 to get free running frequency 03 of 4.5kHz; lock range of 2 kHz and capture range of 100Hz having the supply voltage of ±10V.
- 2A Determine the output voltage (Vout), if the op-amp in Fig. Q2A is ideal. 02



- **2B** Design a wide band reject filter of lower cut-off frequency f_h = 2kHz, f_l = 400Hz **04** and pass-band gain is 2. Also, draw the graph defining pass-band region and stop-band region.
- 2C Design 4-bit R-2R ladder type DAC. Compute the full-scale voltage and % 04 resolution of a 5-bit DAC.
- 3A Explain the working of Phase Locked Loop circuit using its functional block 03 diagram, and also explain about the three stages of its operation.

3B Design an inverting adder circuit using op-amp to get the output expression given **03** below. V₁, V₂, V₃ are inputs. Assume $R_F=10k\Omega$.

$$V_0 = -(0.5V_1 - V_2 + 10V_3)$$

3C For the IC 566 Voltage Controlled Oscillator shown in Fig. Q3C, $V_{CC} = 10V$, $R_T = 10k\Omega$, $R_1=1.2k\Omega$, $R_2=10k\Omega$. Compute: a) Frequency output (f_o) b) Voltage to frequency conversion factor c) Variation in f_o if modulation input voltage, V_c is varied between 7.7V and 9.5V, d) List out any two application of the circuit



Fig. Q3C

- 4A With the help of necessary circuit diagrams, elucidate the advantages of practical 03 integrator over simple integrator and also, explain their frequency responses.
- **4B** Describe how 78xx fixed series can be used as Adjustable regulator and derive **04** output voltage equation. Using IC 7805, design a current source to deliver 0.15 A to a 20 Ω resistor, 5 Watt load. (Quiscent current,I_Q=4.2mA for IC 7805). Also, calculate V_{in} if drop-out voltage, V_D=2V.
- 4C Construct an electronic circuit using op-amp which can be utilized to sample the incoming analog signal and holds its value at a stable level for a particular period of time.
- 5A Explain the operation of Shunt voltage regulator using functional block diagram. 04State the difference between Load Regulation and Line Regulation.
- **5B** Design a circuit using op-amps to solve the following differential equation: $K_1 \frac{dV1}{dt} + K_2 V_1 - V_2 = 0$ **03**
- 5C In an electronics laboratory, the measuring instrument is capable of measuring voltages only, but the output of the photodiode sensor is a current which changes proportional to the light intensity. Explain how op-amp can be used to convert the output current of photodiode into voltage.