

**I SEMESTER M.TECH (POWER ELECTRONICS & DRIVES)****END SEMESTER EXAMINATIONS, NOVEMBER 2018****SUBJECT: APPLICATION OF POWER ELECTRONICS IN POWER SYSTEMS [ELE 5122]**

REVISED CREDIT SYSTEM

Time: 3 Hours**Date: 22, November 2018****Max. Marks: 50****Instructions to Candidates:**

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A.** What are components of HVDC system and explain about each? (02)
- 1B.** What are the different HVDC transmission links possible and explain about each configuration? (03)
- 1C.** What is the role of power electronic converters in a power system with distributed energy resources such as photovoltaic, wind energy conversion systems and energy storage devices? (03)
- 1D.** What are the differences between current source converter and voltage source converter? (02)
- 2A.** Describe the working of 6-pulse converter with a neat circuit diagram. Also determine its output voltage V_d in terms of valve firing angle of α . (03)
- 2B.** Prove that for a loss less HVDC converter $\cos \phi = \cos \alpha$ (α is valve firing angle, $\cos \phi$ is power factor) and comment on limitations of α . (02)
- 2C.** Derive the relation for the output voltage of a 6-pulse converter with a valve firing angle of α and overlap angle ($u < 60^\circ$). (05)
- 3A.** Derive the equivalent circuit model for a two terminal HVDC system in terms of valve firing angle α , extinction angle γ , commutation resistance R_C and line resistance R_L . (04)
- 3B.** What are the different Control strategies used in HVDC and explain about them with proper characteristics? (03)
- 3C.** A monopolar HVDC link has one bridge at each terminal. The parameters of the link are: $\alpha_{\min} = 5^\circ$, $\gamma_{\min} = 18^\circ$, $R_L = 5\Omega$, $R_{cr} = 10\Omega$, $R_{ci} = 12\Omega$. $V_{doi} = 117.5\text{kV}$, I_{Ref} at the rectifier is 1kA, I_{Ref} at the inverter is 900A.
- i. If, $V_{dor} = 120\text{kV}$, Calculate $I_d, \alpha, \gamma, P_r, Q_r$
- ii. Repeat (i) if $V_{dor} = 115\text{kV}$ (03)

- 4A.** What are the different types of FACTS controllers used in power system and draw their circuit models? **(03)**
- 4B.** What are the different types of static VAR compensators (SVC) and explain about their working principle? **(05)**
- 4C.** What are the general characteristics of SVC? **(02)**
- 5A.** What are the possible benefits from FACTS devices? **(02)**
- 5B.** Explain about the 12-pulse Thyristor controlled reactor (TCR) with a circuit diagram. **(02)**
- 5C.** What is the importance of Thyristor controlled transformer (TCT) in an SVC and mention its advantages over TCR? **(02)**
- 5D.** Explain about the working of STATCOM with proper circuit diagram and compare STATCOM with SVC. **(04)**