



**I SEMESTER M.TECH. (INDUSTRIAL AUTOMATION AND ROBOTICS)**  
**END SEMESTER EXAMINATIONS, NOV-DEC 2018**

**SUBJECT: ANALOG AND DIGITAL ELECTRONICS [MTE 5131]**  
 24/11/2018

Time: 3 Hours

MAX. MARKS: 50


**Instructions to Candidates:**

- ❖ Answer **ALL** the questions.
- ❖ Data not provided may be suitably assumed

- 1A.** Compare an ideal OP-AMP with a practical OP-AMP in terms of gain, input impedance & bandwidth, and formulate the overall gain of an inverting amplifier. **03**
- 1B.** Subtract  $(6)_{10}$  from  $(5)_{10}$  using 2's complement method. **03**
- 1C.** Design a negative edge triggered 4-bit asynchronous up Binary Counter. **04**
- 2A.** Design a 4-bit Binary to BCD code converter. **04**
- 2B.** Construct a FM demodulator/detector using phase locked loop. **06**
- 3A.** Design a combinational logic circuit for a mobile robot which follows a black line. The robot is embedded with four infrared sensors, where first & fourth sensors are placed to sense outside black line and second & third sensors are placed to detect black line for achieving forward motion. If the condition is not satisfied then the robot should stop. **05**
- 3B.** Discuss the data movement in a 4-bit bidirectional shift register using state timing diagrams. (Take data to be loaded as 1011). **05**
- 4A.** Design the circuits using OP-AMP to perform the following operations: **05**
- a.  $V_{out} = \frac{K_B T}{-q} [\ln(V_i) - \ln(RI_a)]$
- b.  $V_{out} = -RI_a e^{\frac{-qV_i}{K_B T}}$

- 4B.** Add the following binary numbers and represent the result in 2's complement form: **05**
- a. 10101110 and 100111
  - b. 10010010 and 110011
  - c. 11001001 and 111110

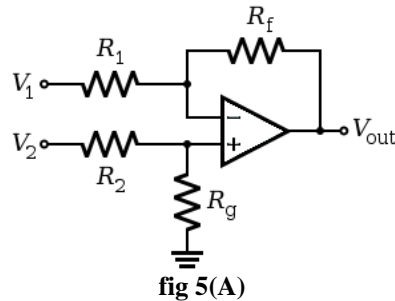- 5A.** In an operational amplifier as shown in **Fig 5(A)**, if  $V_1=10V$ ,  $V_2=20V$ ,  $R_1=R_2=R_g=1Kohm$  and  $R_f=1Kohm$  then calculate the feedback current. **02**



- 5B.** Explain the cyclic codes and recall the applications of cyclic codes in error detection & correction. **03**
- 5C.** Design a serial transfer logic diagram and explain the implementation of 4-bit register to 4-bit register serial data transfer. **05**