

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)

I SEMESTER M.TECH. (INDUSTRIAL AUTOMATION AND ROBOTICS)

END SEMESTER EXAMINATIONS, NOV-DEC2018

SUBJECT: ANALOG AND DIGITAL ELECTRONICS [MTE 5131]

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Data not provided may be suitably assumed

- 1A.** Design a circuit using OP-AMP for diode match finder application. **03**
- 1B.** Design a circuit with an adjustable feedback gain to record 4 musical instruments in parallel with a singer for a common amplified signal. **03**
- 1C.** Design an 8-bit serial in serial out shift register. **04**
- 2A.** Explain grey codes conversion from BCD and identify the use of gray codes in shaft position encoders. **04**
- 2B.** Design a circuit using timer to generate frequency of 2KHz with 50% duty cycle. **06**
- 3A.** Design a BCD to seven segment driver circuit using active low output decoders. **05**
- 3B.** Design a synchronous 3 bit up-down counter with state timing diagram. **05**
- 4A.** Compare the working principles of rectifier circuit with a clipper circuit for analog input signals using OP-AMP. **05**
- 4B.** Add the following unsigned binary numbers and perform 2's complement: **05**
- a. 11111110 and 101111
 - b. 11010010 and 100011
 - c. 10000001 and 100110

5A. Calculate the voltage gain of the OP AMP as shown in **fig 5(A)**.

02

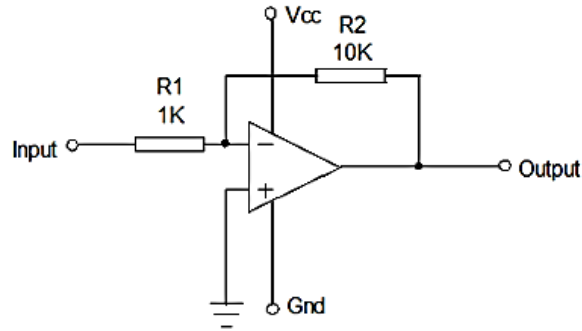


Fig 5(A)

5B. Construct a truth table for 8421-2421 BCD numbers conversion.

03

5C Design a 4 bit parallel in serial out shift register and paraphrase data movement in each clock pulse. (Taking the data flow 1111).

05