

Question Paper

Exam Date & Time: 24-Nov-2018 (10:00 AM - 01:00 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

SCHOOL OF INFORMATION SCIENCES

FIRST SEMESTER MASTER OF ENGINEERING - ME (VLSI DESIGN)

High Level Digital Design [EDA 611]


Marks: 100

Duration: 180 mins.

END SEMESTER DEGREE EXAMINATION NOVEMBER 2018

Answer all the questions.

 - 1) Implement the $F = \sum WXYZ(0, 2, 5, 7, 9, 11, 12, 15)$ logic function using multiplexer (10)
- 2) Design and explain the following with neat diagram (10)
 - a. D-Latch
 - b. D-FlipFlop
 - c. Scan D-FlipFlop
- 3) Design a 1101 sequence detector using Moore Machine (10)
- 4) Design the following (10)
 - a. All 0's Detector
 - b. All 1's Detector
 - c. Equality Comparator
- 5) Explain Carry Select Adder with neat diagram (10)
- 6) For the given circuit, determine the delay of the longest path. (10)



- 7) Design a Synchronous FIFO (10)
- 8) Explain the following (10)
 - a. Single Ended I/O

b. Differential Ended I/O

9) Brief explain the Split & retry operation (10)

10) Design Real Time Clock with following features (10)

a. Display - Hr : Min : Sec

b. Clock freq 500 KHz

-----End-----