

**VII SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)****MAKE-UP EXAMINATIONS, DECEMBER 2018****SUBJECT: MODERN POWER CONVERTERS [ELE 4010]**

REVISED CREDIT SYSTEM

**Time: 3 Hours****Date: 27, December 2018****Max. Marks: 50****Instructions to Candidates:**

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A. A non-ideal buck converter is modeled by including MOSFET on state resistance  $R_{on}$ , an inductor resistance  $R_L$  and a diode voltage drop  $V_D$ . Derive the expression for  $V_o/V_s$  that includes the above effects. (04)
- 1B. Find Duty cycle and Efficiency of a non-ideal buck converter. Given specifications:  $V_s=30V$ ,  $V_o=15V$ ,  $R_o=5\Omega$ ,  $R_{on}=0.016\Omega$ ,  $R_L=0.06\Omega$ ,  $V_D=0.9V$ . (02)
- 1C. Derive a dc transformer model of a non-ideal buck boost converter having inductor winding resistance  $R_L$  and MOSFET on state resistance  $R_{on}$ . All other losses can be ignored. (04)
- 2A. Draw the circuit schematic of a Cuk converter and derive an expression for output voltage  $V_o$ . (Apply inductor volt sec balance and capacitor charge sec balance.) (02)
- 2B. Design a Cuk converter for the following specifications:  $V_s=45V$ ,  $V_o=-15V$ ,  $P_o=25W$ ,  $f_s=150kHz$ .
  - (a) Maximum inductor ripple currents should not exceed 10% of its average value.
  - (b) Maximum voltage ripple across  $C_1$  should not exceed 5% of its average value.
  - (c) Maximum output voltage ripple is less than 1%. (04)
- 2C. Draw the circuit schematic of a SEPIC converter and derive the expressions for output voltage  $V_o$ , inductors  $L_1$  and  $L_2$ , Capacitors  $C_1$  and  $C_2$ . (Apply inductor volt-sec balance and capacitor charge sec balance) (04)
- 3A. With a neat circuit schematic of a flyback DC-DC converter, draw suitable waveforms to develop expressions for calculating average load voltage, the necessary filter circuit to be used. (04)
- 3B. A forward converter has the following parameters  $V_s=100V$ ,  $N_1/N_2 = N_1/N_3=1$ ,  $L_m=1mH$ ,  $L_x=70\mu H$ ,  $R=20\Omega$ ,  $C=33\mu F$  and  $D=0.35$ . The switching frequency is  $150kHz$ . Determine (i) the output voltage and output voltage ripple (ii) the average, maximum and minimum values of current in  $L_x$ . (04)
- 3C. With suitable circuit diagram and waveforms of a Push-Pull dc-dc converter, deduce an expression for the output voltage. (02)
- 4A. Draw the circuit schematic a SLR dc-dc converter. Also sketch waveforms of inductor current and capacitor voltage of the tank circuit for  $\omega_s < \omega_o$ . (03)

- 4B.** A series resonant dc dc converter has the following parameters:  $V_s=24V$ ,  $L_r=1.2\mu H$ ,  $C_r=12nF$ ,  $f_s=1.5MHz$  and  $R_o=5\Omega$ . Determine the output voltage. **(03)**
- 4C.** A parallel resonant dc-dc converter supplying a resistive load of  $10\Omega$  from a source voltage of  $100V$ . The switching frequency is 20% excess of the resonant frequency of  $100\text{ KHz}$ , and characteristic impedance  $Z_o = 5\Omega$ . Select suitable values of  $L_r$  and  $C_r$  for the converter and hence determine the output voltage. **(04)**
- 5A.** ZCS converter has the following data:  $V_s=25V$ ,  $V_o=12V$ ,  $I_o=1A$ ,  $Z_o=12\Omega$ ,  $f_s=200kHz$ . Determine time interval for each mode. (Assume  $f_s=0.4f_o$ ). **(04)**
- 5B.** Make a comparison between ZCS and ZVS switching schemes **(02)**
- 5C.** Discuss the steps involved in developing the small signal model of a Buck converter using state space averaging technique **(04)**