Reg. No.



## MANIPAL INSTITUTE OF TECHNOLOGY MANIPAL

(A constituent Institution of MAHE, Manipal)

## VII SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING) END SEMESTER EXAMINATIONS, DECEMBER 2018

## SUBJECT: SOLID STATE DRIVES [ELE 4011]

REVISED CREDIT SYSTEM

Time: 3 Hours		Date: 01, December 2018	Max. Marks: 50
Instructions to Candidates:			
	<ul> <li>Answer ALL the question</li> </ul>	ons.	
	<ul> <li>Missing data may be sui</li> </ul>	tably assumed.	
1A.	What are the components of	load torque? How they are mode	ed? (03)
1B.	Explain the functions of a power modulator? What are the main factors which decide the choice of electrical drive for a given application?		
1C.	In the mechanism shown below Fig. 1C motor drives the winch drum through a reduction gear with a gear tooth ratio of 0.1. The friction torque at winch shaft is 15N-m and at motor shaft to 10 N-m, motor speed is 1500 rpm. Calculate the equivalent moment of inertia of the drive referred to motor shaft and motor torque if gears have an efficiency of 90%.		
		Gear Box	
	Motor ωm J <sub>m</sub> = 0.5Kg-m <sup>2</sup>		Cable Drum

0.5Kg-m<sup>2</sup>  $J_g=0.15 \text{ Kg.m}^2$ Referred to  $\omega_m$  v Load500Kg

Fig.1C

(03)

**2A.** With relevant waveforms and triggering sequence, explain Singal phase fully controlled rectifier feeding a separately excited DC motor operating in controlled freewheeling motoring mode with dis-continuous conduction, when  $\alpha = 60$ . Derive the expression for the average voltage developed across the armature. (05)

ELE 4011

3A. 4kW, 1000rpm 230V, 20 A dc motor has an armature resistance and inductance of 1.4  $\Omega$  and 16.5mH respectively. The motor is fed by a three phase fully controlled rectifier with an AC source voltage of 170.3 60 Hz. Find the critical torque. Draw load voltage and current waveform for a firing angle of 60° when the motor develops torque of 9 N-m. (04) 3B. With relevant waveforms and triggering sequence, explain Three phase fully controlled rectifier feeding a separately excited DC motor armature operating in motoring mode with continuous conduction. Derive also the expression for the average voltage developed across the armature. (04) 3C. Discuss the effect of armature current ripple on the performance of a DC motor. (02) 4A. A 220V,1500rpm,11.6A separately excited motor is controlled by a single phase fully controlled rectifier with an AC source voltage source of 230V,50Hz enough filter inductance is 28.36mH, and armature resistance is  $=2\Omega$  calculate the motor torques for the fallowing firing angle is 150° and speed is -640 rpm. (05) 4B. Describe the working principle of direct Field orientation control of induction motor with the help of its neat block diagram. Mention its advantages. (05) 5A. Explain the principle of rotor resistance control. Find the effective value of resistance included when static resistance control scheme is used for speed control of wound rotor induction motors. (03) Discuss the theoritical principle of slip energy recovery. What are its limitations? Explain any 5B. (04) two converter options for supersynchronous speed control with the help of circuir diagram. 5C.

A separately excited dc motor is fed from 200 V, 15 Amp, dc supply through a chopper

operating at 400Hz the load torque is 25 N-m at a speed of 1000rpm. The motor has armature resistance =  $0.2\Omega$  armature inductance is 2mH. Neglecting all motor and chopper losses. calculate (a) The minimum and maximum values of armature current and armature current

2**B**.

excursion.

With a block schematic explain how power factor control can be achieved statically in synchronous machine. (03)

(05)