



SEVENTH SEMESTER B.TECH. (E & C) DEGREE END SEMESTER EXAMINATION
DECEMBER 2018

SUBJECT: ANALOG AND MIXED SIGNAL DESIGN (ECE - 4013)

TIME: 3 HOURS

MAX. MARKS: 50

Instructions to candidates

- Answer **ALL** questions.
- Missing data may be suitably assumed.

- 1A. Design a RLC band-pass biquad using active transconductor blocks with a Q of 10 and a cut-off frequency of 1.59 MHz. Give comments about sensitivity and tenability.
- 1B. Discuss the merits and demerits of fully differential design in mixed signal design. Illustrate the realization of fully differential Gm-C integrator circuit.
- 1C. With neat diagram explain compensation of finite Bandwidth effects in Operational Trans conductance amplifiers.
- (4+3+3)
- 2A. Discuss the design methods and layout guidelines employed in Analog and Mixed-Signal Circuit Design with respect to following:
 [i] Floor Planning [ii] Power supply and grounding issues [iii] Fully Differential Design
- 2B. With neat diagram of Analog design octagon explain trade-offs and challenges present in the design of high performance amplifiers.
- (5+5)
- 3A. Design a current sink using $V_{DD} = -V_{SS} = 2.5V$ to sink a current of $10 \mu A$. Using the $10 \mu A$ n-channel reference, design three current sources of values $10 \mu A$, $20 \mu A$ and $50 \mu A$. Estimate the variation in I_o for the same current mirror for V_{DD} changing from 2.4 to 2.6V. Assume $L=5 \mu m$, $K_n=50 \mu A/V^2$, $\lambda=0.06/V$, $V_{thn}=0.83 V$, $V_{GS}=1.2V$.
- 3B. Give the general block diagram of Tow-Thomas biquad. Design a Gm-C Low pass biquad for a pole frequency of 10 MHz and Q_p of 10 using i) Tow Thomas structure ii) Distributive feedback structure. Compare both structures
- (4+6)
- 4A. Design a 3 bit charge scaling DAC and determine the value of the output voltage for $D_2 D_1 D_0 = 010$ and 101 . Assume $V_{REF}=5V$ and $C=0.5pF$. What is the drawback of this converter and how is it overcome?
- 4B. Draw the circuit diagram of a sinusoidal oscillator employing two OTA's and 3 capacitors. Write the expression for frequency of operation.
- 4C. Give the internal circuit of CMOS Operational Trans conductance amplifier and explain the OTA performance parameters.

(4+3+3)

- 5A. Discuss the differences between Nyquist rate ADC's and Oversampling ADC's. Sketch and explain the block diagram of first order sigma delta modulator. Use a time discrete integrator with the transfer function $H(z) = 1/Z - 1$.
- 5B. Give OTA implementation of:
- i) Floating Inductance
 - ii) resistor in a differential form.

Write the equivalent expression for inductance and resistance.

(5+5)