



SECOND SEMESTER B.TECH. (E & C) DEGREE END SEMESTER EXAMINATION

JUNE 2019

SUBJECT: BASIC ELECTRONICS (ECE - 1051)

TIME: 3 HOURS

MAX. MARKS: 50

Instructions to candidates

- Answer **ALL** questions.
- Missing data may be suitably assumed.

- 1A. Draw the self -bias circuit using n-p-n transistor. If $R_1=10k\Omega$, $R_2=1k\Omega$, $V_{CC}=15V$, $I_C=3.12mA$, $V_{BE}=0.7V$ and $\beta=100$, Calculate i) R_E ii) Base voltage V_B
- 1B. Draw the input and output characteristics of n-p-n transistor in CE configuration indicating the different regions of operation. Also, explain the Early effect.
- 1C. With neat diagrams explain how transistor is used as LED driver and inverter. (4+3+3)
- 2A. A Zener voltage regulator needs to maintain an output voltage of 20 V across a $1k\Omega$ load with an input that will vary between 30 and 50 V. Determine the proper value of R_S and the maximum current I_{ZMax}
- 2B. With neat input and output waveforms draw the circuit diagram of full wave bridge rectifier and explain the operation.
- 2C. Realize each of the following equations using single OPAMP.
(i) $V_O = 2V_1$ (ii) $V_O = -(5V_1 + 2V_2)$ where V_1 and V_2 are the inputs. (4+3+3)
- 3A. Simplify the following using K-Map and implement using only NAND gates.
 $F(A, B, C, D) = \sum m(0, 2, 5, 10, 11, 15) + \sum d(7, 8, 14)$
- 3B. Realize a 3 bit asynchronous up counter using -ve edge triggered JK flip-flops. Also draw the timing diagram of each flip-flop output.
- 3C. Write down the truth table of a full adder circuit. Obtain the expression for Sum and Carry_{out} of a full adder. Implement a full adder using two half adders and an additional gate. (4+3+3)
- 4A. Consider a FM wave given by the expression $V = 10 \cos[2\pi 10^6 t + 0.1 \sin 10^3 \pi t]$ with frequency sensitivity 5Hz/volt. Find the carrier frequency, modulation index, maximum frequency deviation, bandwidth, modulating frequency and amplitude.
- 4B. Derive an expression for FM signal in time domain. Mention any four differences between AM and FM.
- 4C. Consider an AM modulated wave with the message signal $m(t) = 10\cos(2\pi 50t)$, carrier signal $c(t) = 50\cos(2\pi 10^5 t)$. Find modulation index, sideband frequencies, bandwidth, total power delivered if $R_L=1K\Omega$, amplitude of each sideband component. (4+3+3)

- 5A. With a neat block diagram explain the function of each block in a digital communication system.
- 5B. Highlight the function of three basic multiple access methods.
- 5C. Highlight the function of following terms with reference to electronic communication systems:
i) BTS ii) NSS iii) HLR

(4+3+3)