ANIPAL INSTITUTE OF TECHNOLOGY

Reg. No.

(A constituent unit of MAHE, Manipal)

FOURTH SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.) END SEMESTER DEGREE EXAMINATION, JUNE - 2019

SUBJECT: ANALOG SYSTEM DESIGN [ICE 2204]

TIME: 3 HOURS

Instructions to candidates : Answer ALL questions and missing data may be suitably assumed.

- 1A Design an OpAmp circuit for amplifying a 5mV output from a sensor to 3V.
- 1B For the circuit in Fig.Q1B, obtain the output voltage and find the CMRR considering $(R_3/R_1)\neq (R_4/R_2)$.
- 1C Compare and contrast the working, design and applications of a V to I converter with regard to an I to V converter.
- 2A In the lossy integrator of Fig.Q2A, if Rf=100K Ω , C= 10nF, R=10k Ω , determine the response for a 1V peak sine wave.
- 2B Discuss on the working of any 3 different clamper circuits using OpAmp.
- 2C Design a practical differentiator circuit using OpAmp. How does it differ from a basic differentiator?
- 3A Determine the quality factor of a band pass filter with f_1 =400Hz and f_h = 2kHz.
- 3B Derive the design equations for a Weinbridge Oscillator oscillator.
- 3C Design a second order low pass filter with a higher cut off frequency of 1KHz. Draw the frequency response of the filter.
- 4A What is meant by a zero crossing detector? Describe with a circuit.
- 4B Discuss on the internal architecture of a 555 timer.
- 4C Design an OpAmp square wave generator for generating a signal of 1KHz frequency.
- 5A The basic step of a 9-bit DAC is 10.3mV. If 000000000 represents 0V, what output does 101101111 give?
- 5B With neat circuit diagram, explain the working of a D/A convertor with R-2R ladder circuit.
- 5C Discuss on the working of a flash type ADC.



MAX. MARKS: 50

(2+3+5)

(2+4+4)

(2+3+5)

(2+4+4)

(2+4+4)