MANIPAL INSTITUTE OF TECHNOLOGY

(A constituent unit of MAHE, Manipal)

FOURTH SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.) END SEMESTER DEGREE EXAMINATION, APRIL/MAY - 2019

SUBJECT: ANALOG SYSTEM DESIGN [ICE 2204]

TIME: 3 HOURS

MAX. MARKS: 50

Instructions to candidates : Answer ALL questions and missing data may be suitably assumed.

- 1A Design a non-inverting amplifier whose gain is variable over the range 0.5 to 5 by means of a 100k pot.
- 1B Draw the circuit of an instrumentation amplifier and derive the output equation. List out the advantages of the instrumentation amplifier over normal amplifier.
- 1C Find Vn, Vp and Vo in the circuit shown in Fig.Q1C if $i_s=1mA$. Find the resistance R, that when connected in parallel with the 1mA current source will cause Vo to drop to half the value found in the first case.

(2+4+4)

2A Consider the circuit in Fig.Q2A with ideal OpAmp. The IV characteristics of the diode is described by the relation

 $I = Io\left(e^{\frac{V_T}{V}} - 1\right)$, where V_T=25mV, I₀=1µA and V is the voltage across the diode. For an input voltage of V_i=-1V, find out the output voltage V₀.

- 2B Describe the working of an ideal OpAmp half wave rectifier and differentiate it between a precision diode?
- 2C Compare and contrast the working of a normal OpAmp integrator with a lossy integrator with regard to circuit specifications, frequency response characteristics and cut off frequencies.

(2+3+5)

- 3A Determine the order of a low pass Butterworth filter to provide 40dB attenuation at $\omega/\omega_h = 2$.
- 3B Derive the design equations for an RC Phase shift oscillator.
- 3C Given a bandpass filter with resonant frequency fo of 1000Hz and a bandwidth of 3000Hz, find its quality factor, low cut-off frequency and high cut-off frequency. Draw the frequency response of this filter.

(2+3+5)

- 4A Discuss on the necessary conditions for a circuit to work as an oscillator.
- 4B Describe the working of a Schmitt trigger using OpAmp and obtain the upper and lower threshold voltages.
- 4C Explain the working of a 555 timer as an astable multivibrator. If $R_A = 2.2 \text{ K}\Omega$, $R_B = 3.9 \text{ K}\Omega$ and $C = 0.1 \mu F$. Determine the positive pulse width t_c, negative pulse width t_d and free running frequency f_o.

(2+3+5)

- 5A Design a 555 one shot whose pulse width can be varied anywhere from 1ms to 1s using a $1M\Omega$ pot.
- 5B Illustrate the working of a Successive Approximation type ADC and describe how it converts an analog signal with digital representation as 110101 to a digital output.

5C With a neat circuit diagram, explain the working of a D/A convertor using binary weighted resistors. Discuss its shortcomings.


