



VI SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)
MAKE-UP EXAMINATIONS, JUNE 2019

SUBJECT: MEASUREMENTS & INSTRUMENTATION [ELE 3202]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 12, June 2019

Max. Marks: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.
- ❖ Graph Sheet may be used.

- 1A.** A resistance of approximate value of 50Ω is to be measured by Voltmeter- Ammeter method using a 1A ammeter having a resistance of 2Ω and a voltmeter of 50V with a resistance of 5000Ω .
- a. Calculate the measured and true value of resistance
 - b. Determine the relative error by two circuit combinations. If the reading of the meters are 0.67A and 36.1V, with an accuracy of $\pm 0.5\%FS$, calculate the true value of resistance. (error corresponds to standard deviation) **(03)**
- 1B.** Applying the related fundamentals of electromagnetic wave propagation, determine the shielding effectiveness in dB for a 20 mil thick sheet of copper ($\sigma = 5.8 \times 10^7 \text{ S/m}$) at 1MHz given: (1 mil=0.0254 mm)
- a. An electric source at a distance 1 m from the shield
 - b. A magnetic source at a distance 1 m from the shield **(03)**
- 1C.** In an electrodynamic instrument the total resistance of the voltage coil circuit is $8.2k\Omega$ while the mutual inductance varies from $-173\mu\text{H}$ at zero deflection to $+175\mu\text{H}$ at full scale deflection of 95° . If 100V potential difference is applied across the voltage circuit, current of 3A at a power factor of 0.75 is passed through the current coil. What will be the deflection if the spring constant is $4.63 \times 10^{-6} \text{ N - m/rad}$. **(04)**
- 2A.** An AC Bridge as shown in the **Fig Q2A**, is used to measure an unknown inductance L_x , which has inherent resistance R_x . The bridge parameters are $R_1 = 20k\Omega$; $R_2 = 50k\Omega$; $C_2 = 0.0037\mu\text{F}$. The operating frequency $\omega = 10^5 \text{ rad/sec}$. C_1 is adjustable from 10pF to 150pF and R_4 is adjustable from 0 to $10k\Omega$. Derive expressions for R_x and L_x to show that resistive and reactive balance are independent of each other. Also determine the largest values of R_x and L_x that can be measured with given parameters. **(03)**
- 2B.** With a neat diagram, explain and develop the mathematical model of a potentiometer having a load of resistance R_m . Let the total resistance of the potentiometer be R_p . **(03)**

- 2C. A coaxial capacitor has dimensions $a = 3\text{mm}$, $b = 12\text{mm}$, and a length of 1m . The region between the conducting cylinders contains three different dielectrics: $\epsilon_{R1} = 5$, ($3 < r < 6\text{mm}$); $\epsilon_{R2} = 3$, ($6 < r < 9\text{mm}$) and $\epsilon_{R3} = 1$, ($9 < r < 12\text{mm}$).
- Calculate the overall capacitance 'C'
 - Plot the electric field variation with respect to the radius (E_r v/s r) if $E_{r_{\max}} = 100\text{ V/m}$. **(Use the graph sheet provided)** (04)
- 3A. With a neat diagram, derive the mathematical model of a piezoelectric transducer when connected to an ideal charge amplifier. Further comment on its output variation according to variation in the frequencies of the input signal. (03)
- 3B. Inserting a resistance R_3 in parallel with capacitance C in the high pass filter shown in **Fig. Q3B** turns it into a circuit known as zero-pole circuit that finds applications in control.
- Sketch the modified circuit and derive its mathematical model so as to justify its name.
 - Specify standard component values for a zero frequency of 100 Hz , a pole frequency of 1 KHz and a high frequency gain of 0dB . (03)
- 3C. A dual OPAMP instrumentation amplifier shown in **Fig. Q3C** offers an advantage in that a high CMRR can be obtained via appropriate adjustment of the pot. Derive its mathematical model and prove that:
- $$V_0 = \left(1 + \frac{R_2}{R_1}\right)(V_2 - V_1) \quad (04)$$
- 4A. Consider a 4 bit binary weighted D/A converter having the circuit components defined as $R = 10\text{K}\Omega$; $R_f = 5\text{K}\Omega$ and $V_{ref} = -10\text{V}$. For an input binary word of 1101, determine the following:
- Resolution
 - Input current
 - Output voltage (03)
- 4B. With an appropriate schematic of a 10 bit successive approximation A/D converter employing SAR, obtain the equivalent binary output for an analog voltage input of 0.6 V . Consider the reference voltage to be 1 V . Highlight all the steps involved in this A/D conversion process. (03)
- 4C. With neat diagram, explain the operation of analog signal isolation using the magnetic medium. Highlight the importance of signal modulators as well as signal demodulators in the process. (04)
- 5A. With the help of neat schematic describe the working of R-2R Ladder Network DAC. Prove that for digital input of 0100 equivalent analog voltage is $(-V_s/4)$ with appropriate circuit connections. Assume V_s as reference/source voltage. (03)
- 5B. With a neat diagram, explain the various elements of a Distributed control system (DCS). Also list out the advantages of using DCS for process control. (03)
- 5C. With the help of neat block diagram explain working of a Digital Energy Meter focusing on signal measurement, its conditioning as well as its display. (04)

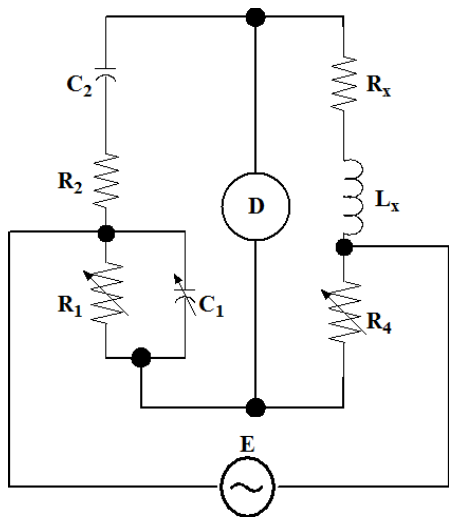


Fig. Q2A

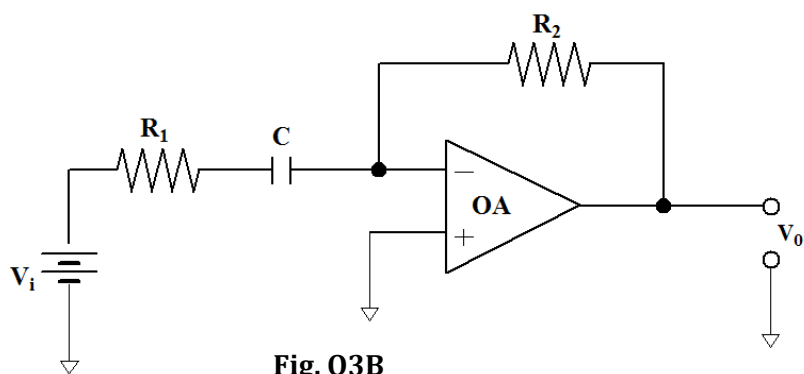


Fig. Q3B

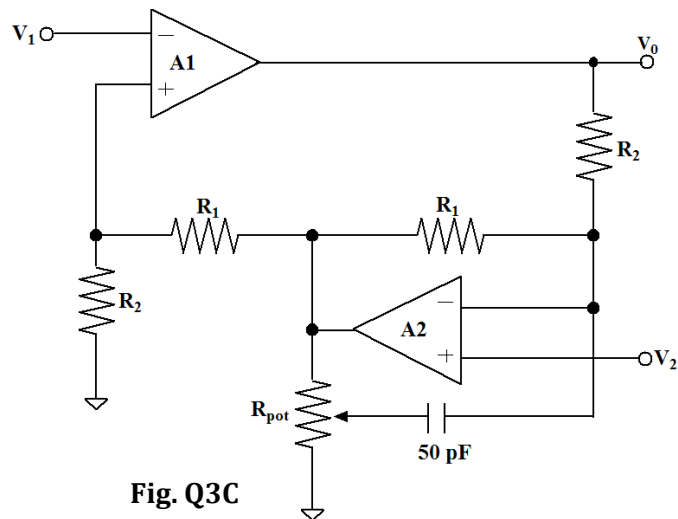


Fig. Q3C

Standard Resistor Values ($\pm 5\%$)

| | | | | | | |
|-----|----|-----|------|-----|------|------|
| 1.0 | 10 | 100 | 1.0K | 10K | 100K | 1.0M |
| 1.1 | 11 | 110 | 1.1K | 11K | 110K | 1.1M |
| 1.2 | 12 | 120 | 1.2K | 12K | 120K | 1.2M |
| 1.3 | 13 | 130 | 1.3K | 13K | 130K | 1.3M |
| 1.5 | 15 | 150 | 1.5K | 15K | 150K | 1.5M |
| 1.6 | 16 | 160 | 1.6K | 16K | 160K | 1.6M |
| 1.8 | 18 | 180 | 1.8K | 18K | 180K | 1.8M |
| 2.0 | 20 | 200 | 2.0K | 20K | 200K | 2.0M |
| 2.2 | 22 | 220 | 2.2K | 22K | 220K | 2.2M |
| 2.4 | 24 | 240 | 2.4K | 24K | 240K | 2.4M |
| 2.7 | 27 | 270 | 2.7K | 27K | 270K | 2.7M |
| 3.0 | 30 | 300 | 3.0K | 30K | 300K | 3.0M |
| 3.3 | 33 | 330 | 3.3K | 33K | 330K | 3.3M |
| 3.6 | 36 | 360 | 3.6K | 36K | 360K | 3.6M |
| 3.9 | 39 | 390 | 3.9K | 39K | 390K | 3.9M |
| 4.3 | 43 | 430 | 4.3K | 43K | 430K | 4.3M |
| 4.7 | 47 | 470 | 4.7K | 47K | 470K | 4.7M |
| 5.1 | 51 | 510 | 5.1K | 51K | 510K | 5.1M |
| 5.6 | 56 | 560 | 5.6K | 56K | 560K | 5.6M |
| 6.2 | 62 | 620 | 6.2K | 62K | 620K | 6.2M |
| 6.8 | 68 | 680 | 6.8K | 68K | 680K | 6.8M |
| 7.5 | 75 | 750 | 7.5K | 75K | 750K | 7.5M |
| 8.2 | 82 | 820 | 8.2K | 82K | 820K | 8.2M |
| 9.1 | 91 | 910 | 9.1K | 91K | 910K | 9.1M |

Standard Capacitor Values ($\pm 10\%$)

| | | | | | | |
|------|-------|--------|--------------|-------------|-------------|------------|
| 10pF | 100pF | 1000pF | .010 μ F | .10 μ F | 1.0 μ F | 10 μ F |
| 12pF | 120pF | 1200pF | .012 μ F | .12 μ F | 1.2 μ F | |
| 15pF | 150pF | 1500pF | .015 μ F | .15 μ F | 1.5 μ F | |
| 18pF | 180pF | 1800pF | .018 μ F | .18 μ F | 1.8 μ F | |
| 22pF | 220pF | 2200pF | .022 μ F | .22 μ F | 2.2 μ F | 22 μ F |
| 27pF | 270pF | 2700pF | .027 μ F | .27 μ F | 2.7 μ F | |
| 33pF | 330pF | 3300pF | .033 μ F | .33 μ F | 3.3 μ F | 33 μ F |
| 39pF | 390pF | 3900pF | .039 μ F | .39 μ F | 3.9 μ F | |
| 47pF | 470pF | 4700pF | .047 μ F | .47 μ F | 4.7 μ F | 47 μ F |
| 56pF | 560pF | 5600pF | .056 μ F | .56 μ F | 5.6 μ F | |
| 68pF | 680pF | 6800pF | .068 μ F | .68 μ F | 6.8 μ F | |
| 82pF | 820pF | 8200pF | .082 μ F | .82 μ F | 8.2 μ F | |