



VI SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)

MAKE-UP EXAMINATIONS, JUNE 2019

SUBJECT: POWER ELECTRONICS [ELE 3201]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 10 June 2019

Max. Marks: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A.** Sketch the safe operating area of power MOSFET clearly indicating all the operating limits. **(02)**
- 1B.** Draw a neat circuit for forced voltage commutation of an SCR. Hence, plot the waveforms for voltage across the capacitor, voltage across the SCR and voltage across the load. **(04)**
- 1C.** With the help of a neat sketch of Triac's structure, explain its working in first quadrant when turned on with positive gate current. **(04)**
- 2A.** A single phase to single phase Cycloconverter is delivering power to a resistive load. The frequency ratio $f_o/f_s = 1/3$. The firing delay angle α for all the thyristors are the same. Sketch the output voltage waveform in synchronization with input voltage for $\alpha = 45^\circ$. **(02)**
- 2B.** A controlled half-wave rectifier has an ac input of 120 V rms at 60 Hz, $R = 2 \Omega$, $L = 20 \text{ mH}$ and $V_{dc} = 100 \text{ V}$. The delay angle is 45° . Determine an expression for the output current and hence find the rms value of the current. **(04)**
- 2C.** A controlled single phase bridge rectifier has 20Ω resistive load and has a 120 V rms, 60 Hz ac source. The delay angle is 45° . Determine average load current, rms load current and the input power factor. **(04)**
- 3A.** A buck converter has the following parameters: $V_s = 15 \text{ V}$, $D = 0.6$, $L = 10 \mu\text{H}$, $C = 50 \mu\text{F}$ and $R = 5 \Omega$. The switching frequency is 150 kHz. Determine output voltage, maximum and minimum inductor currents. **(04)**
- 3B.** A boost converter has an input of 5 V and an output of 25 W at 15 V. The minimum inductor current must be no less than 50 percent of the average. The output voltage ripple must be less than 1 percent. The switching frequency is 300 kHz. Determine the duty ratio, inductor and capacitor values. **(04)**
- 3C.** Discuss the differences between voltage source inverters and current source inverters **(02)**
- 4A.** With the help of neat circuit schematic and triggering sequence, plot any two phase voltage waveforms and corresponding line voltage waveform for a three phase square wave bridge inverter when conduction angle of each device is 180° . **(05)**

- 4B.** With a neat circuit schematic, explain the working of a single phase full bridge square wave inverter. Hence, plot the output voltage waveform in synchronization with the switching scheme. Also, draw the harmonic spectrum. **(05)**
- 5A.** Discuss how unipolar switching technique can be applied to a single phase full bridge inverter. Support your answer with relevant waveforms **(05)**
- 5B.** With the help of neat circuit schematic, draw the voltage across the resonant capacitor and the current through the resonant inductor for a zero voltage switched buck converter. **(05)**