|  |   | Reg. No.                 |            |            |              |             |        |            |              |       |          |              |      |        |
|--|---|--------------------------|------------|------------|--------------|-------------|--------|------------|--------------|-------|----------|--------------|------|--------|
| North Rep W  | MANIPAL IN<br>(A constituent unit of I  | STITUTE<br>MAHE, Manipa  | OF<br>5761 | TE<br>104) | CHI          | IOI         | LOG    | ξY         |              |       | <u> </u> |              |      |        |
| III SEM B.Tech (BME) DEGREE END SEMESTER EXAMINATIONS, NOVEMBER 2019 |   |                          |            |            |              |             |        |            |              |       |          |              |      |        |
|  | SUBJE   | CT: DIGIT                | AL E       |            | CTR<br>NT 6  | ONI         | CS (I  | BME        | E 215        | (3)   |          |              |      |        |
|  | Thursda   | y, 21 <sup>st</sup> Nove | mbe        | r, 20      | <b>19:</b> 8 | <b>3.30</b> |        | )<br>to 11 | <b>.30</b> A | ٩M    |          |              |      |        |
| TIME   | : 3 HOURS   | <b>-</b>                 |            |            | <u> </u>     |             |        |            |              |       | MA       | <b>AX.</b> I | MAR  | KS: 50 |
| 1 4  | ATT /•  | Instru                   | ction      | ns to      | Can          | didat       | tes:   |            |              |       |          |              |      |        |
| 1. Ans<br>2. Dra   | wer ALL questions.<br>w labeled diagrams where  | ver necessary            | <b>7</b> • |            |              |             |        |            |              |       |          |              |      |        |
| 1A.  | Depicting the necessary   | steps and ca             | lcula      | tions      | s perf       | orm         | the fo | ollow      | ving:        |       |          |              |      | 04     |
|  | (a)Add using BCD cod  | de                       |            |            |              |             |        |            |              |       |          |              |      |        |
|  | ( <i>i</i> ) 75 + 38<br>( <i>ii</i> ) 197 + 184   |                          |            |            |              |             |        |            |              |       |          |              |      |        |
|  | (b) Convert into,   |                          |            |            |              |             |        |            |              |       |          |              |      |        |
|  | $(i) (36)_8 = ()_{10} = ($<br>$(ii) (A32)_{16} = ()_{10}$   | $()_{16} = ()_8$         |            |            |              |             |        |            |              |       |          |              |      |        |
| 1B.  | <ol> <li>Simplify the following functions to a minimum number of literals using Boolean simplifications.</li> </ol> |                          |            |            |              |             |        | 03         |              |       |          |              |      |        |
|  | (i) F(x, y, z) = xyz  | $+ \bar{x}y + xy\bar{z}$ |            |            |              |             |        |            |              |       |          |              |      |        |
|  | (ii) F(w, x, y, z) = y  | $w(w\bar{z} + wz)$       | +xy        | ,          |              |             |        |            |              |       |          |              |      |        |
|  | (iii) F(x, y, z) = (x   | (y+z)(y+z)               | xz)        |            |              |             |        |            |              |       |          |              |      |        |
| 1C.  | Realize the following Bo<br>terms.  | oolean functio           | on in      | to (i)     | Sum          | n of N      | Ain-t  | erms       | . (ii)       | ) Pro | ducts    | of M         | Iax- | 03     |

 $F(A,B,C) = AB + \bar{A}C$ 

- 2A. Draw the circuit of a 4 bit parallel adder/ 2's complement positive difference subtractor 04 using the IC 7483. Explain the operation of the circuit with suitable examples.
- 2B Obtain the simplified Boolean expression for the following Boolean function using 03
   Karnaugh map. Also simplify the expression without using don't cares, and realize using basic gates.

$$f(A, B, C, D) = \sum m (0, 2, 4, 5, 6, 7, 8) + \sum d (10, 11, 12, 13, 14)$$
$$d \rightarrow don't \ cares$$

- What is a De-multiplexer? Realize and draw the circuit of 1×4 line De-multiplexer with 03 active low outputs.
- 3A. Realize and draw the circuit of a full adder using  $3 \times 8$  line decoder with appropriate gates. 04

3B. Realize and draw the circuit of 2 bit magnitude comparator. 03

- 3C. Draw the circuit of a D flip flop using appropriate gates. Give its complete truth table and 03 obtain its excitation table.
- 4A. Realize Octal numbers (0 to7) to seven segment display using ROM circuit. Draw the 04 complete circuit.
- 4B. Design a  $4 \times 1$  MUX to realize the following function.

$$F(A, B, C, D) = \sum m(0, 2, 3, 5, 7, 10, 11, 12, 14, 15)$$

4C Design and draw an Encoder using diode matrix to satisfy the following truth table. 03

| Inputs<br>w <sub>3</sub> w <sub>2</sub> w <sub>1</sub> w <sub>0</sub> |   |   |   | Outputs<br>y3 y2 y1 y0 |  |  |  |  |  |  |  |
|---|---|---|---|------------------------|--|--|--|--|--|--|--|
| 0   | 0 | 0 | 1 | 1011                   |  |  |  |  |  |  |  |
| 0   | 0 | 1 | 0 | 0101                   |  |  |  |  |  |  |  |
| 0   | 1 | 0 | 0 | 1010                   |  |  |  |  |  |  |  |
| 1   | 0 | 0 | 0 | 0111                   |  |  |  |  |  |  |  |

03

5A. Design a synchronous counter to count the following count sequence using JK flip flops. 04Also verify the counting with timing waveforms.

000, 001, 010, 100, 110, 111, 000, ... ....

- 5B. Draw the circuit of a 3 bit shift register using D flip flops to operate as (i) PIPO (ii) PISO. 03Explain the operation with the appropriate truth table.
- 5C. Draw the circuit of a Mod-11 asynchronous counter. List the count sequence and draw the 03 timing waveforms.