

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



MANIPAL INSTITUTE OF TECHNOLOGY

(A constituent unit of MAHE, Manipal 576104)

III SEMESTER B.Tech. (BME) DEGREE MAKE UP EXAMINATIONS NOV/DEC 2019-20

SUBJECT: NETWORK ANALYSIS (BME 2154)

(REVISED CREDIT SYSTEM)

Saturday, 28th December 2019: 8.30 AM to 11.30 AM.

TIME: 3 HOURS

MAX. MARKS: 50

Instructions to Candidates:

1. Answer ALL questions.
2. Draw labeled diagram wherever necessary. Any missing data may suitably be assumed.

- 1A.** For the circuit shown in Fig.1A, find the currents I_1 and I_2 . Also calculate the power dissipation in all the resistors. (4)

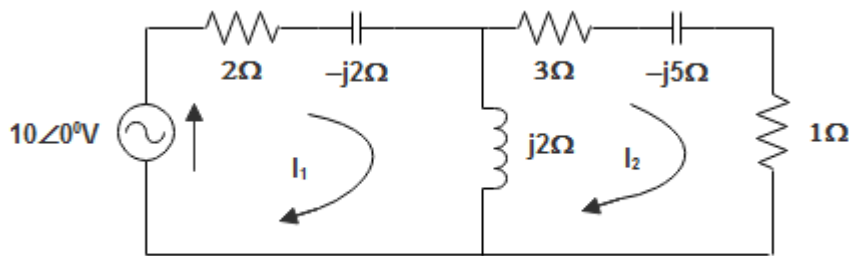


Fig.1A

- 1B.** For the circuit shown in Fig.1B, using node voltage analysis, find the currents in all resistors. (3)

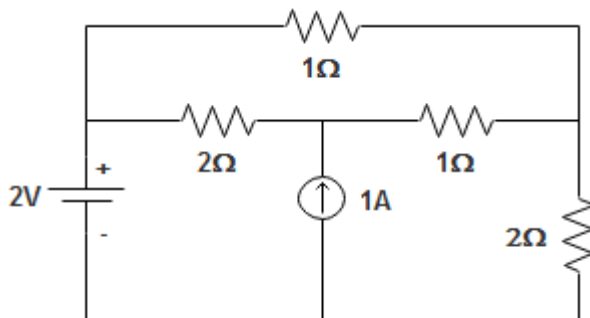


Fig.1B

- 1C.** For a series RLC resonant circuit, $R=5\Omega$, $L=4\text{mH}$, $C=0.1\mu\text{F}$ and $V=10$ volts. Find the frequency of resonance, quality factor, voltage drop across L, C and R at resonance, maximum current of the circuit and half power band width. (3)

- 2A. For the circuit shown in Fig.2A, determine the current I in 10Ω resistor using superposition theorem. (4)

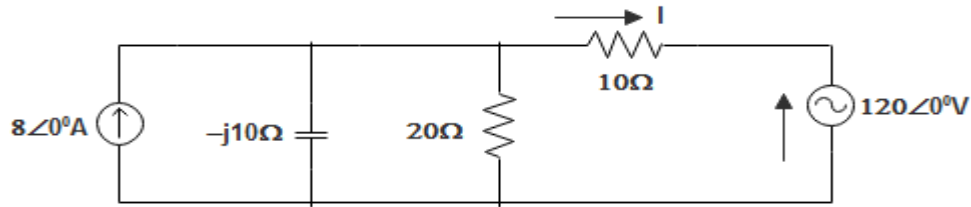


Fig. 2A

- 2B. For the network shown in Fig.2B, determine the current I in 2Ω resistor connected across the terminals AB using Thevenin's theorem. (3)

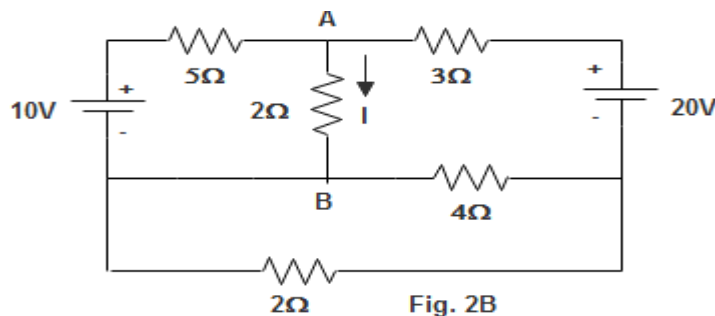


Fig. 2B

- 2C. In the network shown in Fig 2C, find the value of load resistance R_L when it receives maximum power. What is the maximum power? (3)

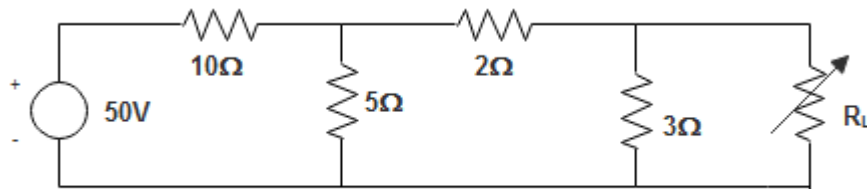


Fig.2C

- 3A. For the circuit shown in Fig.3A, a steady state is reached with K is open for $t < 0$. At $t = 0$ the switch K is closed. Find, $v_a(0^-)$, $v_b(0^-)$, $v_a(0^+)$, $v_b(0^+)$ and $v_b(\infty)$ (4)

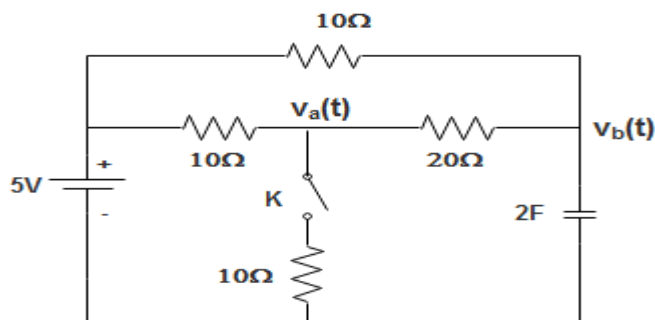


Fig. 3A

- 3B.** In the network shown in Fig.3B, the switch K is closed at $t=0$. Using Laplace transform solve for the current $i(t)$ and sketch the waveform. (3)

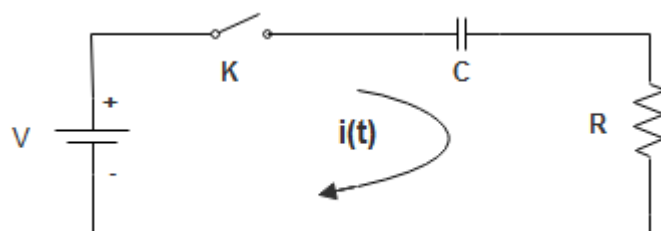


Fig. 3B

- 3C.** Determine the inverse Laplace transform of the following. (3)

(i) $F(s) = \frac{1}{(s+1)(s+2)^2}$

(ii) $F(s) = \frac{5s^2+4s+1}{(s+3)(s+1)^2}$

- 4A.** For the circuit shown in the fig. 4A, determine Z-Parameters. (4)

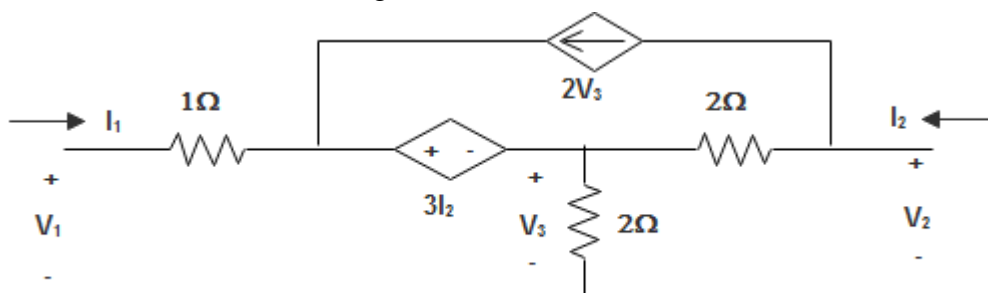


Fig. 4A

- 4B.** For the waveform shown in Fig.4B, determine its Laplace transform. (3)

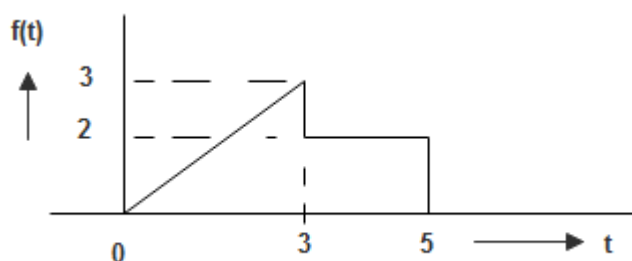


Fig. 4B

- 4C.** For the periodic waveform $v(t)$ shown in Fig.4C, determine its Laplace transform. (3)

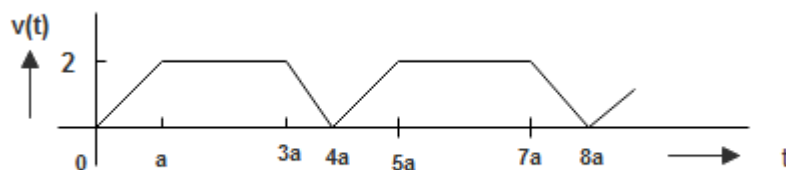


Fig.4C

- 5A.** For the network shown in Fig. 5A, find the expressions of, (4)

$$(i) \alpha_{12}(s) = \frac{I_2(s)}{I_1(s)} \quad (ii) Z_{12}(s) = \frac{V_2(s)}{I_1(s)}$$

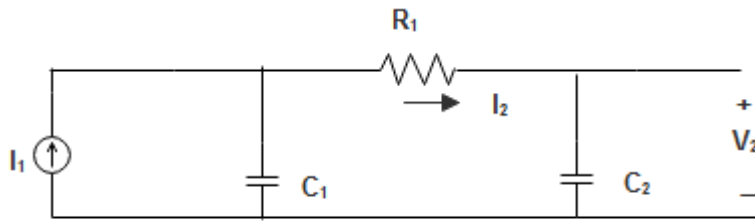


Fig. 5A

- 5B.** A step voltage is applied to a low pass RC circuit whose time constant is RC. Show that (3)
for the output waveform the rise time t_r is given by,

$$t_r = 2.2 \times RC$$

- 5C.** A square wave whose peak to peak amplitude is 1 Volt extends ± 0.5 Volts w.r.t. ground. (3)
The duration of the positive section is 0.1 seconds and of the negative section is 0.2 seconds. If this waveform is impressed upon a high pass RC circuit whose time constant is 0.2 seconds. Calculate and sketch the output waveform and label all voltage levels.