



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)

III SEMESTER B.TECH. (MECHATRONICS ENGINEERING)

MAKE UP EXAMINATIONS, DEC 2019

SUBJECT: DIGITAL SYSTEM DESIGN [MTE 2152]

CREDIT SYSTEM

(26 /12 /2019)

- 1A Realize the Boolean function $f(W, X, Y, Z) = \sum m(1,3,5,7,8,12,14)$ using
- i. Basic gates
 - ii. Only NAND gates
 - iii. Only NOR gates
- 5 CO1
- 1B Design a one digit BCD adder using 74LS283. 3 CO2
- 1C Draw the flow chart of Digital system design flow. 2 CO4
- 2A Realize the Boolean function $f(w, x, y, z) = \sum m(0,1,5,6,7,9,13,14)$ using
- a) 8 to 1 multiplexer
 - b) 4 to 1 multiplexer with gates at the input
 - c) 4 to 1 multiplexer with 2 to 1 multiplexers at the input.
- 5 CO2
- 2B Define a programming element in an FPGA. List the 4 programming elements, mentioning the differences between them. 3 CO4
- 2C Demonstrate a 4 to 16 decoder using 2 to 4 decoders. 2 CO2
- 3A Design a synchronous 3 bit gray code up counter using D flip flops. 5 CO3
- 3B Implement a mod 60 counter using 74LS90. 3 CO3
- 3C What is race around condition? Mention the condition and type of flip flop in which it occurs. How can it be avoided? 2 CO3
- 4A Design an Asynchronous Mod 8 up counter using JK flip flops. Draw the waveforms at each flipflop to show the entire count. 5 CO3
- 4B Draw the state diagram (Mealy m/c) of a sequence detector which has a single input x and a single output z. The output variable z will be high if it detects 1001 and 011 in a continuous data stream. 3 CO3
- 4C Draw the logic circuit of a 4 bit Ring Counter with single circulating '1' using IC74194 wired as left shift. 2 CO3
- 5A Design a sequence detector (Moore FSM) to detect the sequence 010 in a continuous data input stream. Use D Flip flops. 5 CO3
- 5B Write a gate level Verilog code for a 1 bit full adder. Using this as a component write a structural Verilog code for a 4 bit full adder. 3 CO5
- 5C Write a behavioural Verilog code for a one bit full adder 2 CO5